

4. tiha vaja iz VISOKOFREKVENČNE TEHNIKE - 23.12.2016

1. LC nihajni krog niha na svoji rezonančni frekvenci $f=10.7\text{MHz}$. Kolikšna je kvaliteta $Q=?$ nihajnega kroga, če je povprečna moč izgub v vezju $P=10\text{mW}$ pri napetosti $U=10V_{\text{eff}}$ na kondenzatorju $C=100\text{pF}$?

- (A) 135 (B) 17 (C) 33 (D) 67

2. Lestvičasto pasovno sito vsebuje zaporedne kroge L_1+C_1 v zaporednih vejah in vzporedne kroge $L_2\parallel C_2$ v vzporednih vejah. V ozkopasovnem situ $B\ll f_0$ je težko izdelati:

- (A) zaporedni kondenzator C_1 (B) vzporedni kondenzator C_2 (C) zaporedno tuljavo L_1 (D) vzporedno tuljavo L_2

3. Lastnosti oscilatorja so predstavljene v Riekejevem diagramu. Naslednje veličine so izrisane v Riekejevem diagramu kot funkcija prilagoditve bremena Γ :

- (A) frekvenca in izhodna VF moč (B) frekvenca in fazni šum (C) stabilnost in izhodna VF moč (D) izkoristek in fazni šum

4. Motnjo na frekvenci $f=1\text{GHz}$ oslabimo tako, da vzporedno vходу sprejemnika vežemo štrcelj iz koaksialnega kabla s pomočjo T-člena. Kolikšna naj bo dolžina štrclja in kako naj bo zaključen, če kabel vsebuje dielektrik $\epsilon_r=2.25$? ($c_0=3\cdot 10^8\text{m/s}$)

- (A) 2.5cm kratek stik (B) 5cm odprte sponke (C) 10cm odprte sponke (D) 15cm $\Gamma=0$

5. Rezine "AT" kremenovega kristala ($v=3320\text{m/s}$) običajno ne moremo brusiti tanjše od $d<50\mu\text{m}$, ker se tanjša rezina lahko prelomi. Če je na ohišju kristala napisana frekvenca $f=108.15\text{MHz}$, gre najverjetneje za naslednji mehanski rod nihanja rezine:

- (A) 3. overton (B) osnovni rod (C) 7. overton (D) 5. overton

6. Kateri rodovi nihanja kremenovega kristala ne sklapljajo mehanske energije v okoliški zrak in torej ne potrebujejo vakuumskega ohišja za najvišji Q ?

- (A) tlačni rodovi (B) strižni rodovi (C) katerikoli notranji rodovi (D) rodovi glasbenih vilic

7. Rezina "AT" kremenovega kristala debeline $d=100\mu\text{m}$ in premera $2r=8\text{mm}$ ima 2D in 3D rezonance tik nad frekvenco osnovnega 1D rodu. Neželjene 2D in 3D rezonance lahko zadušimo z naslednjo lastnostjo nanosenih elektrod:

- (A) oblika (B) debelina (C) prevodnost (D) hrapavost

8. Mehanski rezonator iz piezo keramike (peizelektrični sklop) ima naslednje elektromehanske lastnosti v primerjavi s kremenovim kristalom:

- (A) višji Q in šibkejši sklop (B) višji Q in močnejši sklop (C) nižji Q in močnejši sklop (D) nižji Q in šibkejši sklop

9. Mikroprocesor uporablja kremenov kristal v oscilatorju ure na $f=20\text{MHz}$. V vezju oscilatorja kvaliteta rezonatorja dosega $Q_L=5000$. Kolikšno časovno konstanto $\tau=RC$ je smiselno vgraditi v zakasnitev vezja za RESET mikroprocesorja?

- (A) $1\mu\text{s}$ (B) $100\mu\text{s}$ (C) 10ms (D) 1s

10. V LC ($Q_L=30$) oscilatorju za $f=100\text{MHz}$ uporabimo silicijev NPN tranzistor z VF šumnim številom $F=3\text{dB}$. Vezje za nastavitve delovne točke skrbno načrtujemo tako, da ne poslabšamo faznega šuma. Pri odmiku $\Delta f=100\text{kHz}$ je potek faznega šuma naslednji:

- (A) $L(\Delta f)=\alpha \cdot f^{-3}$ (B) $L(\Delta f)=\alpha \cdot f^{-2}$ (C) $L(\Delta f)=\alpha \cdot f^{-1}$ (D) $L(\Delta f)=\text{konst.}$

11. Signala dveh podobnih oscilatorjev za $f_1=3.0\text{GHz}$ in $f_2=3.1\text{GHz}$ mešamo, da dobimo razliko $f_2-f_1=100\text{MHz}$. Kolikšen je fazni šum razlike $L'(\Delta f)=?$ pri odmiku $\Delta f=100\text{kHz}$, če je fazni šum vsakega oscilatorja posebej $L(\Delta f)=-90\text{dBc/Hz}$ pri istem odmiku?

- (A) -87dBc/Hz (B) -90dBc/Hz (C) -93dBc/Hz (D) -84dBc/Hz

12. Polprevodniški izvor šuma izdelamo s silicijevo diodo s PN spojem, v kateri izkoriščamo plazovni preboj. Pri kakšni zaporni napetosti plazovna dioda proizvaja najmočnejši šum v področju visokih frekvenc?

- (A) 0.7V (B) 2V (C) 6V (D) 18V

Priimek in ime:

Elektronski naslov:

1. A LC circuit is oscillating at its resonant frequency $f=10.7\text{MHz}$. What is the $Q=?$ of the circuit, if the average dissipated power equals to $P=10\text{mW}$ corresponding to a voltage $U=10V_{\text{eff}}$ on the capacitor $C=100\text{pF}$?

- (A) 135 (B) 17 (C) 33 (D) 67

2. A ladder band-pass includes series L_1+C_1 circuits in series branches and parallel circuits $L_2\parallel C_2$ in parallel branches. In a narrow-band filter $B\ll f_0$ it is hard to make:

- (A) series capacitor C_1 (B) parallel capacitor C_2 (C) series inductor L_1 (D) parallel inductor L_2

3. The performance of an oscillator is presented in a Rieke diagram. The following quantities are plotted in the Rieke diagram as a function of load matching Γ :

- (A) frequency and output RF power (B) frequency and phase noise (C) stability and output RF power (D) efficiency and phase noise

4. An interference at $f=1\text{GHz}$ is attenuated by connecting a coaxial-cable stub in parallel to the receiver input using a T-adaptor. What should be the stub length and how should the stub be terminated, if the cable uses a dielectric $\epsilon_r=2.25$? ($c_0=3\cdot 10^8\text{m/s}$)

- (A) 2.5cm short (B) 5cm open (C) 10cm open (D) 15cm $\Gamma=0$

5. An AT-cut quartz plate ($v=3320\text{m/s}$) is usually not made thinner than $d<50\mu\text{m}$, since even thinner plates break easily. If the crystal is marked $f=108.15\text{MHz}$ on the package, this frequency most likely represents the following mechanical mode of oscillation:

- (A) 3rd overtone (B) fundamental mode (C) 7th overtone (D) 5th overtone

6. Which modes of oscillation of a quartz crystal do not couple mechanical energy in the surrounding air and therefore do not require a vacuum envelope for the highest Q ?

- (A) pressure modes (B) shear modes (C) any bulk modes (D) tuning-fork modes

7. An AT-cut quartz plate with a thickness $d=100\mu\text{m}$ and diameter $2r=8\text{mm}$ has 2D and 3D resonances just slightly above the 1D-fundamental-mode frequency. The unwanted 2D and 3D resonances can be suppressed by the following property of the plated electrodes:

- (A) shape (B) thickness (C) conductivity (D) roughness

8. A mechanical resonator made of piezoelectric ceramic (piezoelectric coupling) has the following electro-mechanical properties when compared to a quartz crystal:

- (A) higher Q and weaker coupling (B) higher Q and stronger coupling (C) lower Q and stronger coupling (D) lower Q and weaker coupling

9. A microprocessor uses a crystal oscillator at $f=20\text{MHz}$ as its clock source. The resonator achieves a $Q_L=5000$ in the oscillator circuit. What is a sensible choice for the time constant $\tau=RC$ determining the microprocessor RESET delay?

- (A) $1\mu\text{s}$ (B) $100\mu\text{s}$ (C) 10ms (D) 1s

10. A LC ($Q_L=30$) oscillator for $f=100\text{MHz}$ employs a silicon NPN transistor with a RF noise figure of $F=3\text{dB}$. The bias circuit is carefully design to avoid degrading the phase noise. At a frequency offset of $\Delta f=100\text{kHz}$ the phase noise is proportional to:

- (A) $L(\Delta f)=\alpha \cdot f^{-3}$ (B) $L(\Delta f)=\alpha \cdot f^{-2}$ (C) $L(\Delta f)=\alpha \cdot f^{-1}$ (D) $L(\Delta f)=\text{konst.}$

11. The signals of two similar oscillators at $f_1=3.0\text{GHz}$ and $f_2=3.1\text{GHz}$ are mixed to obtain the difference $f_2-f_1=100\text{MHz}$. What is the difference phase noise $L'(\Delta f)=?$ at an offset $\Delta f=100\text{kHz}$, if each oscillator alone has $L(\Delta f)=-90\text{dBc/Hz}$ at the same offset?

- (A) -87dBc/Hz (B) -90dBc/Hz (C) -93dBc/Hz (D) -84dBc/Hz

12. A semiconductor noise source includes a PN-junction silicon diode using the avalanche breakdown. At what reverse voltage the avalanche diode produces the largest amount of radio-frequency noise?

- (A) 0.7V (B) 2V (C) 6V (D) 18V

Name:

Email: