

## 5. tiha vaja iz VISOKOFREKVENČNE TEHNIKE - 23.1.2017

1. Frekvenčni sintetizator za  $f=450\text{MHz}$  vsebuje VCO s kvaliteto  $Q_{VCO}=30$ . Kolikšno izboljšanje faznega šuma  $L(\Delta f)$  lahko pričakujemo pri frekvenčnem odmiku  $\Delta f=500\text{kHz}$ , ko VCO uklenemo s PLL s primerjalno frekvenco  $f_{REF}=25\text{kHz}$  na referenco  $Q_{XTAL}=3000$ ?

- (A) 0dB (B) 20dB (C) 40dB (D) 60dB
2. V fazno-sklenjeni zanki uporabimo sito z dvema kondenzatorjem  $C_1=1\mu\text{F}$ ,  $C_2=3.3\mu\text{F}$  in uporom  $R=10\text{k}\Omega$ . Kolikšno je razmerje med frekvenco pola in frekvenco ničle  $\omega_{POL}/\omega_{NIČLA}=?$  prevajalne funkcije  $H(\omega)$  povratne vezave?

- (A) 3.30 (B) 4.30 (C) 10.9 (D) 18.5
3. Za neznani VCO izmerimo odziv: 0V=420MHz, 1V=425MHz, 2V=431MHz, 3V=436MHz, 4V=440MHz, 5V=444MHz, 6V=447MHz, 7V=450MHz in 8V=452MHz. Kolikšen je največji  $K_{VCOMAX}=?$  merjenega vezja?

- (A) 3MHz/V (B) 4MHz/V (C) 5MHz/V (D) 6MHz/V
4. Letalska radijska postaja mora pokriti frekvenčni pas  $f=118.000-137.000\text{MHz}$  v kanalih s frekvenčnim razmakom  $\Delta f=8.333\text{kHz}$ . V kolikšnem območju se giblje faktor deljenja  $N=?$  sintetizatorja s fazno-sklenjeno zanko in skrbno izbrano primerjalno frekvenco?

- (A) 118000-137000 (B) 23600-27400 (C) 14160-16440 (D) 4270-5480
5. PLL sintetizator smatramo uklenjen, ko se fazna napaka zmanjša pod  $|\Delta\phi| \leq 10\text{mrd}$ . Kolikšna je tedaj širina impulzov  $\Delta t=?$  na izhodu frekvenčno/faznega primerjalnika, če sintetizator dela s primerjalno frekvenco  $f_{REF}=25\text{kHz}$ ?

- (A) 64ns (B) 400ns (C) 6.4μs (D) 40μs
6. V LC oscilatorju uporabimo varikap diodo z razponom kapacitivnosti  $C_{MIN}=10\text{pF}$  do  $C_{MAX}=50\text{pF}$ . Varikap diodi je vezana vzporedno kapacitivnost vezja  $C_0=20\text{pF}$ . Kolikšen frekvenčni razpon  $\Delta f=?$  pokrije VCO s tuljavo  $L=1\mu\text{H}$ ?

- (A) 5MHz (B) 7MHz (C) 10MHz (D) 14MHz
7. Pri ugaševanju radijskega sprejemnika najdemo isto radijsko postajo na frekvenci  $f_1=15.55\text{MHz}$  ter na frekvenci  $f_2=16.46\text{MHz}$ . Iz opažanj sklepamo, da radijski sprejemnik uporablja mešanje na medfrekvenco vrednosti:

- (A) 16.005MHz (B) 32.01MHz (C) 910kHz (D) 455kHz
8. V radijski sprejemnik vgradimo mešalnik, ki ima vhodno presečno točko tretjega reda  $P_{IIP3}=+7\text{dBm}$ . Šumno število izboljšamo z linearnim LNA  $G=15\text{dB}$ . Zrcalni odziv zadušimo s sitom, ki ima vstavitev slabljenje  $a=3\text{dB}$ . Kolikšen je  $P_{IIP3}'=?$  celega sprejemnika?

- (A) -8dBm (B) -5dBm (C) -2dBm (D) -11dBm
9. Vitroplast FR4 ima v področju radijskih frekvenc tangens izgubnega kota  $\tan\delta=0.02$ . Če iz dvostranskega vitropasta izdelamo kondenzator tako, da pustimo bakreno folijo na obeh straneh, bo imel kondenzator najvišjo kvaliteto  $Q=?$

- (A) 25 (B) 50 (C) 100 (D) 200
10. V tehniki mikrotraktih vodov izdelamo glavnikasto pasovno sito za  $f_0=1\text{GHz}$ . Četrtrvalovni rezonatorji so na enem koncu ozemljeni preko via lukanj ter na drugem koncu odprtvi. Sito bo imelo prvi neželen odziv pri frekvenci približno:

- (A) 1.5GHz (B) 2GHz (C) 3GHz (D) 4GHz
11. V super-regenerativnem sprejemniku dosežemo gašenje visokofrekvenčnega oscilatorja s primernim načrtovanjem vezja za nastavitev njegove delovne točke. Frekvenco gašenja v tem primeru izbiramo z:

- (A) sklopom antene (B) Q nihajnega kroga (C)  $f_T$  tranzistorja (D) RC vezjem
12. Visokofrekvenčno vezje vgradimo v zaprto kovinsko ohišje v obliki kvadra z notranjimi izmerami  $a=20\text{cm}$ ,  $b=15\text{cm}$  in  $c=10\text{cm}$ . Pri kateri najnižji frekvenci  $f=?$  pričakujemo prvo notranjo rezonanco ohišja? ( $c=3 \cdot 10^8\text{m/s}$ )

- (A) 1.25GHz (B) 1.68GHz (C) 1.8GHz (D) 1.95GHz

Priimek in ime:

Elektronski naslov:

1. A frequency synthesizer for  $f=450\text{MHz}$  includes a VCO with a  $Q_{\text{VCO}}=30$ . What improvement of the phase noise  $L(\Delta f)$  can be expected at an offset  $\Delta f=500\text{kHz}$ , when the VCO is locked with a PLL with a comparison frequency  $f_{\text{REF}}=25\text{kHz}$  to a reference  $Q_{\text{XTAL}}=3000$ ?

- |                                                                                                                                                                                                                                                                                                                     |                 |                       |                      |
|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|-----------------------|----------------------|
| (A) 0dB                                                                                                                                                                                                                                                                                                             | (B) 20dB        | (C) 40dB              | (D) 60dB             |
| 2. A PLL uses a lead-lag loop filter with two capacitors $C_1=1\mu\text{F}$ , $C_2=3.3\mu\text{F}$ and resistor $R=10\text{k}\Omega$ . What is the ratio between the pole and zero frequency $\omega_{\text{POLE}}/\omega_{\text{ZERO}}=?$ of the feedback transfer function $H(\omega)$ ?                          |                 |                       |                      |
| (A) 3.30                                                                                                                                                                                                                                                                                                            | (B) 4.30        | (C) 10.9              | (D) 18.5             |
| 3. The response of an unknown VCO is measured: 0V=420MHz, 1V=425MHz, 2V=431MHz, 3V=436MHz, 4V=440MHz, 5V=444MHz, 6V=447MHz, 7V=450MHz and 8V=452MHz. What is the maximum $K_{\text{VCOMAX}}=?$ of the measured circuit?                                                                                             |                 |                       |                      |
| (A) 3MHz/V                                                                                                                                                                                                                                                                                                          | (B) 4MHz/V      | (C) 5MHz/V            | (D) 6MHz/V           |
| 4. An aviation radio should cover the frequency range $f=118.000\text{--}137.000\text{MHz}$ with a $\Delta f=8.333\text{kHz}$ channel spacing. What is the range of the divider modulo $N=?$ of a PLL synthesizer with a carefully chosen comparison frequency?                                                     |                 |                       |                      |
| (A) 118000–137000                                                                                                                                                                                                                                                                                                   | (B) 23600–27400 | (C) 14160–16440       | (D) 4270–5480        |
| 5. A PLL synthesizer is considered locked when the phase error is below $ \Delta\phi \leq10\text{mrd}$ . What is the corresponding pulse width $\Delta t=?$ at the output of the frequency/phase comparator if the synthesizer uses a comparison frequency $f_{\text{REF}}=25\text{kHz}$ ?                          |                 |                       |                      |
| (A) 64ns                                                                                                                                                                                                                                                                                                            | (B) 400ns       | (C) 6.4 $\mu\text{s}$ | (D) 40 $\mu\text{s}$ |
| 6. A LC oscillator is tuned with a varactor with a capacitance range from $C_{\text{MIN}}=10\text{pF}$ to $C_{\text{MAX}}=50\text{pF}$ . The circuit capacitance connected in parallel to the varactor is $C_0=20\text{pF}$ . What is the VCO frequency coverage $\Delta f=?$ when using a coil $L=1\mu\text{H}$ ?  |                 |                       |                      |
| (A) 5MHz                                                                                                                                                                                                                                                                                                            | (B) 7MHz        | (C) 10MHz             | (D) 14MHz            |
| 7. While tuning a radio receiver we find the same station at a frequency $f_1=15.55\text{MHz}$ and at a frequency $f_2=16.46\text{MHz}$ . From our observations we conclude that our receiver is using an intermediate frequency of:                                                                                |                 |                       |                      |
| (A) 16.005MHz                                                                                                                                                                                                                                                                                                       | (B) 32.01MHz    | (C) 910kHz            | (D) 455kHz           |
| 8. A radio receiver includes a mixer with the input third-order intercept point of $P_{\text{IIP3}}=+7\text{dBm}$ . The noise figure is improved by a linear LNA $G=15\text{dB}$ . The image response is attenuated with a filter with an insertion loss $a=3\text{dB}$ . What is the receiver $P_{\text{IIP3}}'=?$ |                 |                       |                      |
| (A) -8dBm                                                                                                                                                                                                                                                                                                           | (B) -5dBm       | (C) -2dBm             | (D) -11dBm           |
| 9. The glass-fiber-epoxy laminate FR4 has a loss tangent of $\tan\delta=0.02$ in the radio-frequency range. If a capacitor is made from a double-sided piece of FR4 with the copper foil in place on both sides, the capacitor will achieve a maximum $Q=?$                                                         |                 |                       |                      |
| (A) 25                                                                                                                                                                                                                                                                                                              | (B) 50          | (C) 100               | (D) 200              |
| 10. A comb band-pass filter for $f_0=1\text{GHz}$ is built as a microstrip circuit. The quarter-wavelength resonators are grounded on one end through via holes and are left open at the other end. The filter has its first unwanted response at about the frequency:                                              |                 |                       |                      |
| (A) 1.5GHz                                                                                                                                                                                                                                                                                                          | (B) 2GHz        | (C) 3GHz              | (D) 4GHz             |
| 11. In a super-regenerative receiver the radio-frequency oscillator quenching is achieved with an appropriate design of the bias circuit of its active component. The quenching frequency is selected by:                                                                                                           |                 |                       |                      |
| (A) antenna coupling                                                                                                                                                                                                                                                                                                | (B) resonator Q | (C) transistor $f_T$  | (D) RC network       |
| 12. A radio-frequency circuit is installed in a closed rectangular metal box with the internal dimensions $a=20\text{cm}$ , $b=15\text{cm}$ and $c=10\text{cm}$ . At which lowest frequency $f=?$ the first internal resonance of the metal box is expected? ( $c=3\cdot10^8\text{m/s}$ )                           |                 |                       |                      |
| (A) 1.25GHz                                                                                                                                                                                                                                                                                                         | (B) 1.68GHz     | (C) 1.8GHz            | (D) 1.95GHz          |