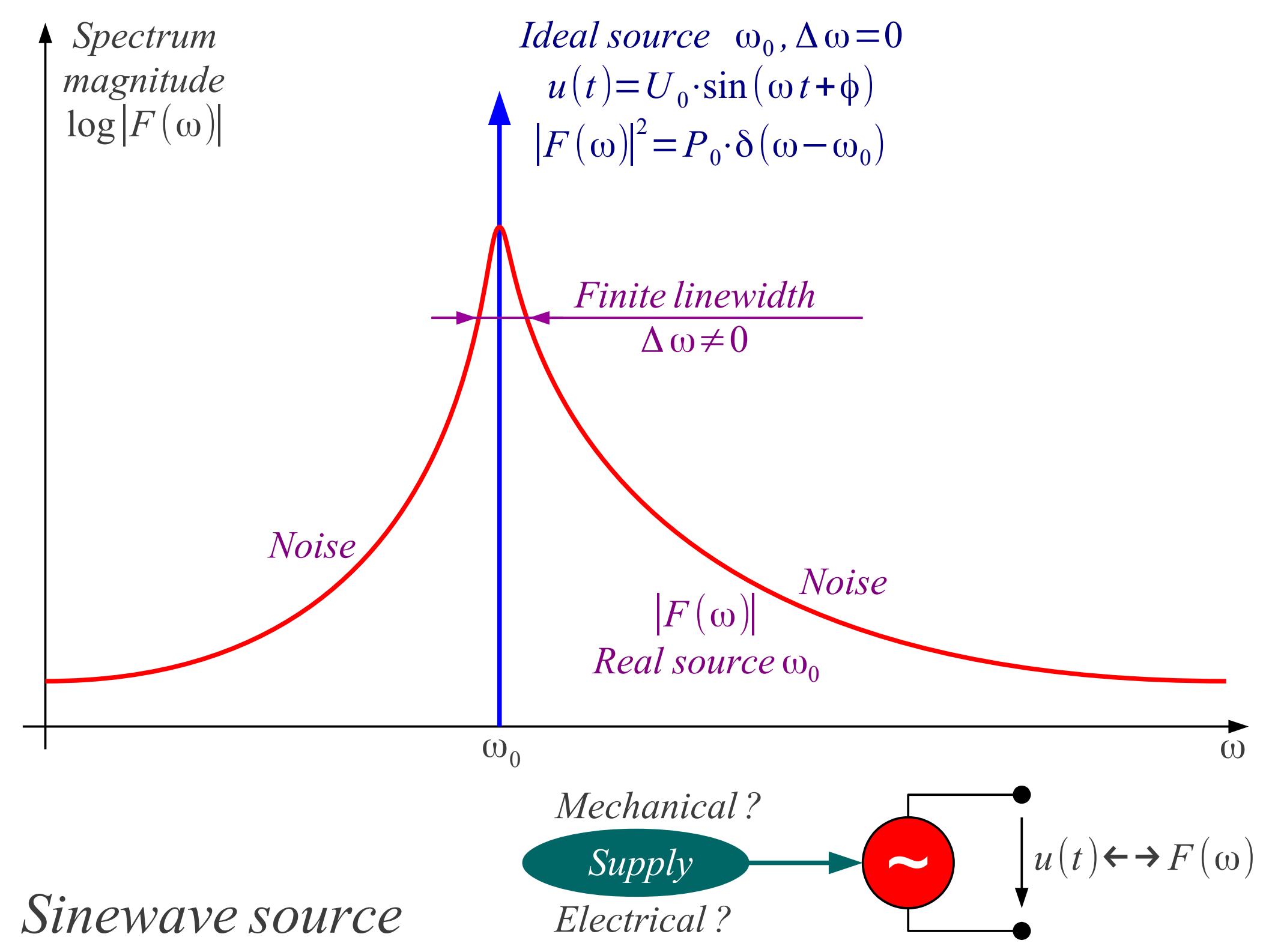


Communication Electronics

Lecture 14:


Electronic oscillator




Alexander
Meissner

1912

Edwin
Armstrong

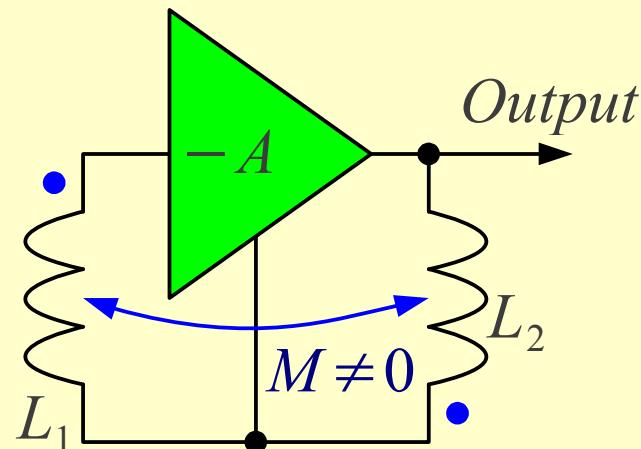


Colpitts 1918

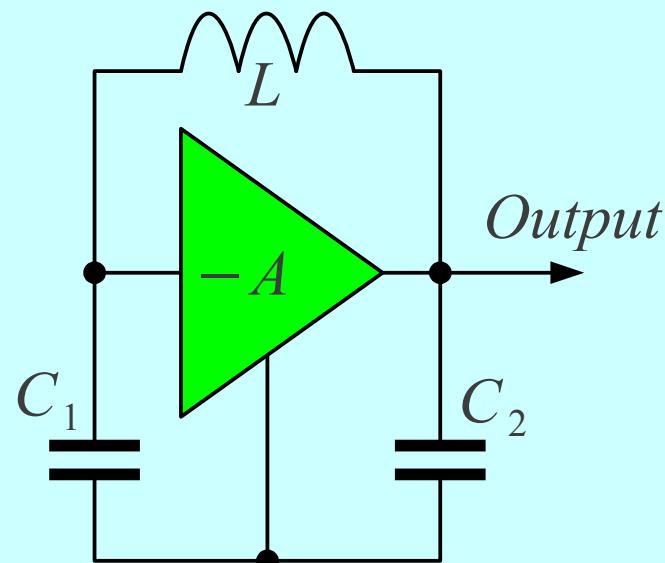


RF oscillators

Triode 1907 Lee DeForest

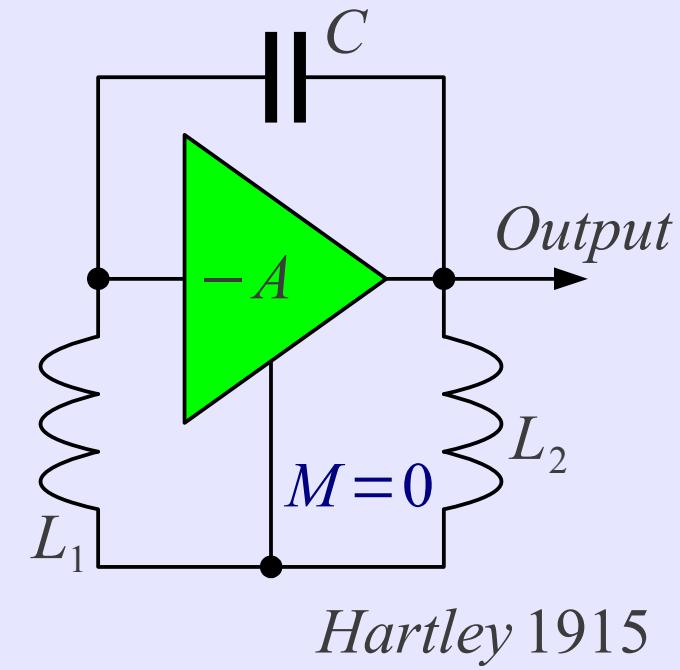



Hartley 1915

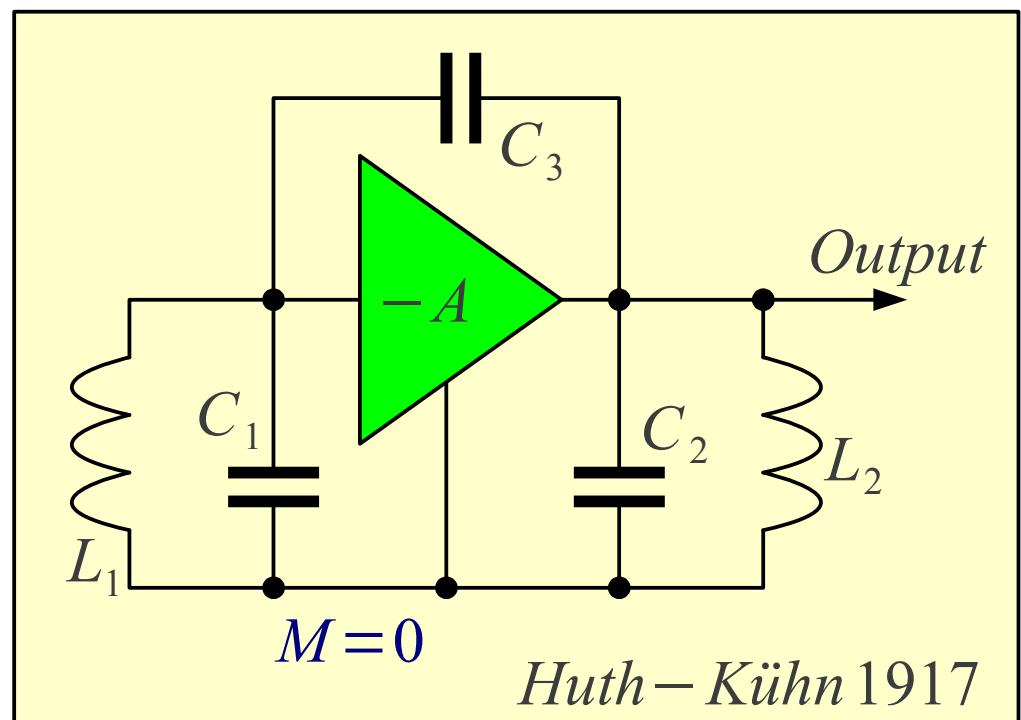

Huth-Kühn 1917



$$|A \cdot H(\omega_0)| = 1$$
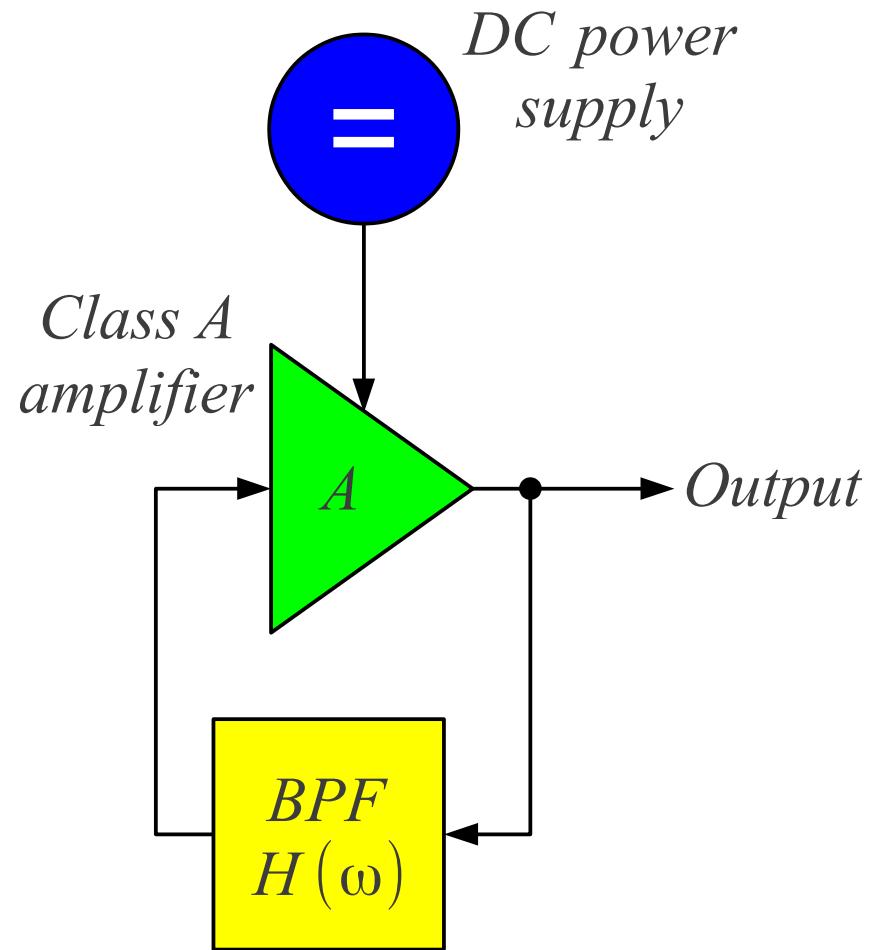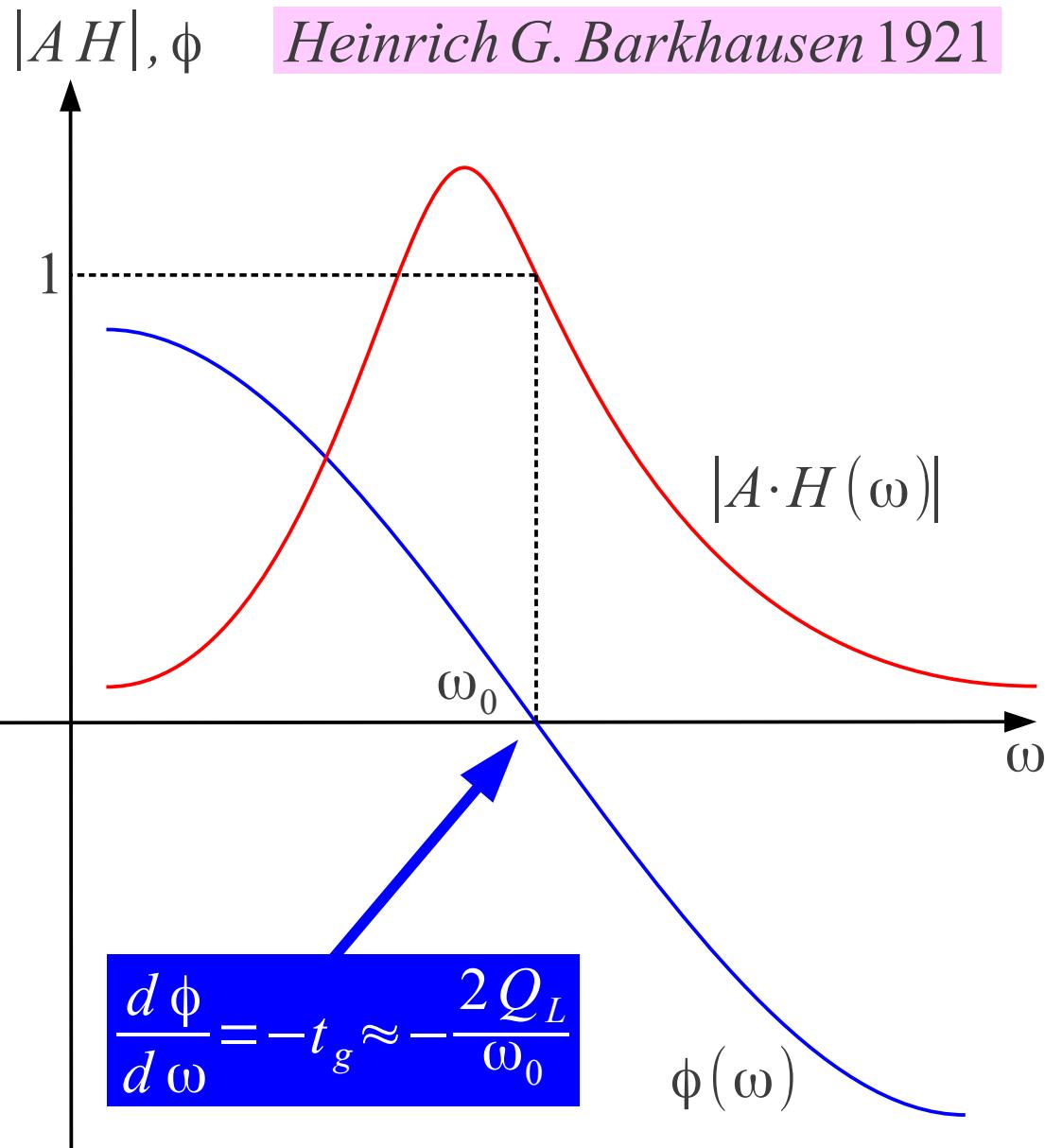
$$\phi(\omega_0) = m \cdot 2\pi \quad m = 0, 1, 2, 3 \dots$$





$$A \cdot H(\omega) = |A \cdot H(\omega)| \cdot e^{j\phi(\omega)}$$

Barkhausen criterion

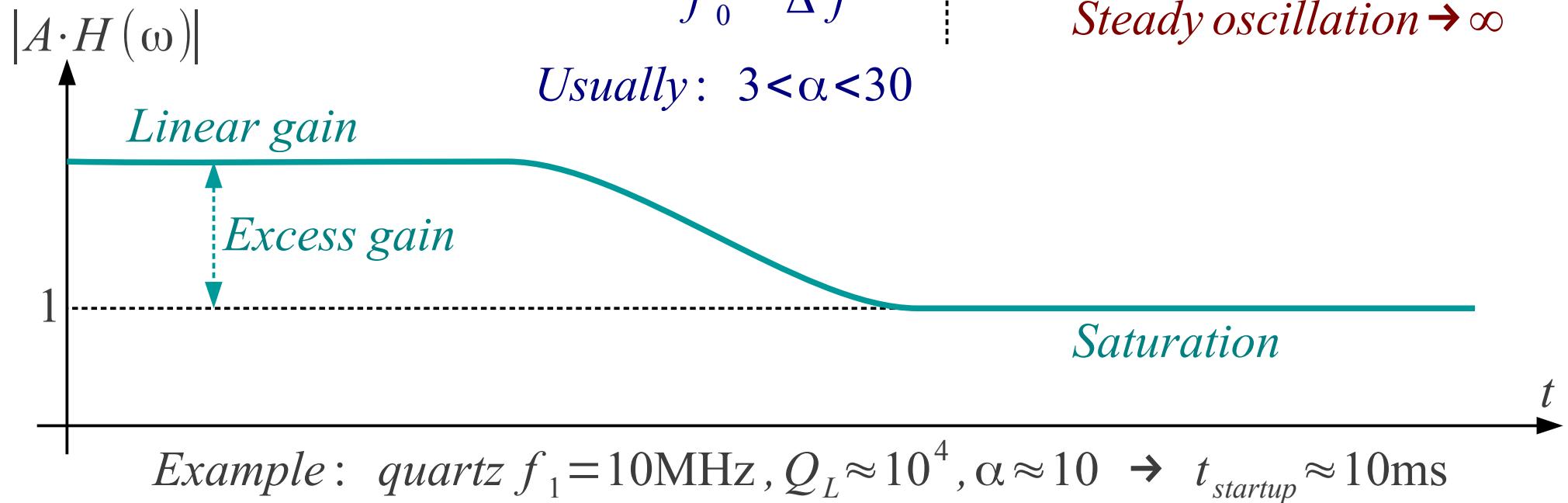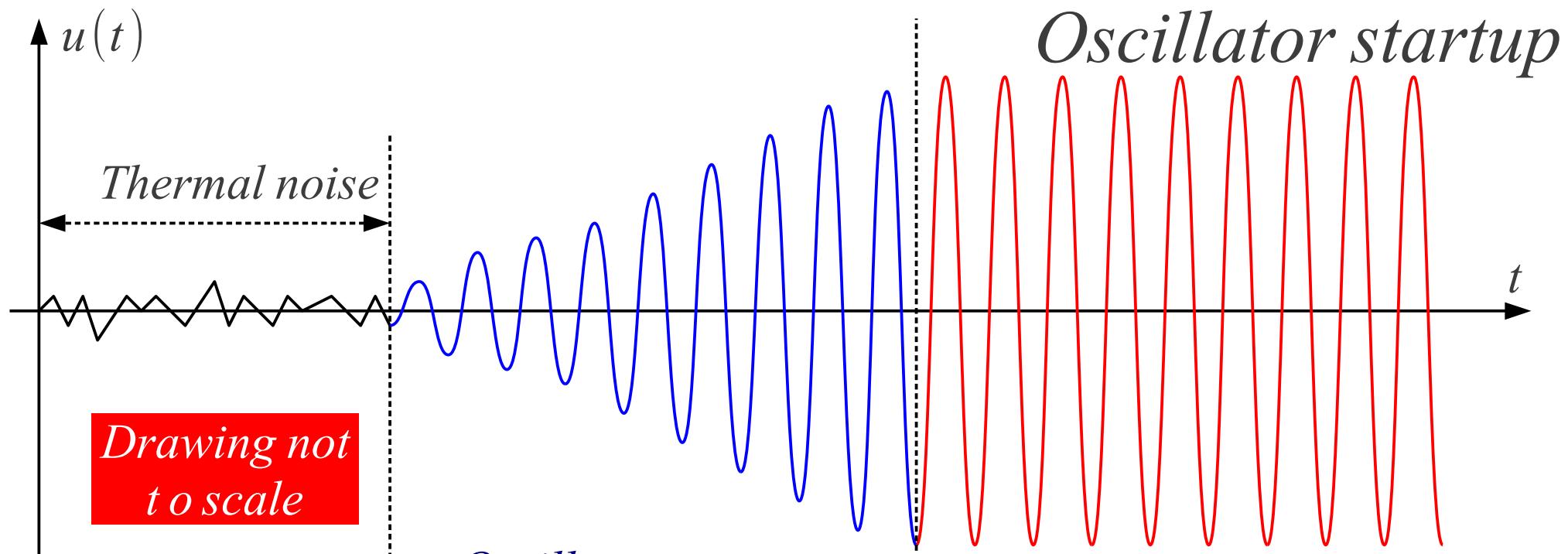


Edwin Armstrong 1922

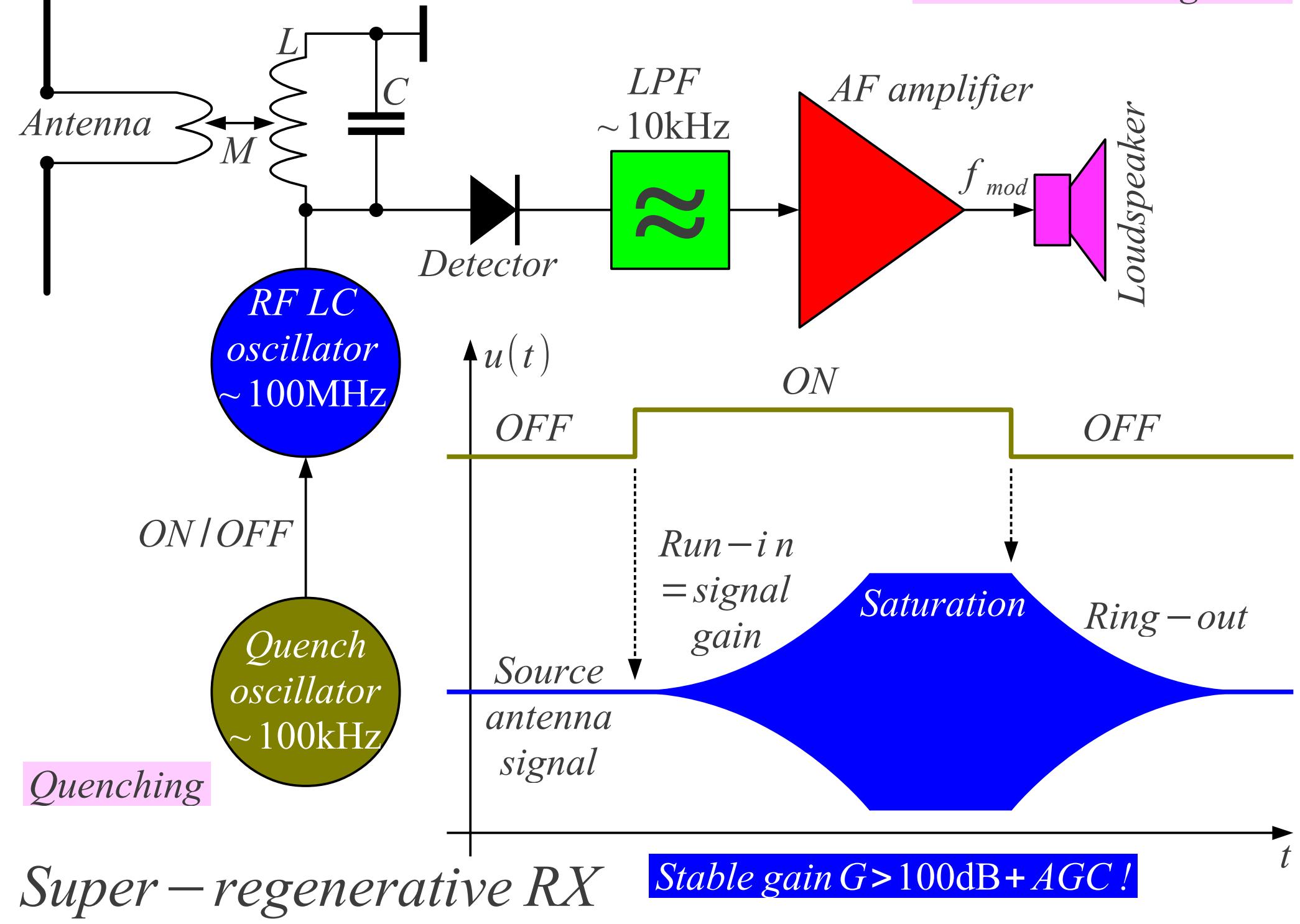

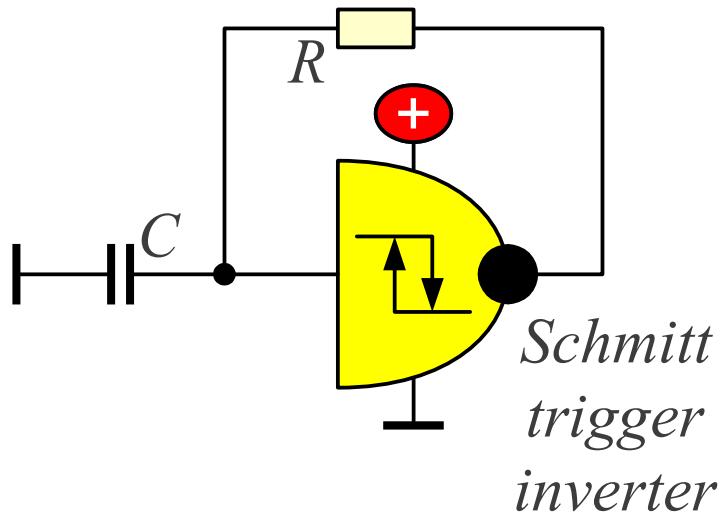


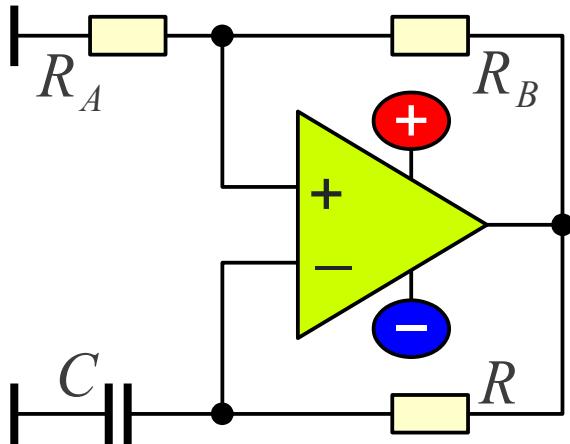
*Astable circuit
oscillates immediately!*



*Circuits with hysteresis
are slow and noisy!*


Different oscillators

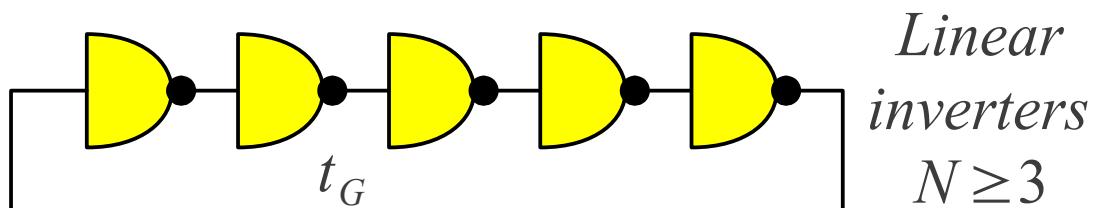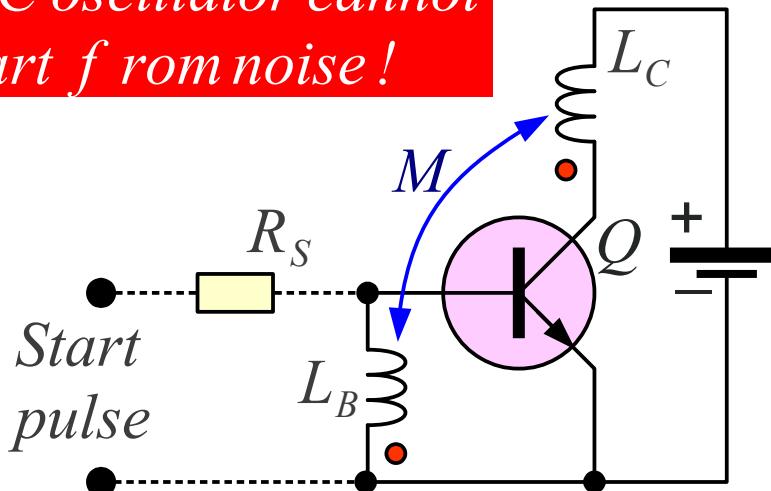
*Class C oscillator cannot
start from noise!*



Any odd number of gates always oscillates!

*Start
from
noise
 $Q_L \approx 1$*

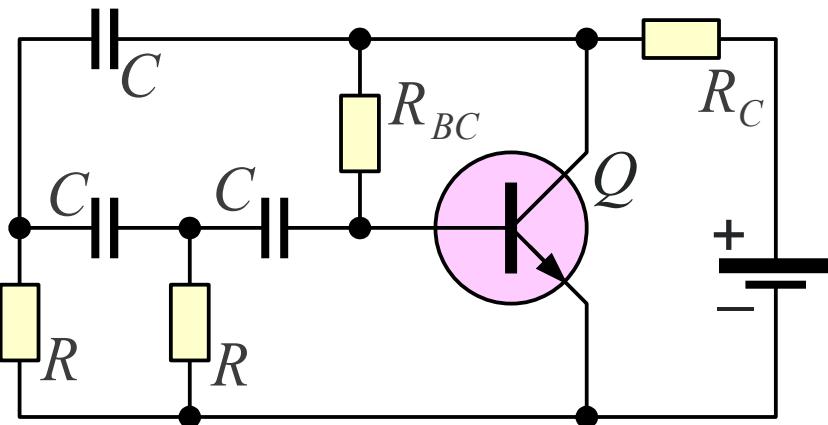

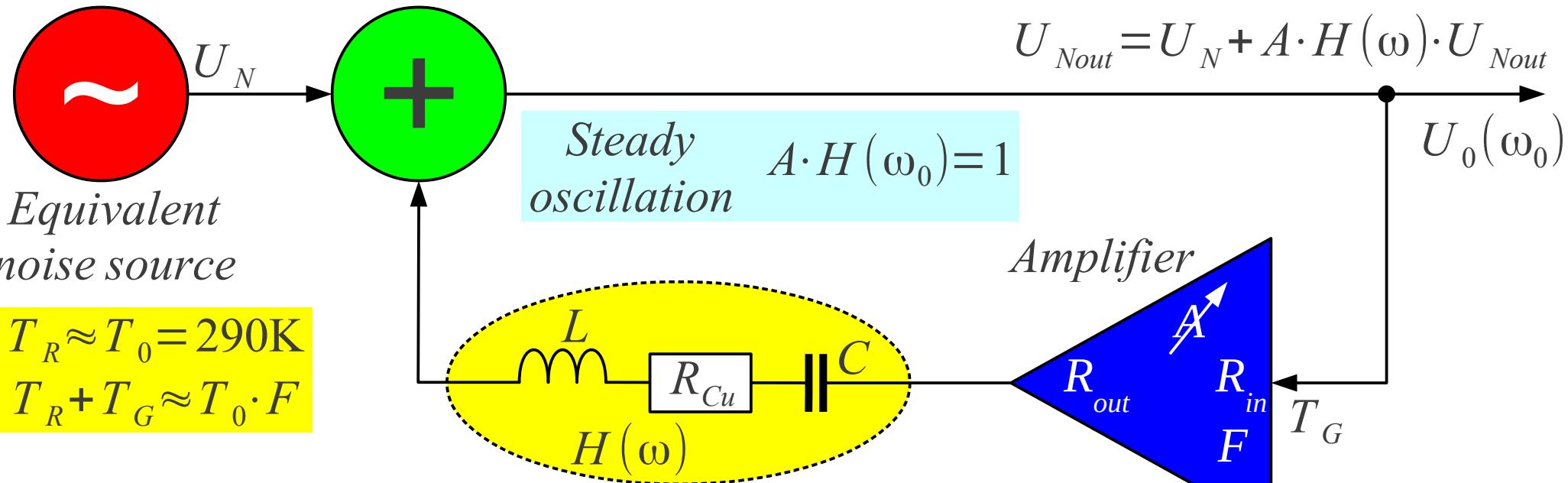

$$H(\omega) = \frac{R_{in}}{\Sigma R + j\omega L + \frac{1}{j\omega C}}$$

Resonator T_R

$$\Sigma R = R_{out} + R_{Cu} + R_{in}$$

$$\Delta\omega = \omega - \omega_0$$

$$A \cdot H(\omega) = \frac{\Sigma R}{\Sigma R + j\omega L + \frac{1}{j\omega C}} \approx \frac{1}{1 + j2Q_L \frac{\Delta\omega}{\omega_0}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Oscillator noise

$$Q_L = \frac{\omega_0 L}{\Sigma R}$$

$$U_{Nout} = \frac{U_N}{1 - A \cdot H(\omega)}$$

$$U_{Nout} \approx \frac{U_N}{1 - \frac{1}{1 + j2Q_L \frac{\Delta\omega}{\omega_0}}} = U_N \cdot \left(1 + \frac{\omega_0}{j2Q_L \Delta\omega}\right)$$

Valid @
 $U_{Nout} \ll U_0$

$$U_{Nout} \approx U_N \cdot \left(1 + \frac{\omega_0}{j 2 Q_L \Delta \omega} \right)$$

$$P = \alpha |U|^2 \quad |a \pm j b|^2 = a^2 + b^2$$

$$P_{Nout} \approx P_N \cdot \left[1 + \left(\frac{\omega_0}{2 Q_L \Delta \omega} \right)^2 \right]$$

$$\omega = 2\pi f \rightarrow \Delta f = f - f_0$$


$$P_{Nout} \approx P_N \cdot \left[1 + \left(\frac{f_0}{2 Q_L \Delta f} \right)^2 \right]$$

P_{Nout} \equiv total noise power

P_A \equiv amplitude - noise power

P_ϕ \equiv phase - noise power

Amplitude and phase noise

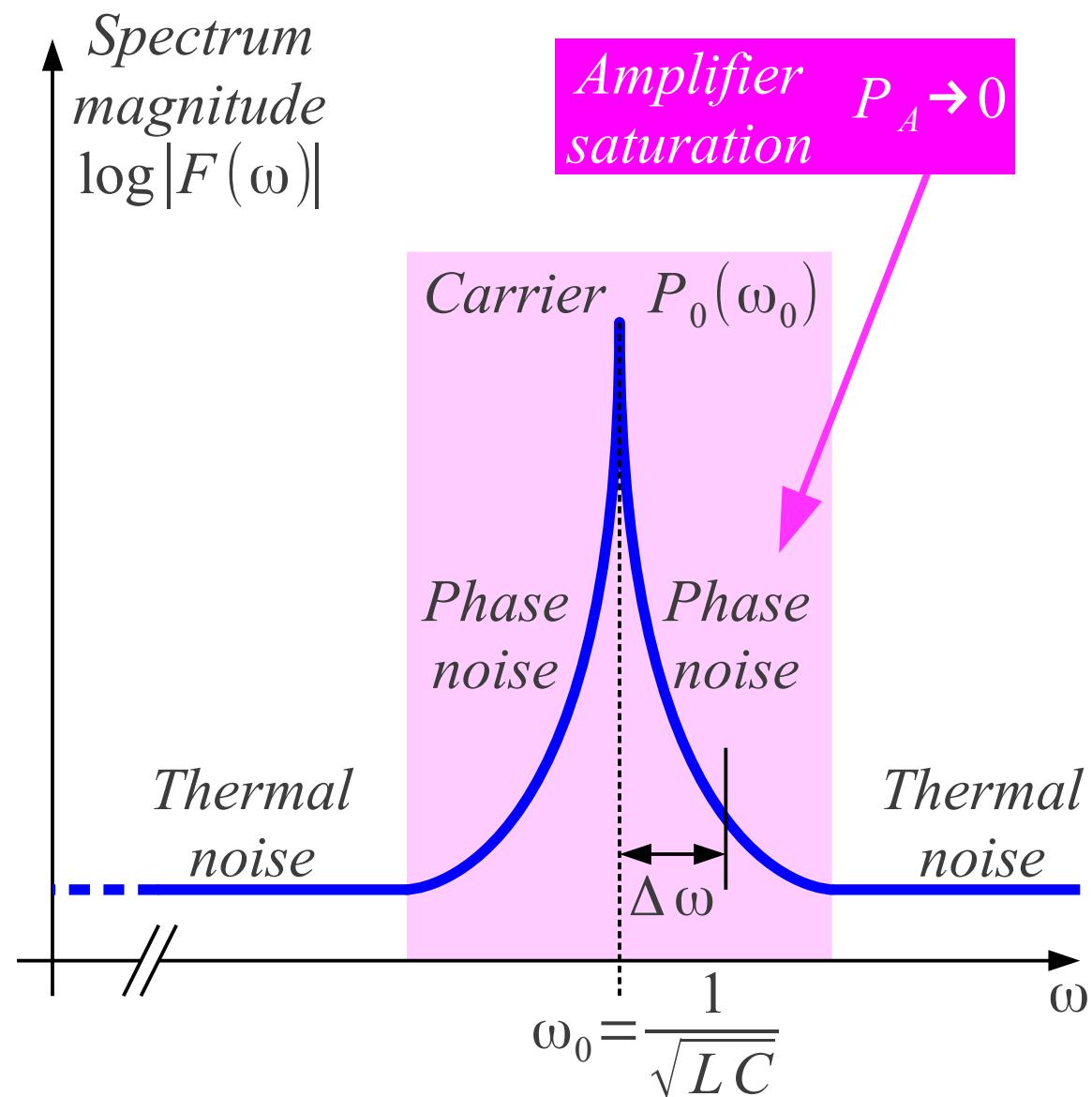

$$P_\phi = P_A = \frac{P_{Nout}}{2} \approx \frac{1}{2} \left[1 + \left(\frac{f_0}{2 Q_L \Delta f} \right)^2 \right] \cdot P_N$$

Relative phase-noise density

$$L(\Delta f) = \frac{1}{P_0} \cdot \frac{d P_\phi}{d f} \quad [\text{Hz}^{-1}]$$

$$\frac{d P_N}{d f} = N_0 = k_B \cdot (T_R + T_G) \approx k_B T_0 F$$


David B. Leeson 1966

Valid @
 $L(\Delta f) \cdot \Delta f \ll 1$

$$L(\Delta f) = \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0}$$

$$\log L(\Delta f)_{\text{dBc/Hz}} = 10 \log_{10} [L(\Delta f) \cdot 1 \text{Hz}]$$

Leeson's equation

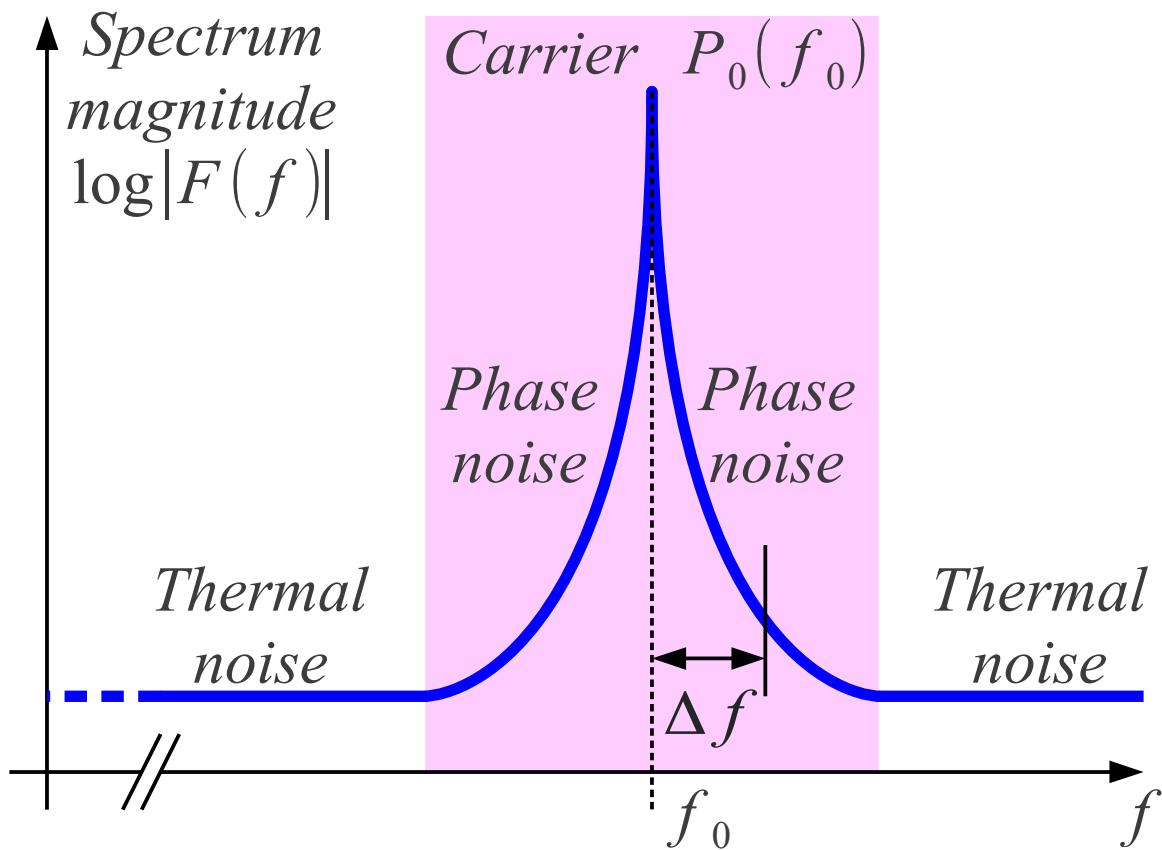

$Q_L \equiv$ resonator loaded Q


$k_B \approx 1.38 \cdot 10^{-23} \text{ J/K} \equiv$ Boltzmann constant

$T_0 \approx 290 \text{ K} \equiv$ circuit temperature


$F \equiv$ amplifier noise figure @ P_0

$P_0 \equiv$ carrier power @ f_0
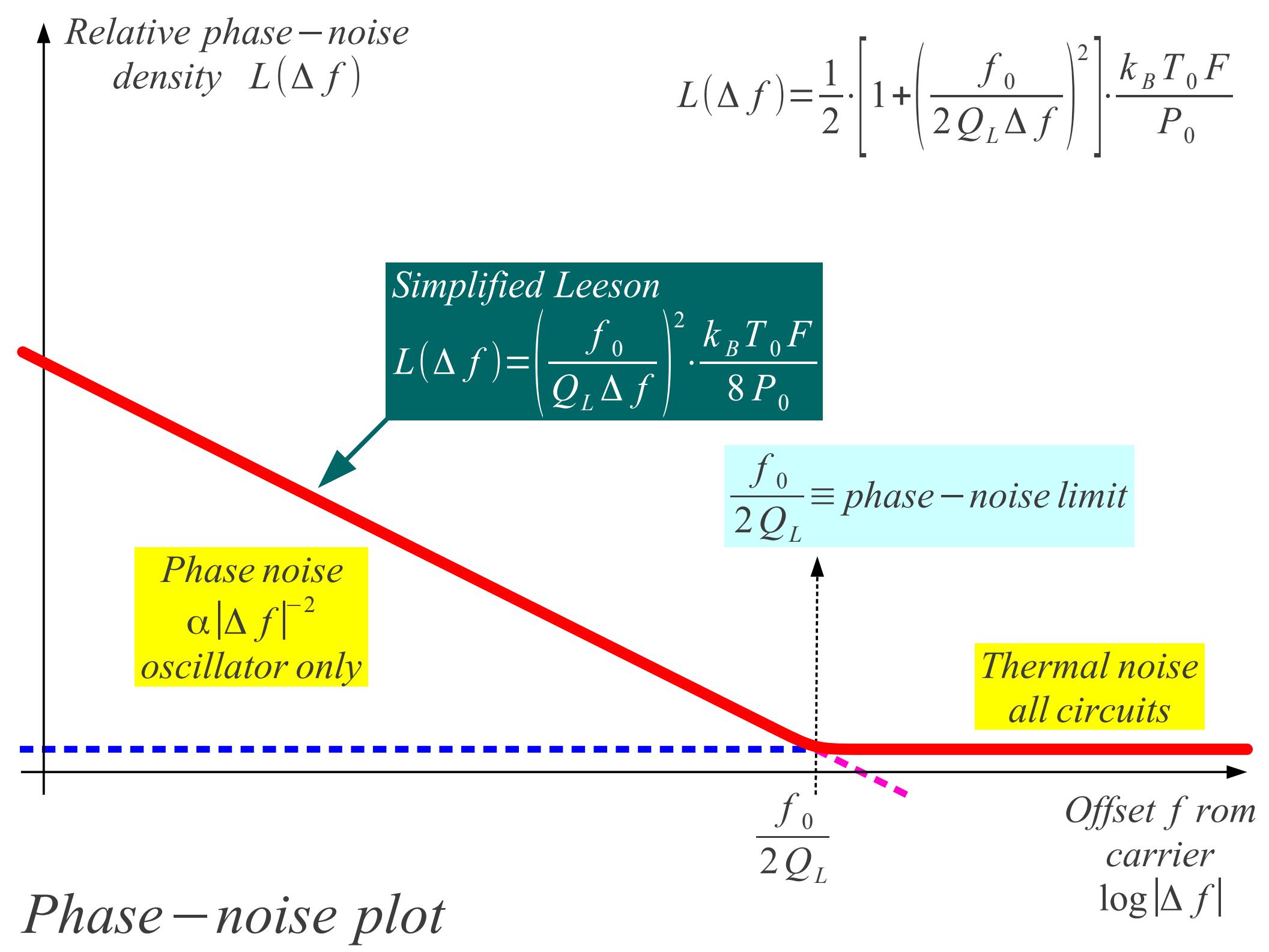
$$\log L(\Delta f)_{\text{dBc/Hz}} = 10 \log_{10} \left\{ \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0} \cdot 1 \text{Hz} \right\}$$



QPSK example

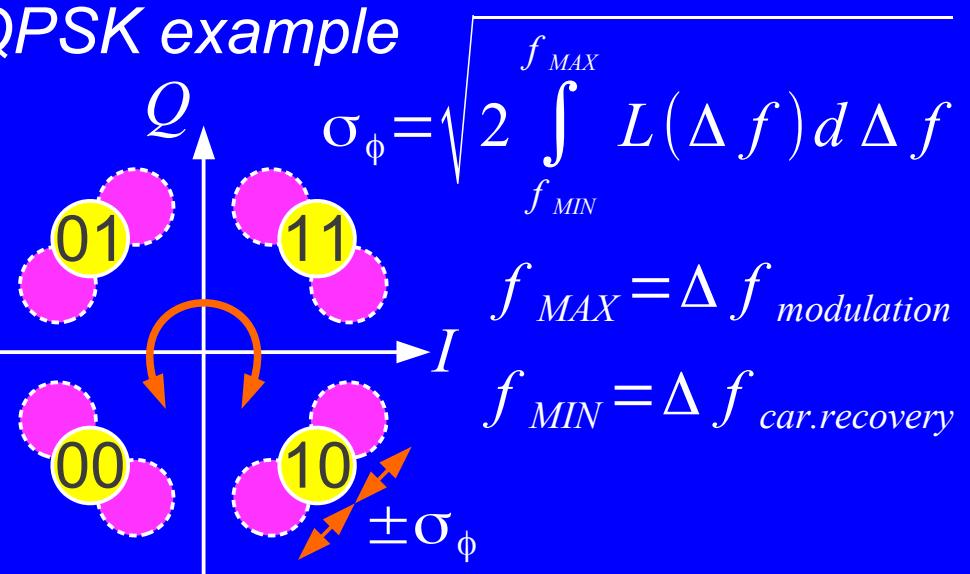

Constellation rotation

Spectrum

$$\log|F(f)|$$

$$\sigma_f = \sqrt{2 \int_{f_{MIN}}^{f_{MAX}} \Delta f^2 L(\Delta f) d\Delta f}$$

deviation = $\pm \sigma_f$

Usual choice

$$f_{MAX} = 3\text{kHz}$$

$$f_{MIN} = 50\text{Hz}$$

$$(S/N)_{voice}$$

Residual FM

Spectrum

$$\log|F(f)| \quad P_i = P_0 \cdot \int_{\Delta f_1}^{\Delta f_2} L(\Delta f) d\Delta f$$

$$P_0$$

$$f_0$$

$$\Delta f_2$$

$$\Delta f_1$$

$$\Delta f_2$$

Adjacent-channel interference

$$u(t)$$


$$\sigma_t = \frac{1}{2\pi f_0} \cdot \sqrt{2 \int_{f_{MIN}}^{f_{MAX}} L(\Delta f) d\Delta f}$$

$$f_{MAX} \leq f_{clock}$$

$$f_{MIN} = \Delta f_{clock.recovery}$$

Clock jitter

Phase – noise consequences

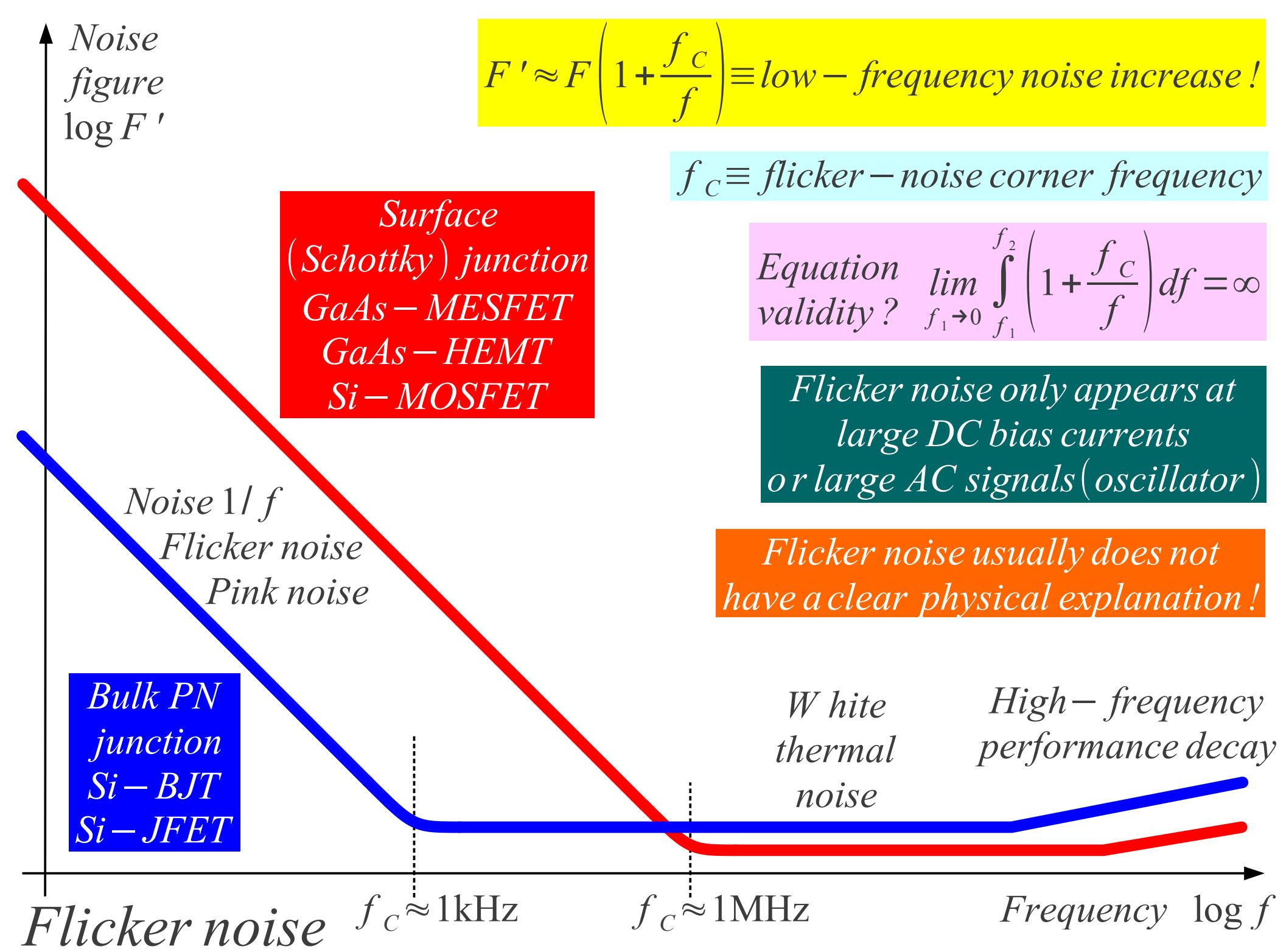

Including noise $1/f$


$$F' = F \cdot \left(1 + \frac{f_C}{|\Delta f|} \right)$$

$$\frac{d P_N}{d f} \approx k_B \cdot T_0 \cdot F'$$

$$\frac{d P_N}{d f} \approx k_B \cdot T_0 \cdot F \cdot \left(1 + \frac{f_C}{|\Delta f|} \right)$$

Leeson with flicker noise

$$L(\Delta f) = \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0} \cdot \left(1 + \frac{f_C}{|\Delta f|} \right)$$

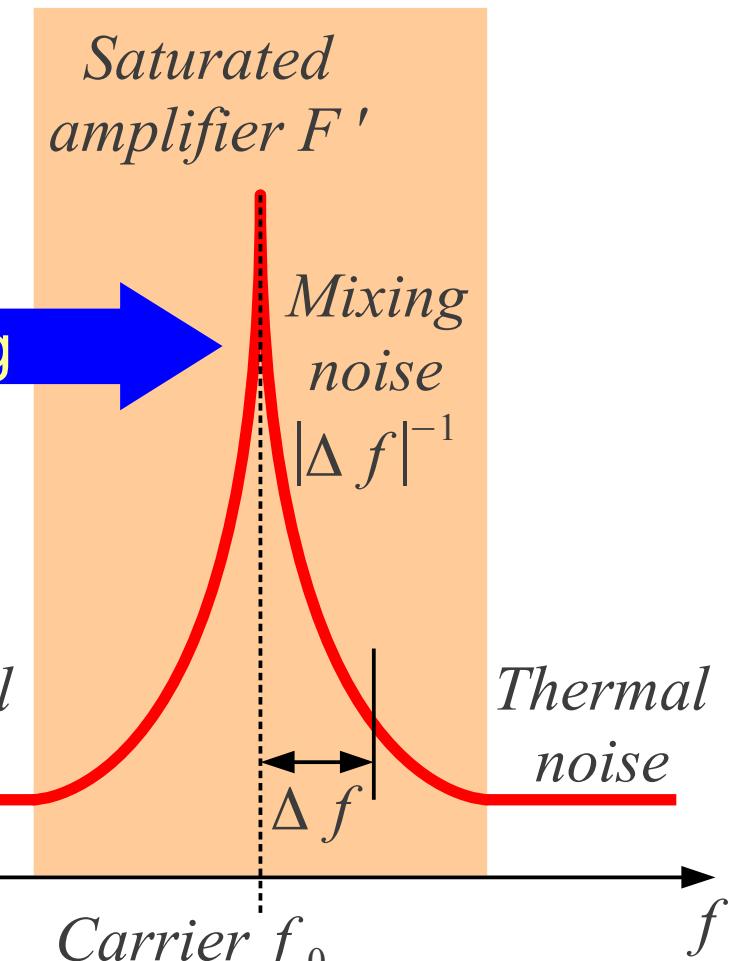

Valid @
 $L(\Delta f) \cdot \Delta f \ll 1$

*Bulk PN junction
Si-BJT
Si-JFET*

$$\log L(\Delta f)_{\text{dBc/Hz}} = 10 \log_{10} \left\{ \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0} \cdot \left(1 + \frac{f_C}{|\Delta f|} \right) \cdot 1 \text{Hz} \right\}$$

Extended oscillator noise

Relative phase-noise density $L(\Delta f)$

$$L(\Delta f) = \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0} \cdot \left(1 + \frac{f_C}{|\Delta f|} \right)$$

$f_C \equiv$ flicker-noise corner frequency

$\frac{f_0}{2Q_L} \equiv$ phase-noise limit

Noise $1/f$
 $\alpha |\Delta f|^{-3}$

Phase noise
 $\alpha |\Delta f|^{-2}$

Thermal noise

f_C

$\frac{f_0}{2Q_L}$

Offset f from carrier
 $\log |\Delta f|$


Phase-noise plot including flicker

The loaded-resonator quality Q_L is the most important quantity for phase noise!

$$L(\Delta f) = \frac{1}{2} \cdot \left[1 + \left(\frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0 F}{P_0} \cdot \left(1 + \frac{f_C}{|\Delta f|} \right)$$


Variable-frequency oscillators	Q_L
<i>RC VCO</i>	~ 1
<i>BWO tube</i>	~ 1
<i>LC varactor VCO</i>	$10 \leftrightarrow 30$
<i>YIG ($Y_3Fe_5O_{12}$) oscillator</i>	$300 \leftrightarrow 1000$

Fixed-frequency oscillators	Q_L
<i>RC oscillator</i>	~ 1
<i>LC tuned circuit</i>	$30 \leftrightarrow 100$
<i>Cavity resonator</i>	$1000 \leftrightarrow 3000$
<i>Ceramic dielectric resonator</i>	$1000 \leftrightarrow 3000$
<i>AT-cut quartz crystal (fundamental)</i>	$3000 \leftrightarrow 10000$
<i>AT-cut quartz crystal (3rd/5th overtone)</i>	$10000 \leftrightarrow 30000$
<i>Electro-optical delay line (\$)</i>	$\sim 10^5$
<i>Sapphire dielectric resonator (\$\$\$)</i>	$\sim 3 \cdot 10^5$
<i>Red HeNe LASER</i>	$\sim 10^8$

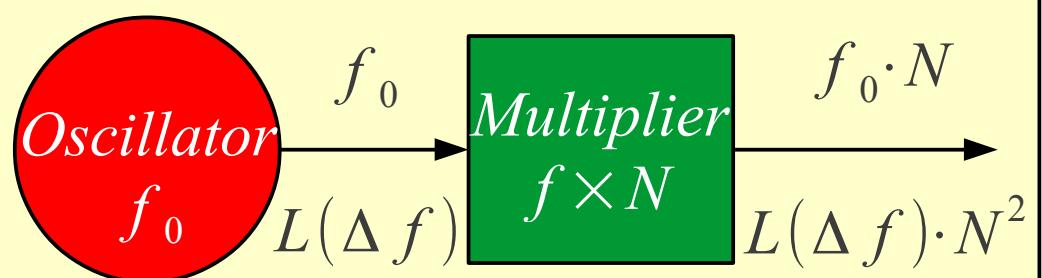

Phase-noise power multiplies with the square of the frequency!
The role of Q_L stays unchanged!

Loaded – resonator quality

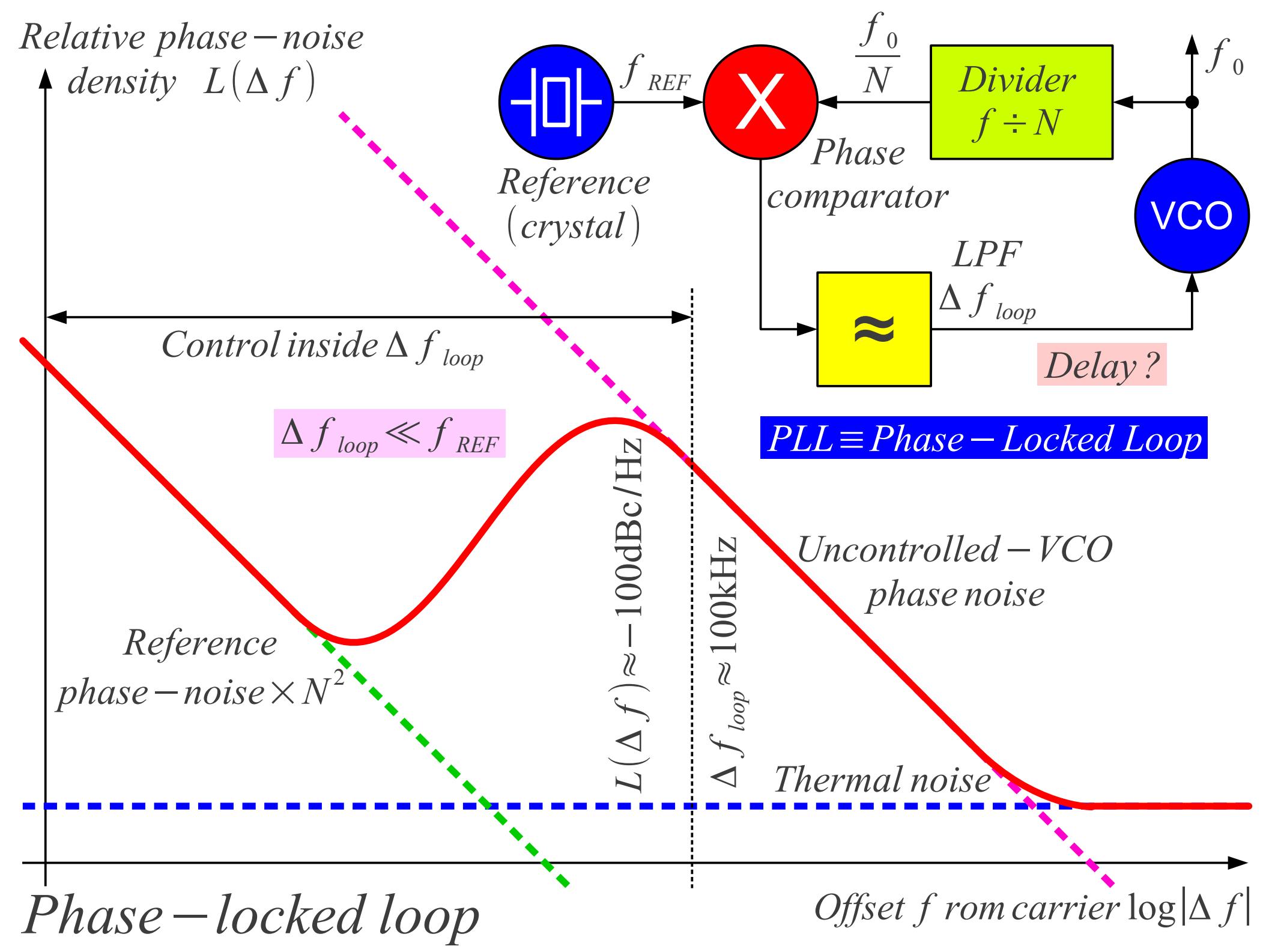

$$\begin{array}{l} \text{Oscillator} \\ \text{with noise} \end{array} \quad A \cdot H(\omega_0) = 1 - \epsilon \quad 0 < \epsilon \ll 1$$

$$A \cdot H(\omega) \approx \frac{1 - \epsilon}{1 + j 2 Q_L \frac{\Delta \omega}{\omega_0}}$$

$$U_{Nout} = \frac{U_N}{1 - A \cdot H(\omega)} \approx \frac{U_N}{1 - \frac{1 - \epsilon}{1 + j 2 Q_L \frac{\Delta \omega}{\omega_0}}} = U_N \frac{1 + j 2 Q_L \frac{\Delta \omega}{\omega_0}}{j 2 Q_L \frac{\Delta \omega}{\omega_0} - \epsilon}$$

$$\frac{d P_N}{d f} \approx k_B T_0 F$$


$$\underset{\omega_0}{Near} \rightarrow \left| 2 Q_L \frac{\Delta \omega}{\omega_0} \right| \ll 1 \rightarrow U_{Nout} \approx \frac{U_N}{j 2 Q_L \frac{\Delta \omega}{\omega_0} - \epsilon} \rightarrow P_{Nout} \approx \frac{P_N}{\epsilon^2 + \left(2 Q_L \frac{\Delta \omega}{\omega_0} \right)^2}$$

$$P_\phi = \frac{P_{Nout}}{2} \approx \frac{P_N / 2}{\epsilon^2 + \left(2 Q_L \frac{\Delta f}{f_0} \right)^2} = \frac{P_N f_0^2}{8 Q_L^2} \cdot \frac{1}{\left(\frac{\epsilon f_0}{2 Q_L} \right)^2 + \Delta f^2}$$

$$\begin{array}{l} \text{Half width} \\ f_{HW} = \frac{\epsilon f_0}{2 Q_L} \end{array}$$

$$L(\Delta f) = \left(\frac{f_0}{Q_L} \right)^2 \cdot \frac{1}{f_{HW}^2 + \Delta f^2} \cdot \frac{k_B T_0 F}{8 P_0} = \frac{C}{f_{HW}^2 + \Delta f^2} \equiv \text{Lorentz spectral line}$$

Derivation of the Lorentz spectral line

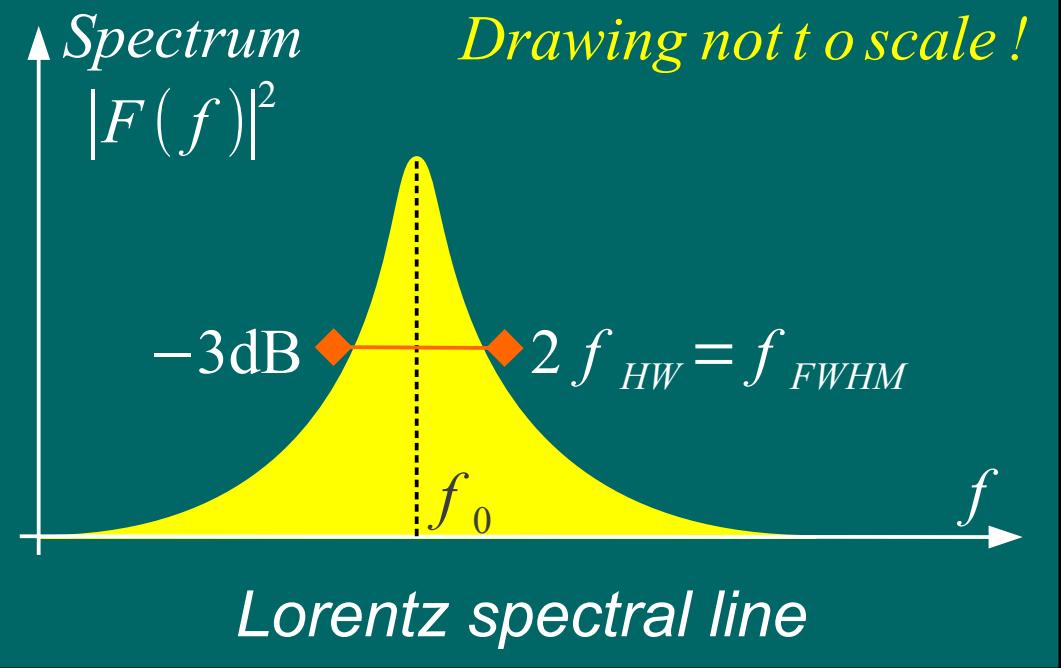

$$L(\Delta f) = \left(\frac{f_0}{Q_L} \right)^2 \cdot \frac{1}{f_{HW}^2 + \Delta f^2} \cdot \frac{k_B T_0 F}{8 P_0}$$

$$f_{HW} \equiv f_{HALF-WIDTH}$$

$$f_{FWHM} \equiv f_{FULL-WIDTH-HALF-MAXIMUM}$$

$$L(\Delta f) = \frac{C}{f_{HW}^2 + \Delta f^2} \quad \epsilon = \frac{2 Q_L f_{HW}}{f_0}$$

$$\int_{-f_0}^{\infty} L(\Delta f) d\Delta f = 1 \approx \int_{-\infty}^{\infty} \frac{C}{f_{HW}^2 + \Delta f^2} d\Delta f = \left[\frac{C}{f_{HW}} \cdot \arctan \frac{\Delta f}{f_{HW}} \right]_{\Delta f = -\infty}^{\Delta f = \infty} = \frac{\pi C}{f_{HW}}$$


$$f_{HW} \approx \pi C = \frac{\pi k_B T_0 F}{8 P_0} \cdot \left(\frac{f_0}{Q_L} \right)^2$$


$$C = \frac{k_B T_0 F}{8 P_0} \cdot \left(\frac{f_0}{Q_L} \right)^2 \approx \frac{f_{HW}}{\pi}$$



Lorentz spectral linewidth

Example $f_0 = 3\text{GHz}$
 $Q_L = 10 \quad P_0 = 0.1\text{mW} \quad F = 10\text{dB}$
 $f_{HW} \approx 14\text{Hz} \quad f_{FWHM} \approx 28\text{Hz} \quad \epsilon \approx 10^{-7}$
without flicker noise !

Phase noise without approximations

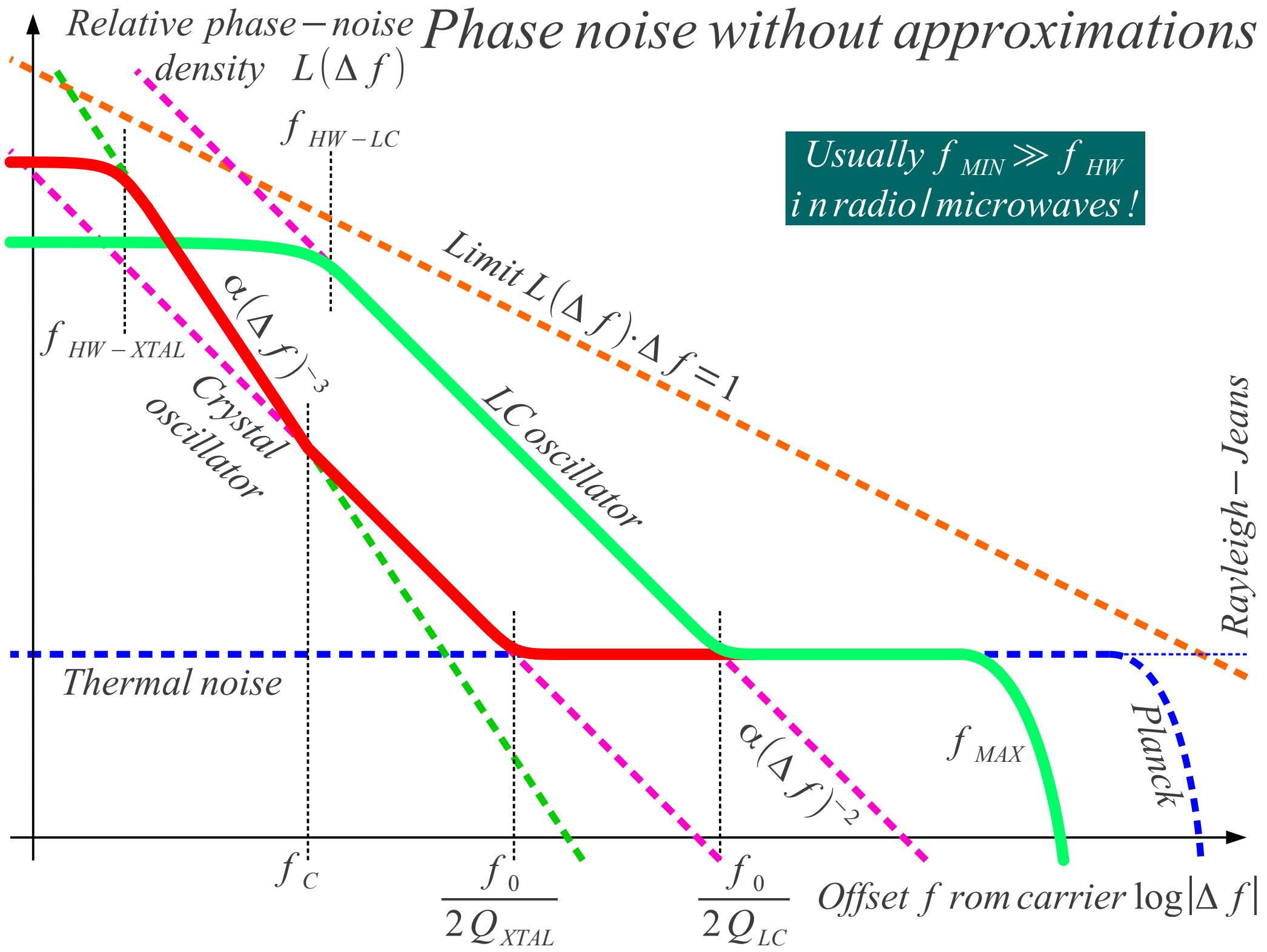

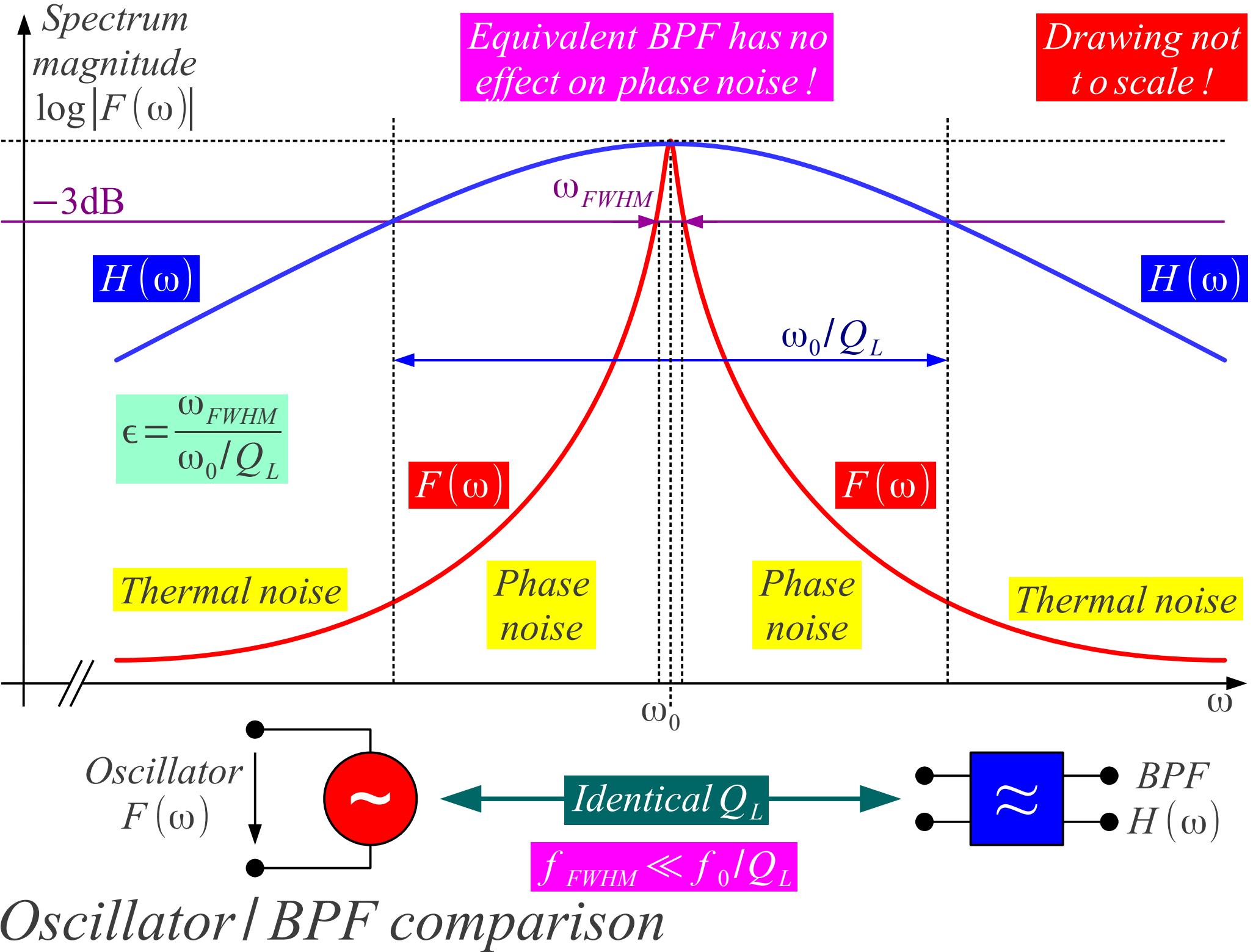

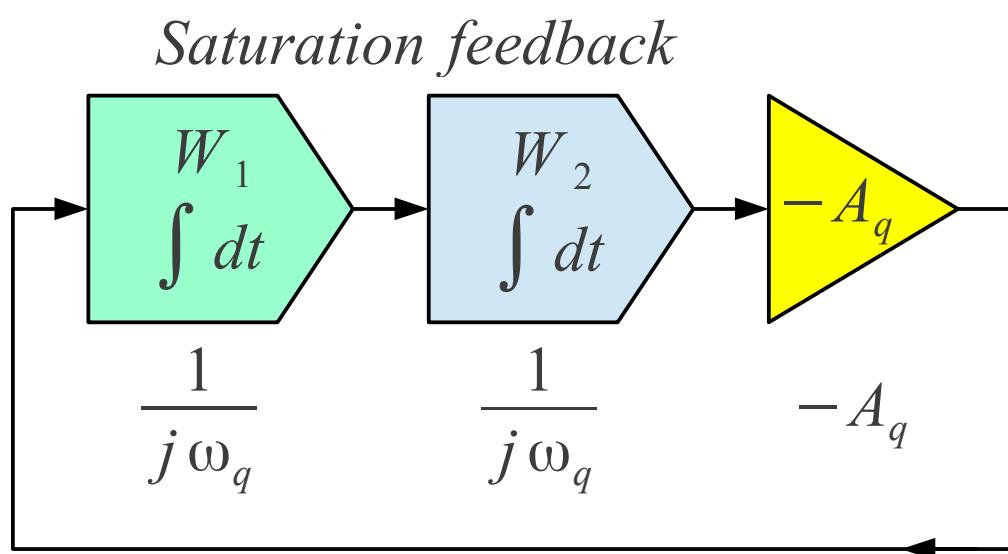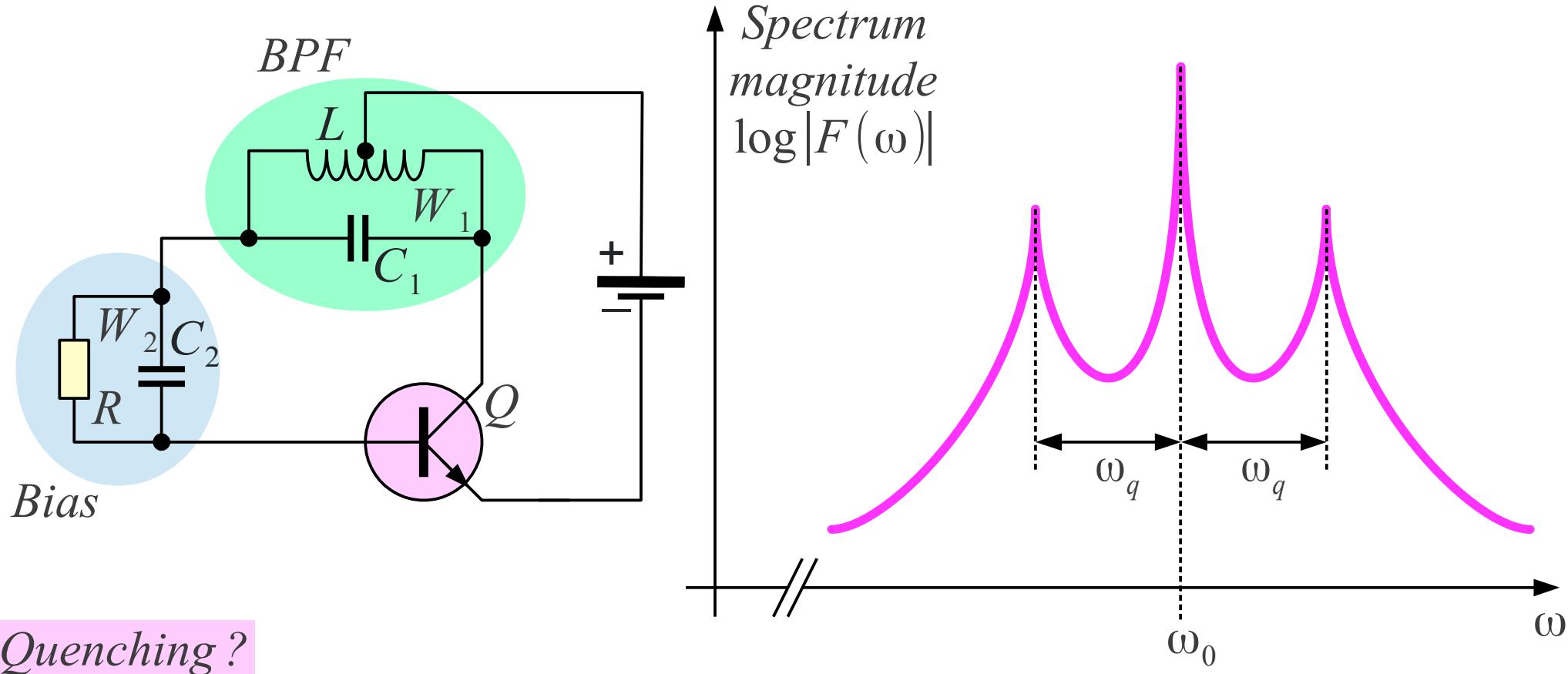


Unsuitable (large) C_2

$$\frac{1}{j\omega_q} \cdot \frac{1}{j\omega_q} \cdot (-A_q) = 1$$



$$\omega_q = \sqrt{A_q}$$

Unstable saturation


Oscillation suppressed

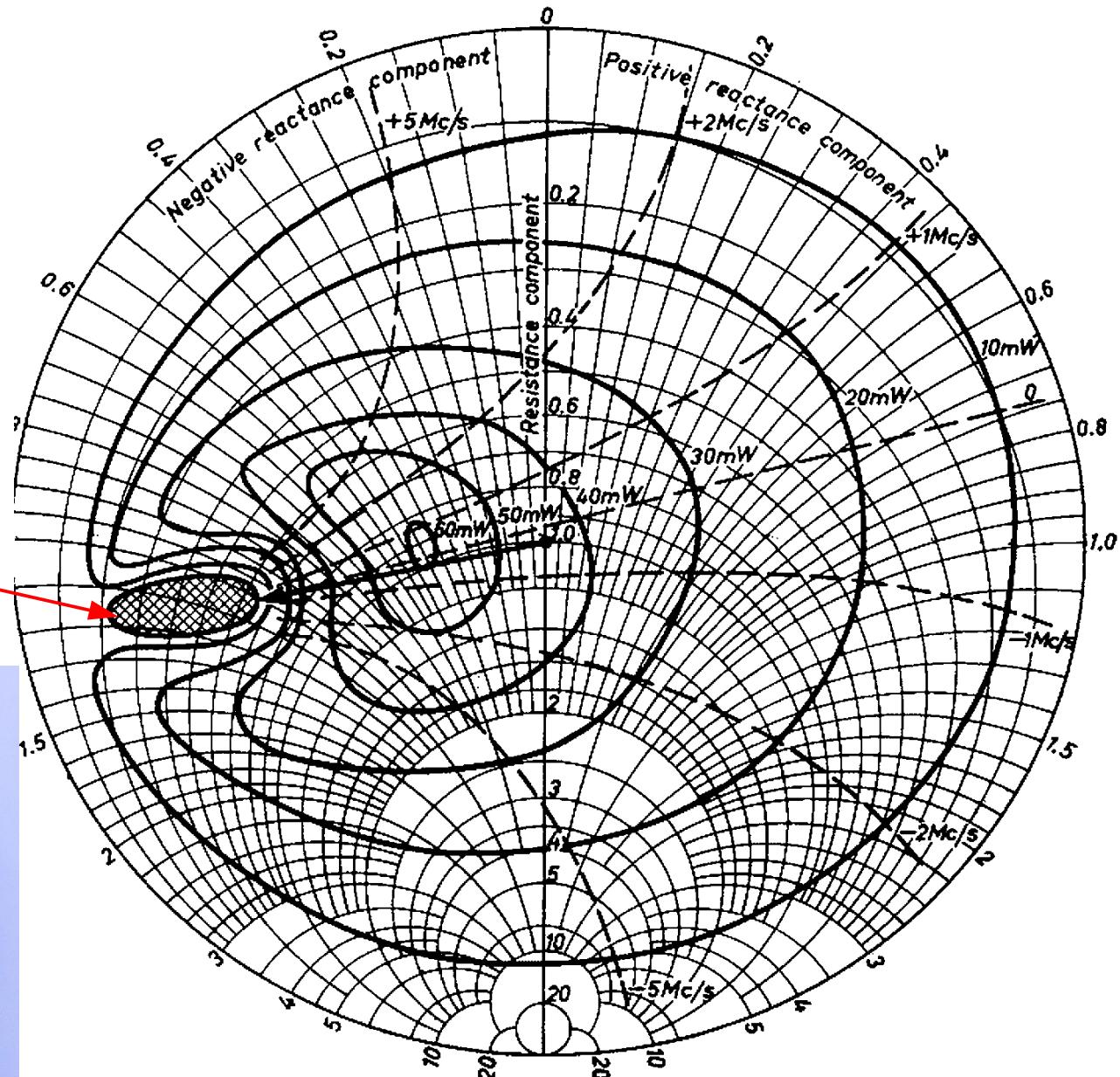

Klystron 2K25 Rieke diagram

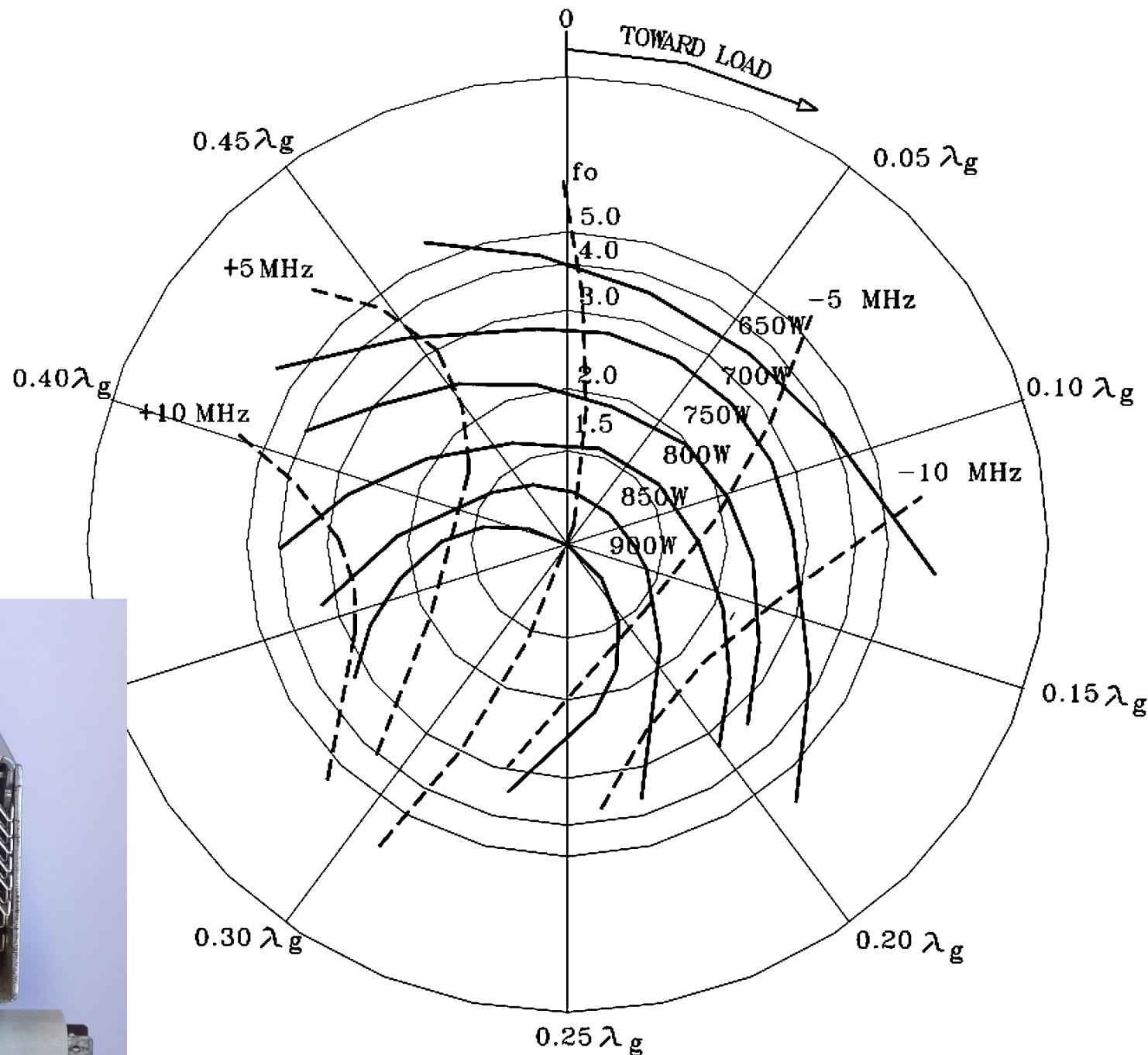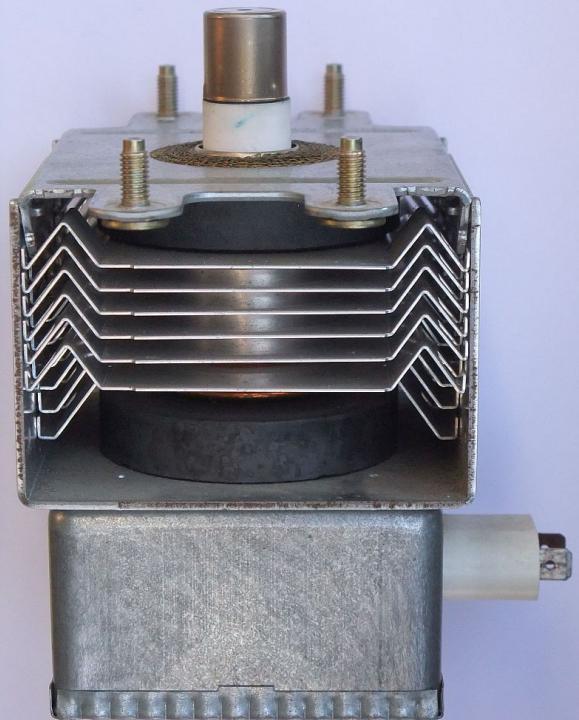

Magnetron 2M214 Rieke diagram

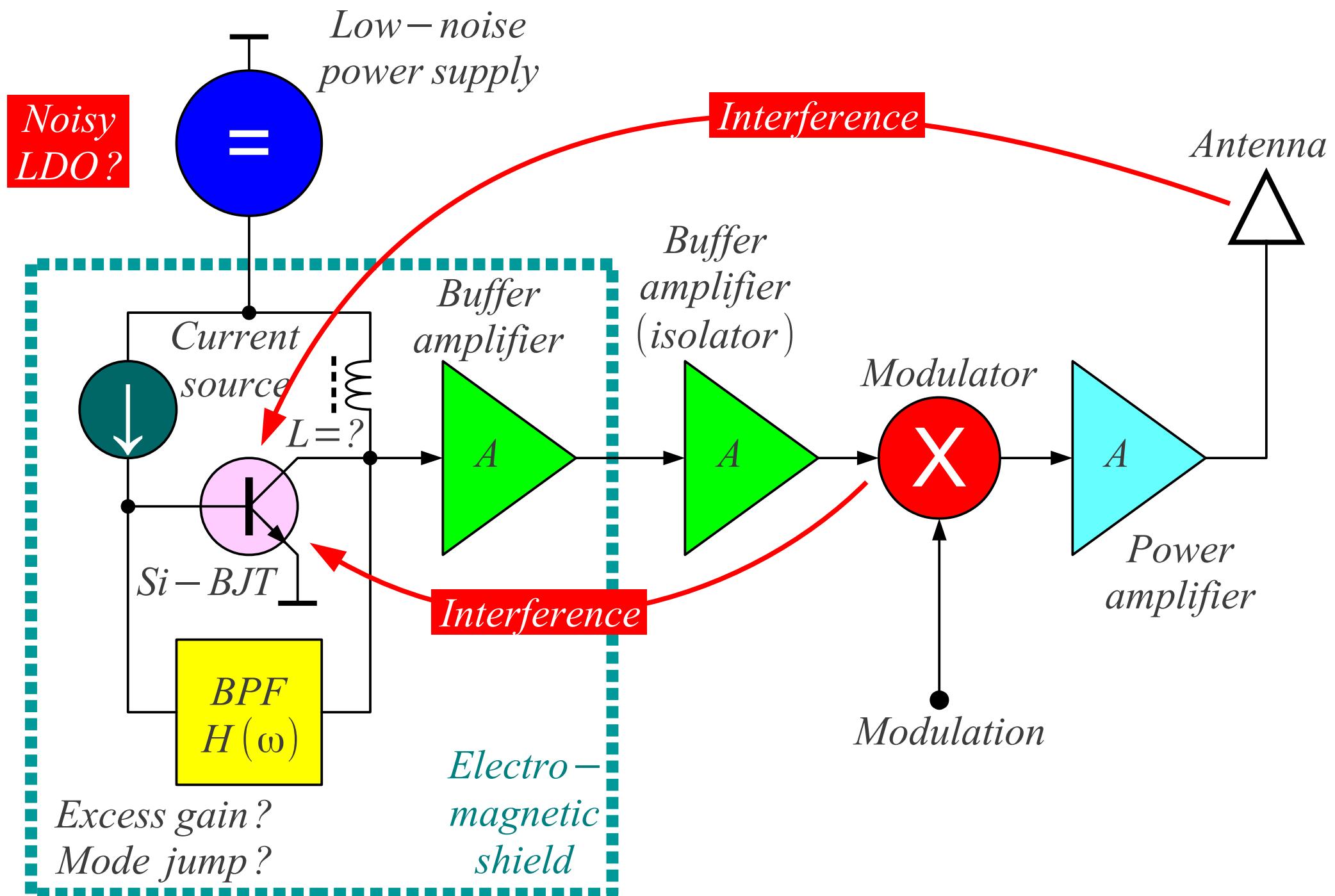

Oscillator design rules