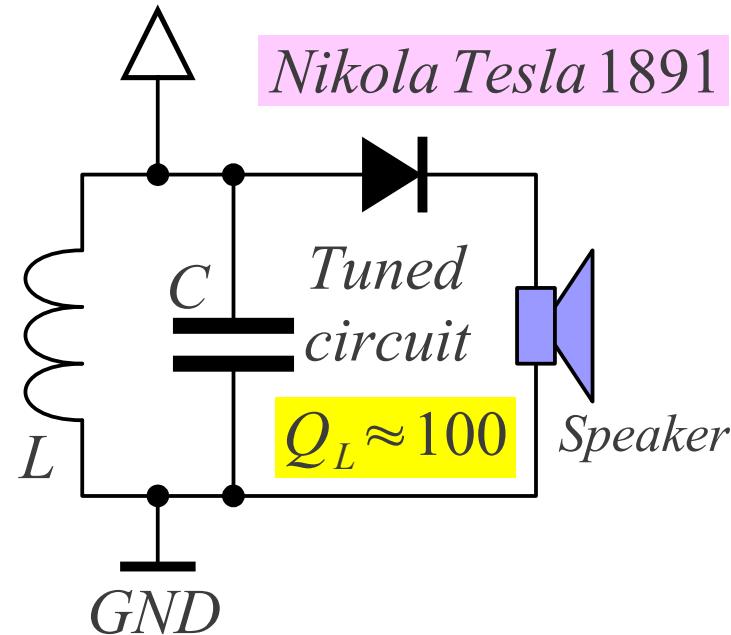


Communication Electronics

Lecture 15:


Frequency synthesizers

*Antenna*




$$B = \frac{f_0}{Q_L}$$


Meissner / Armstrong 1912

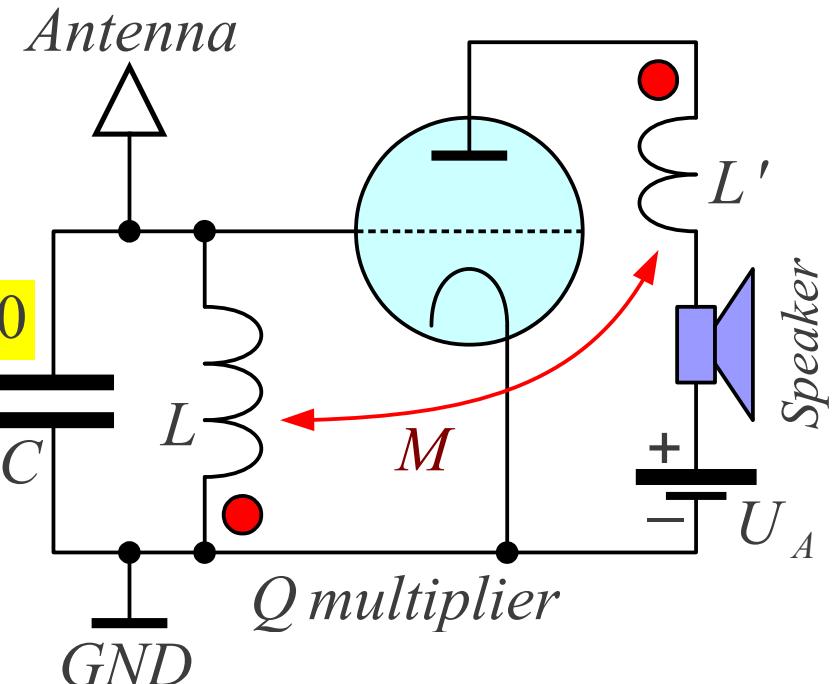

*Antenna*




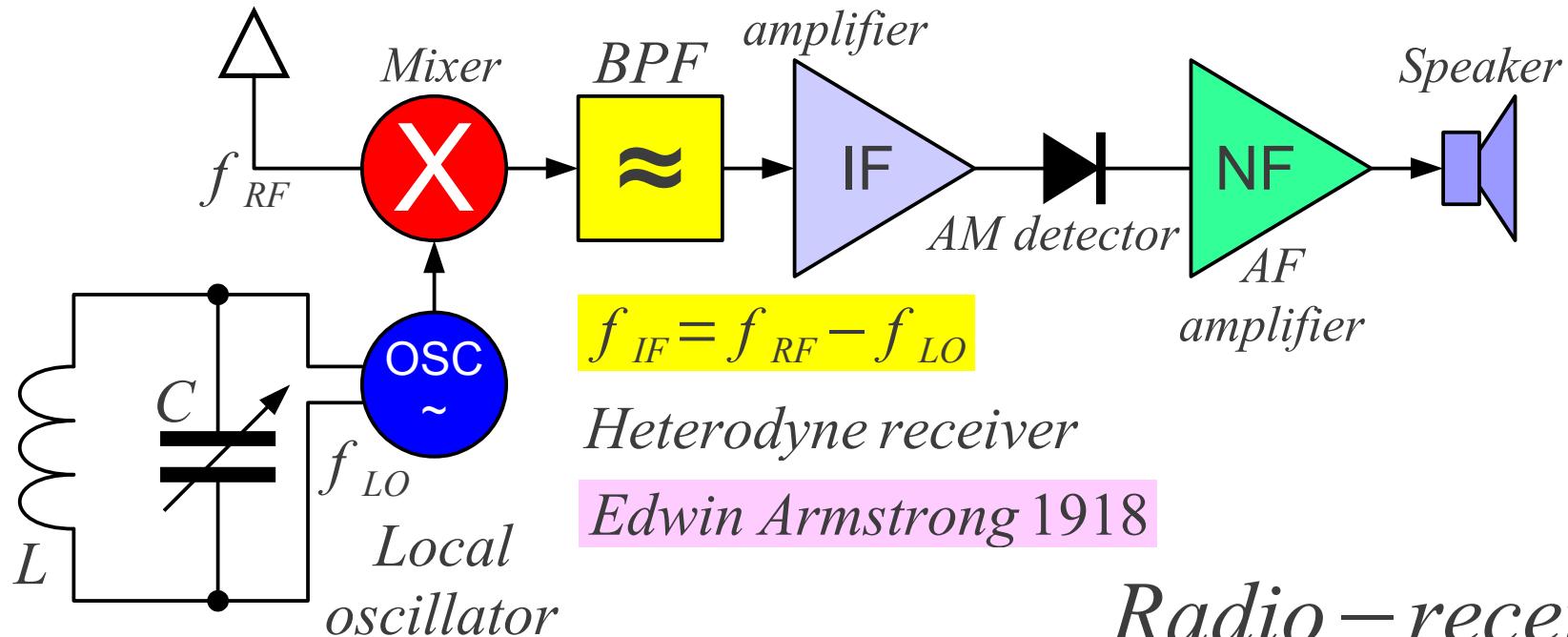


*Radio – receiver tuning*

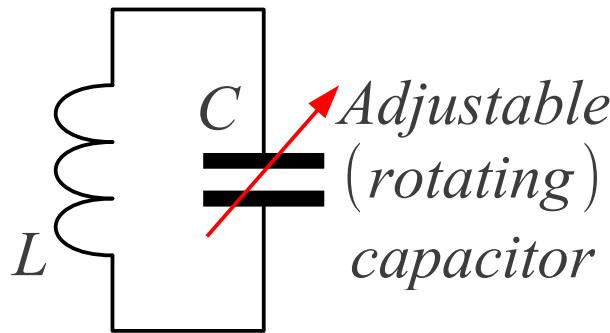

*Adjustable magnetic coupling  
(variometer)*


$$L = L_1 + L_2 \pm 2M$$

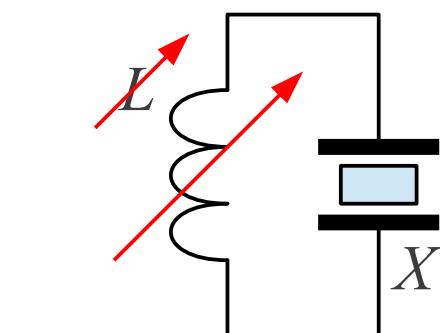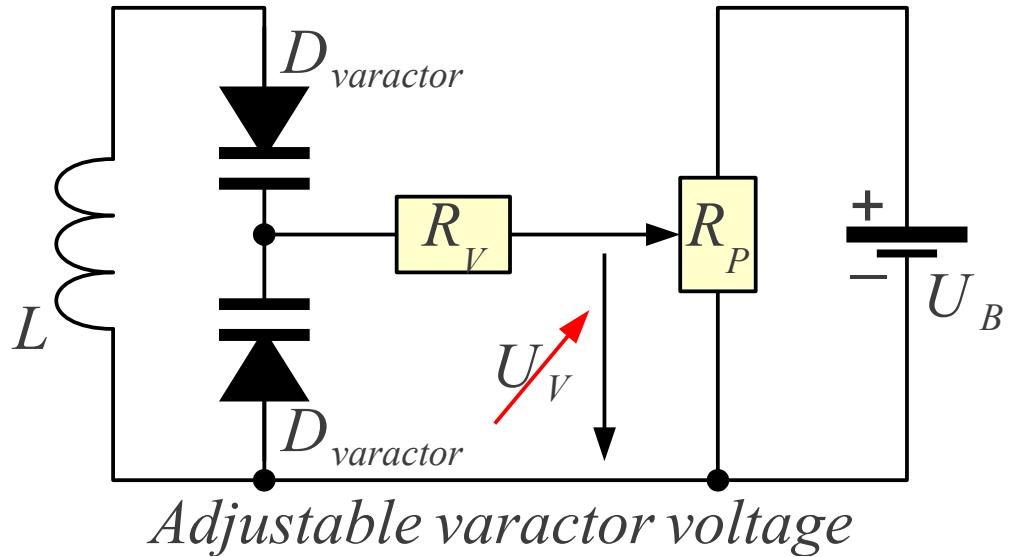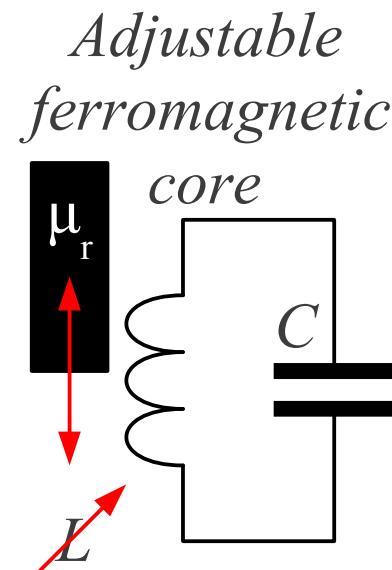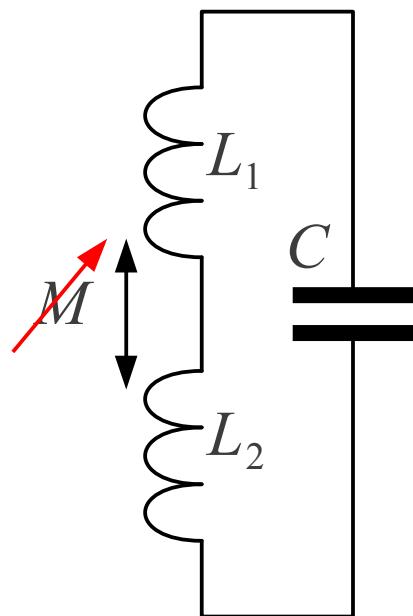



*Quartz-crystal tuning*  
 $\Delta f < 0.1\% f_0$


*Insufficient even for narrowband FM*

*Tuned – circuit frequency adjustment*

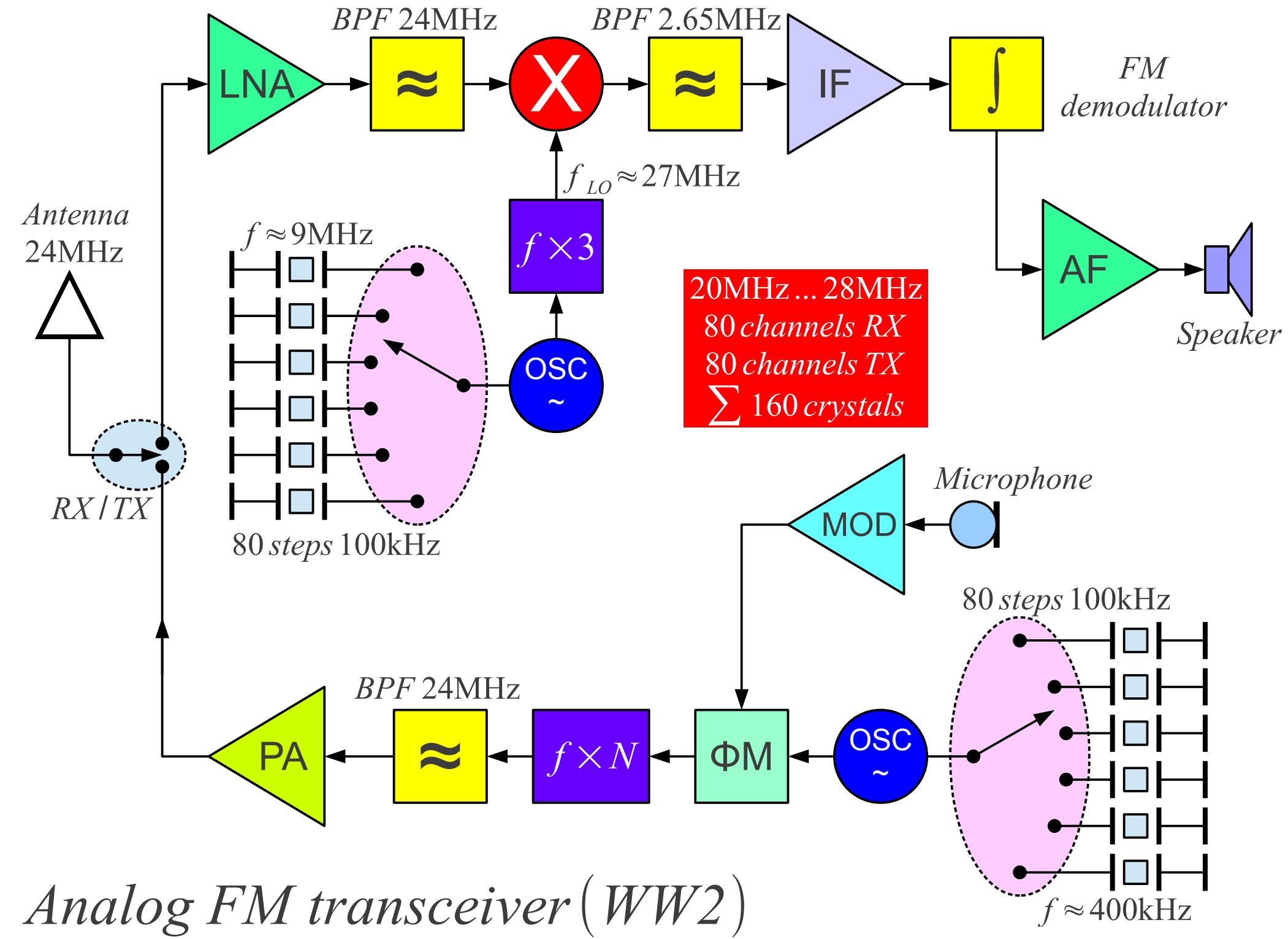

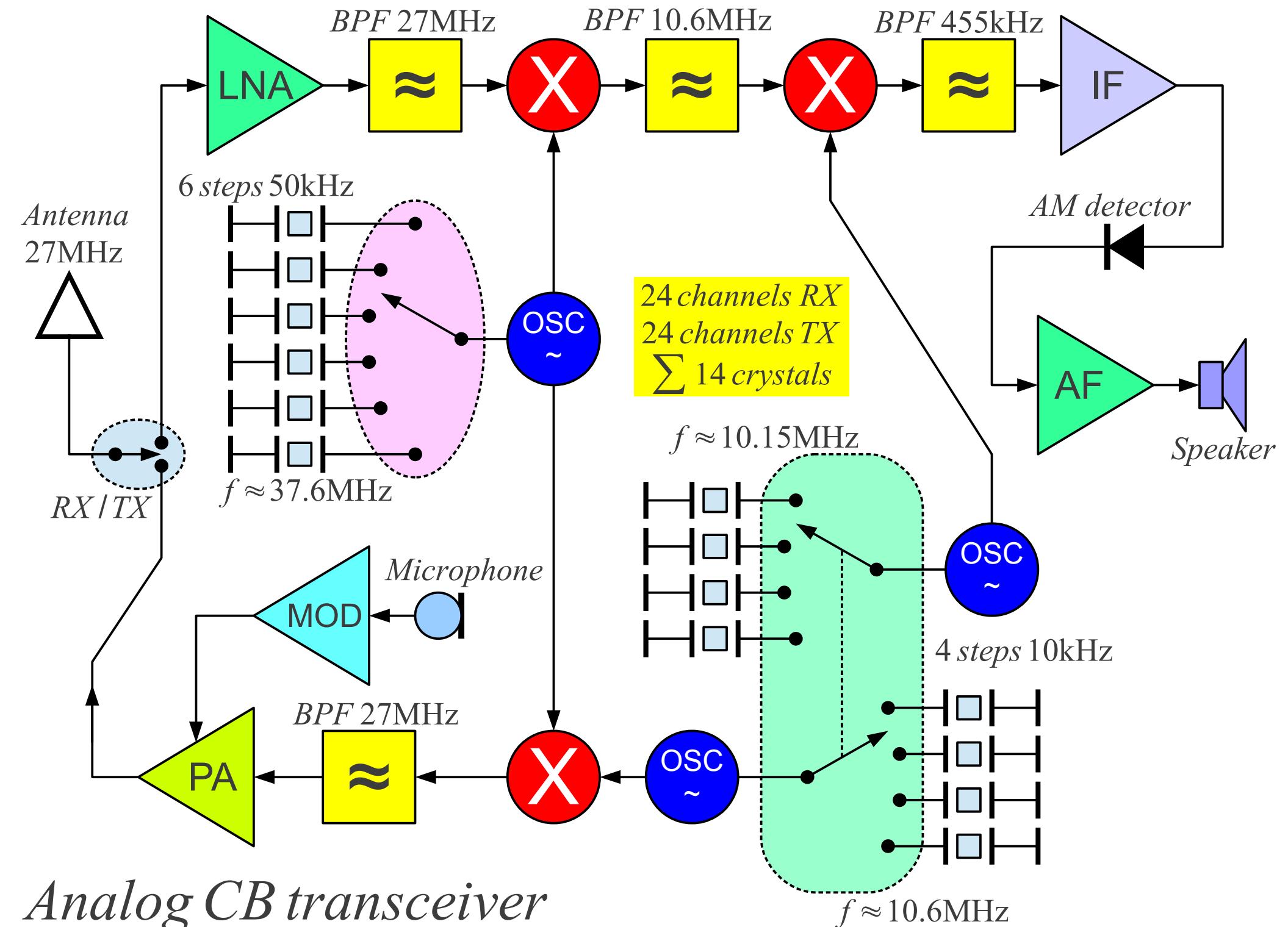

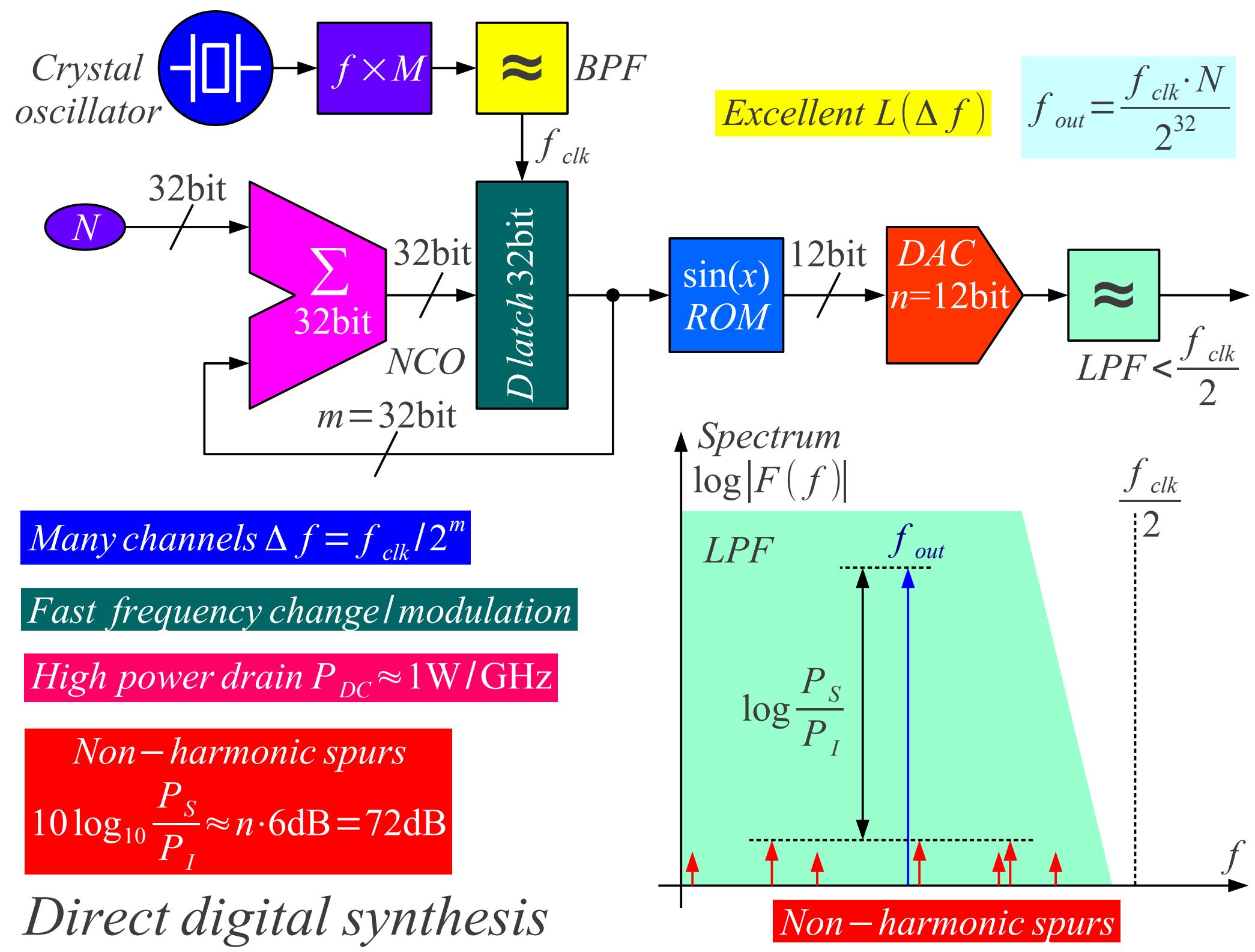

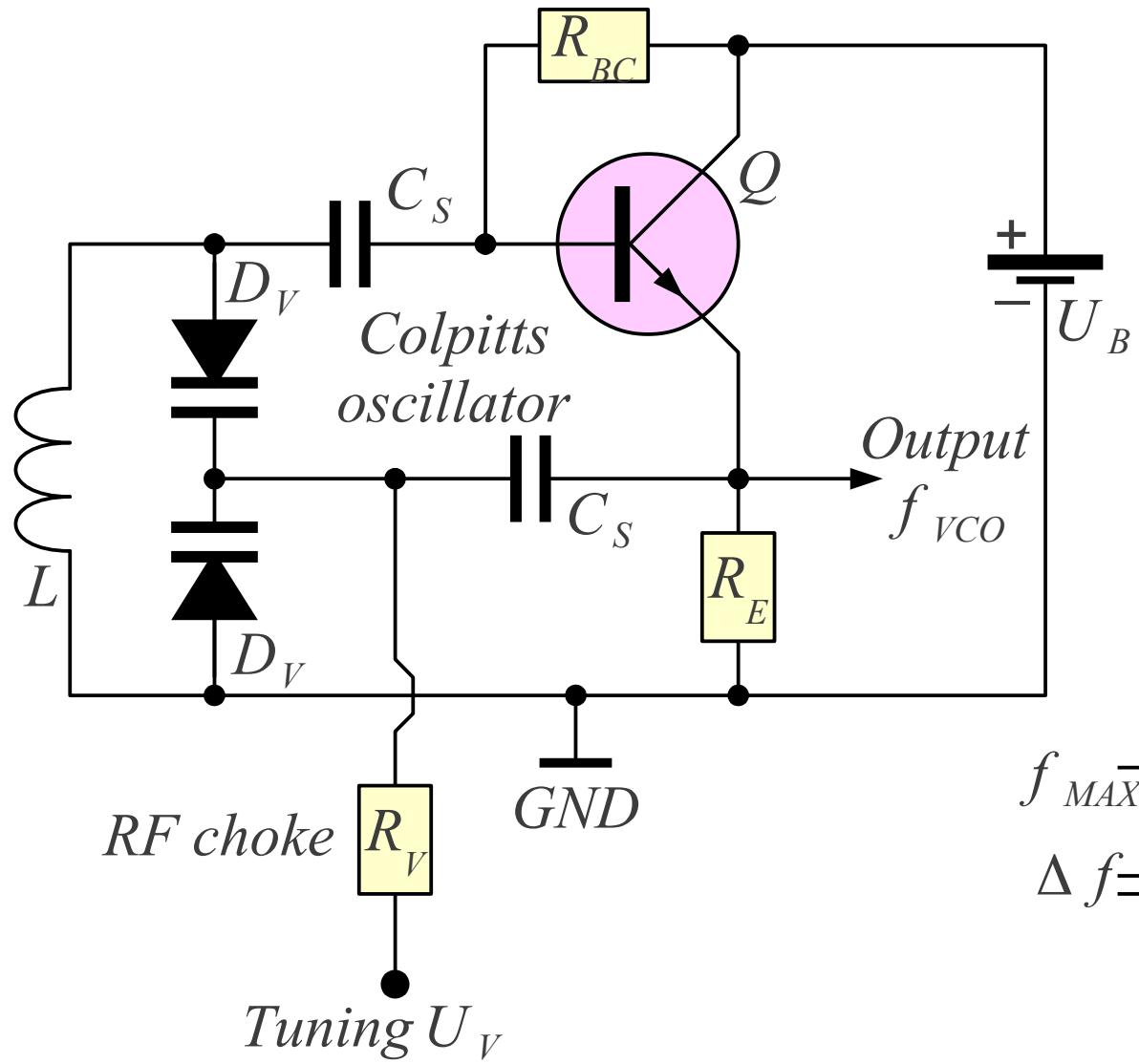


*VCO*≡Voltage – Controlled Oscillator

$$\frac{f_{MAX}}{f_{MIN}} = \left( \frac{C_{MAX}}{C_{MIN}} \right)^{0.5} = \sqrt{\frac{C_{MAX}}{C_{MIN}}}$$

*Voltage – controlled oscillator*

$$K_{VCO} \left[ \frac{\text{rd/s}}{\text{V}} \right] = \frac{d\omega}{dU} = 2\pi \frac{df}{dU}$$
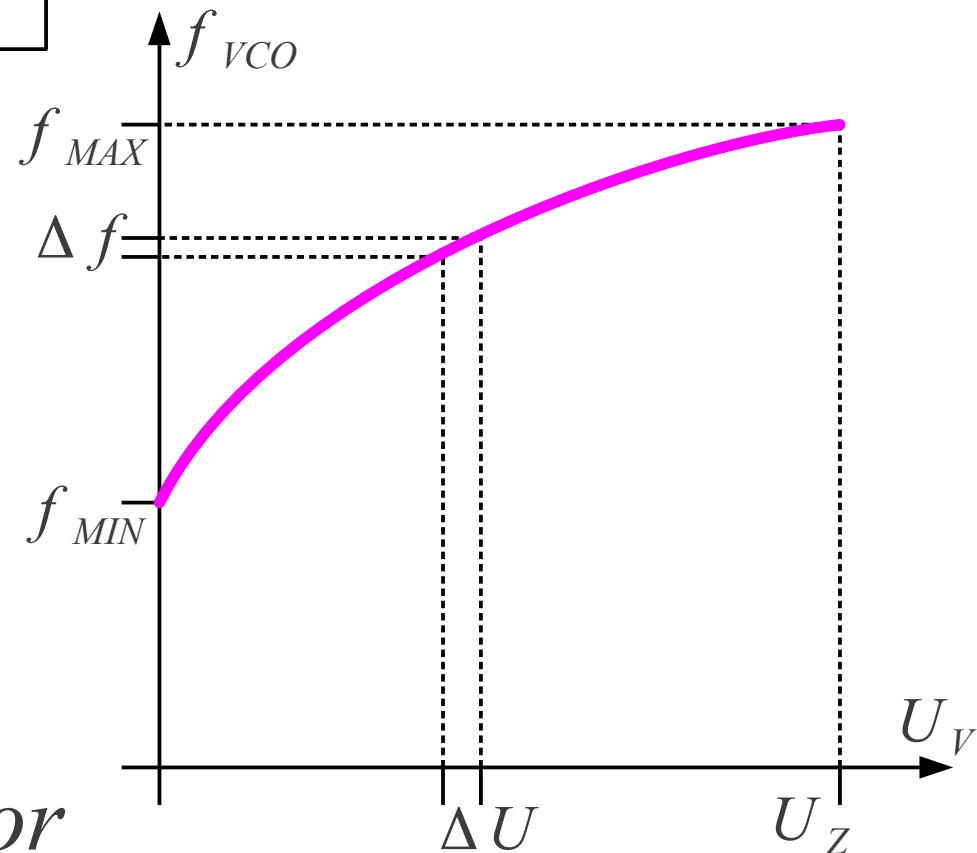
$$K_{VCO} \left[ \frac{\text{Hz}}{\text{V}} \right] = \frac{df}{dU} \approx \frac{\Delta f}{\Delta U}$$



*Comparison of frequency  
or phase or both?*

*Crystal  
oscillator*



$$f_{REF} = \frac{f_{XTAL}}{R}$$

*Locked loop*


$$u_R = U_R \cos(\omega_R t)$$

$$u_N = U_N \cos(\omega_R t + \phi)$$

$$\alpha u_R u_N = \alpha \frac{U_R U_N}{2} \cdot [\cos(2\omega_R t + \phi) + \cos\phi] \rightarrow U_V \approx \alpha \frac{U_R U_N}{2} \cos\phi$$

*Interference!*

$N, R \equiv$  integers!

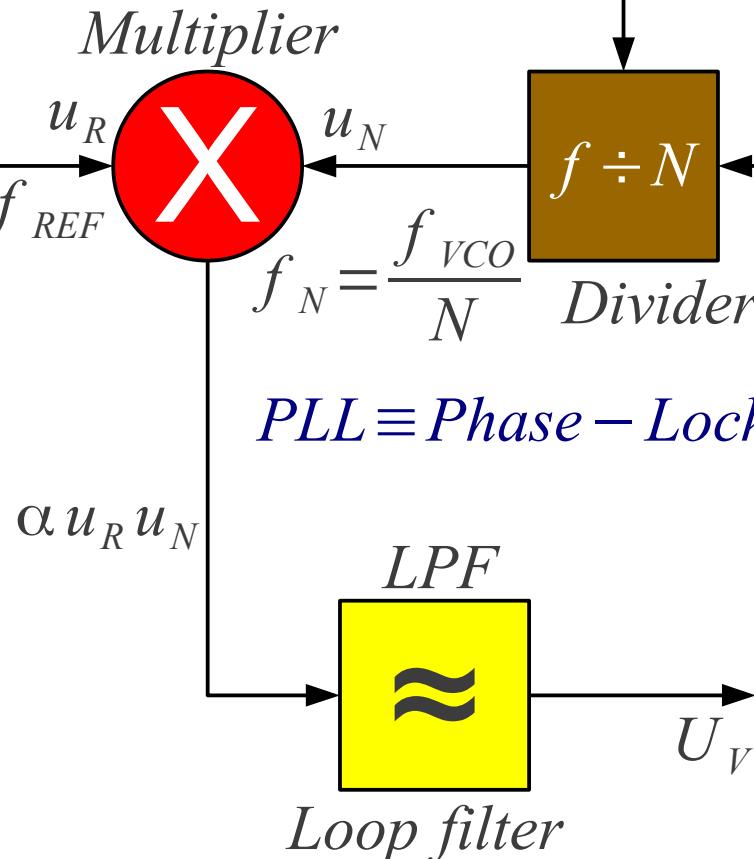


$$f_{VCO} = \frac{N}{R} f_{XTAL}$$

*PLL*  $\equiv$  *Phase – Locked Loop*

*Lock acquisition?  
Interference &  
phase noise?*

*Inexpensive electronics  
low power drain  
single-chip integration  
large choice of  $N$  &  $R$*

*Phase – locked loop*

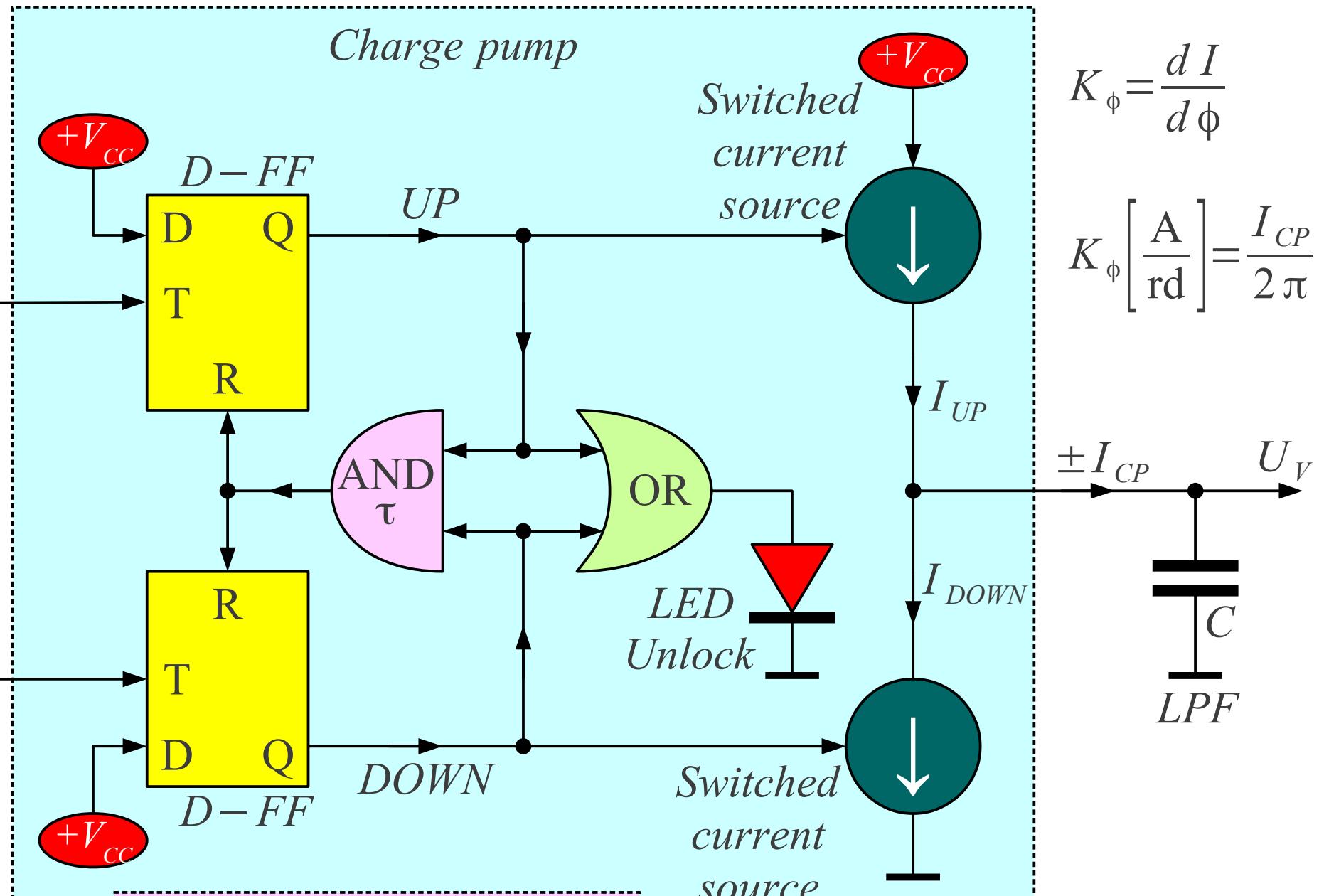

$$K_\phi = \frac{dI}{d\phi}$$

$$K_\phi \left[ \frac{A}{rd} \right] = \frac{I_{CP}}{2\pi}$$


$$I_{UP} = I_{DOWN} = I_{CP} = K_\phi \left[ \frac{A}{cycle} \right]$$

*Frequency / phase comparator*










$$f_N < f_{REF} \quad \phi < \phi_{REF}$$


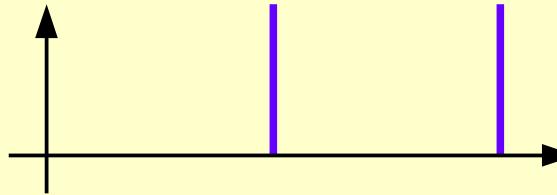
$$f_N > f_{REF} \quad \phi > \phi_{REF}$$



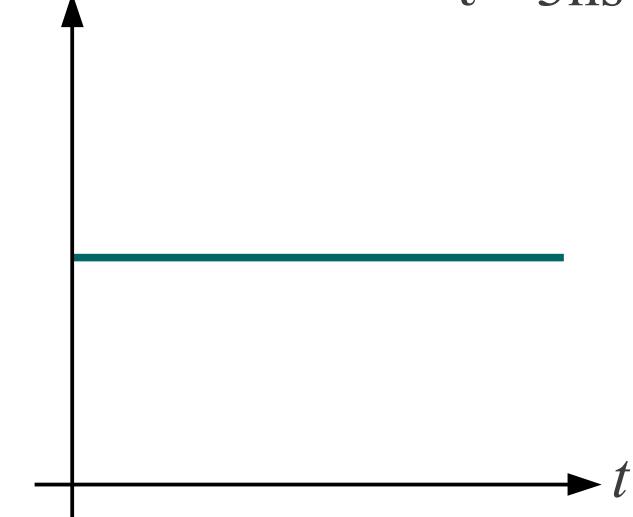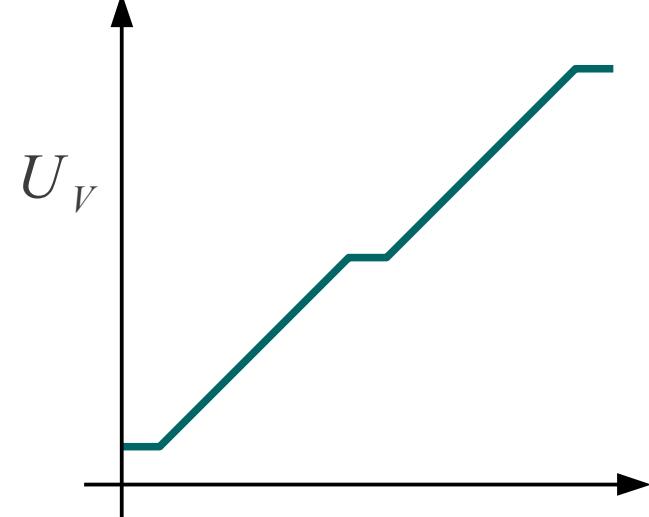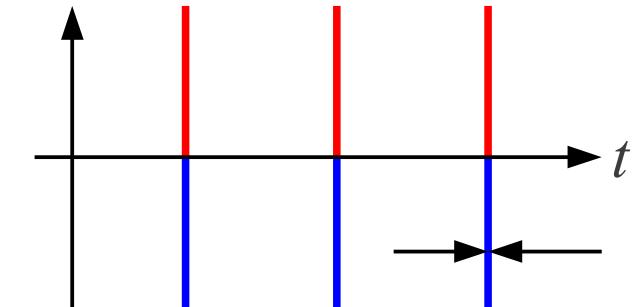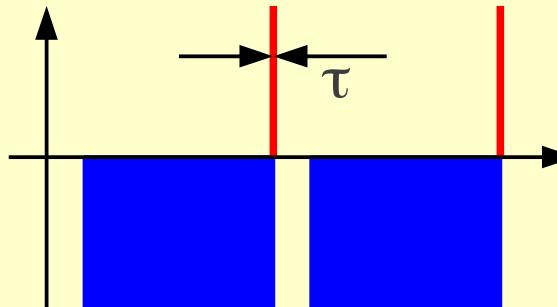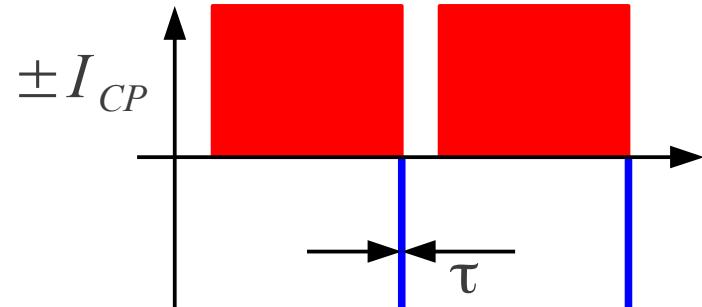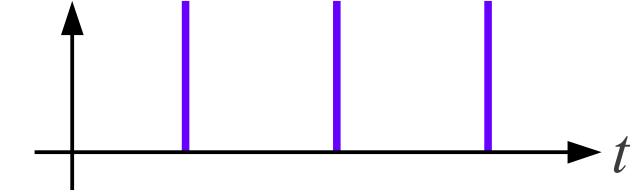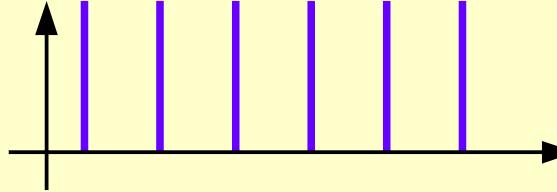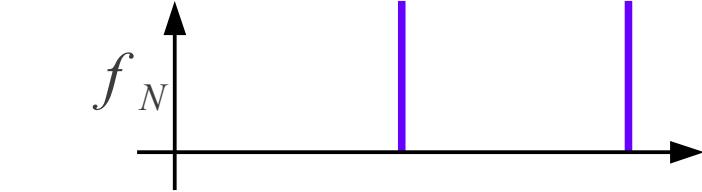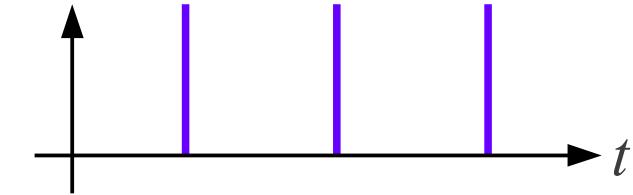
$$f_N = f_{REF} \quad \phi = \phi_{REF}$$



*Charge – pump operation*

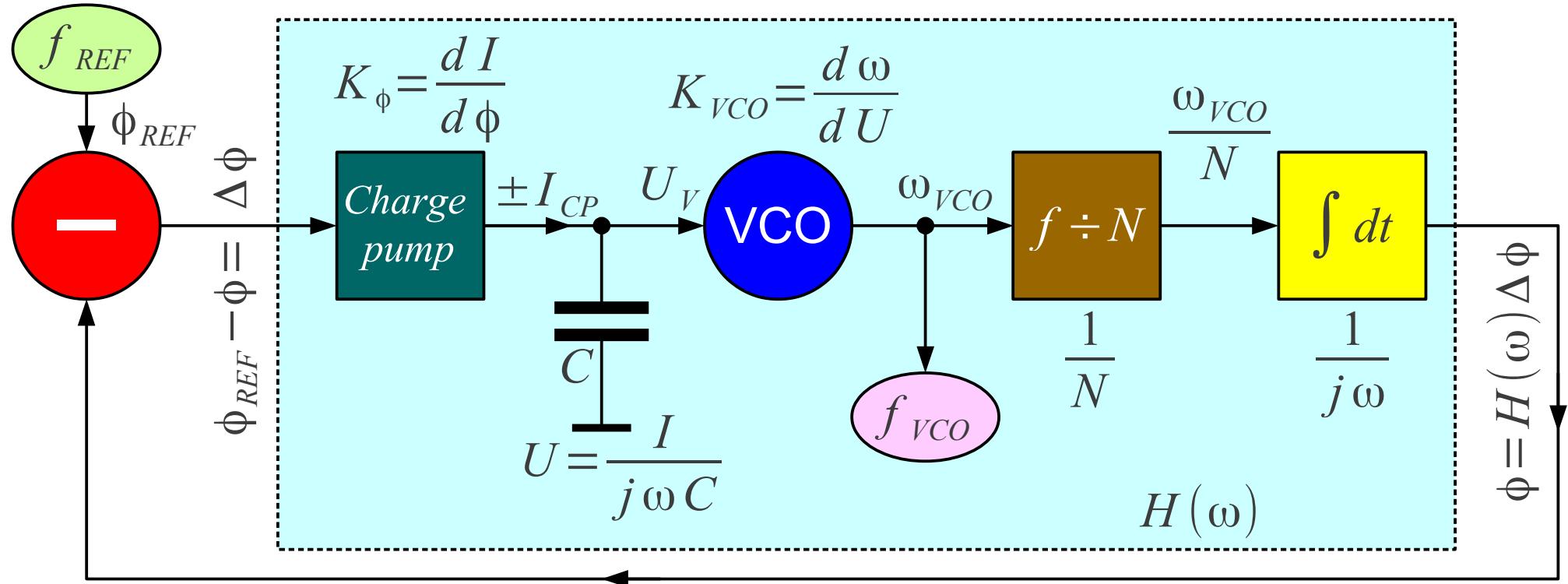Harmonic interference  $\phi = A \cdot e^{st} = A \cdot e^{j\omega t}$  (simplified  $s = \sigma + j\omega$ )



$$\Delta\phi = \frac{\phi_{REF}}{1 + H(\omega)}$$


$$\omega \ll 2\pi f_{REF}$$

$$H(\omega) = K_\phi \cdot \frac{1}{j\omega C} \cdot K_{VCO} \cdot \frac{1}{N} \cdot \frac{1}{j\omega}$$


$$H(\omega) = \frac{-K_\phi K_{VCO}}{\omega^2 C N}$$

$$\omega = \sqrt{\frac{K_\phi K_{VCO}}{C N}}$$

$0 \leftarrow \omega$

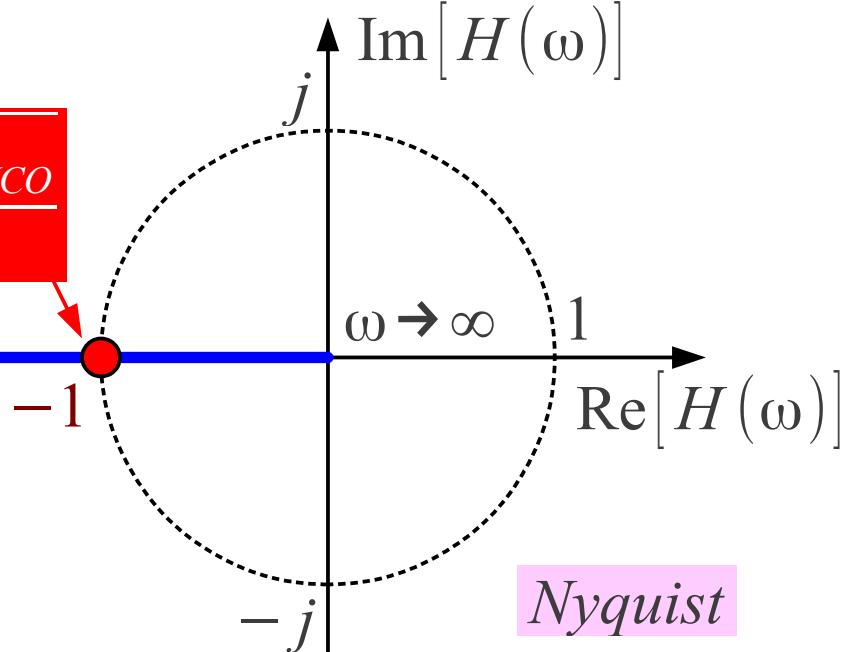

Unstable phase-locked loop

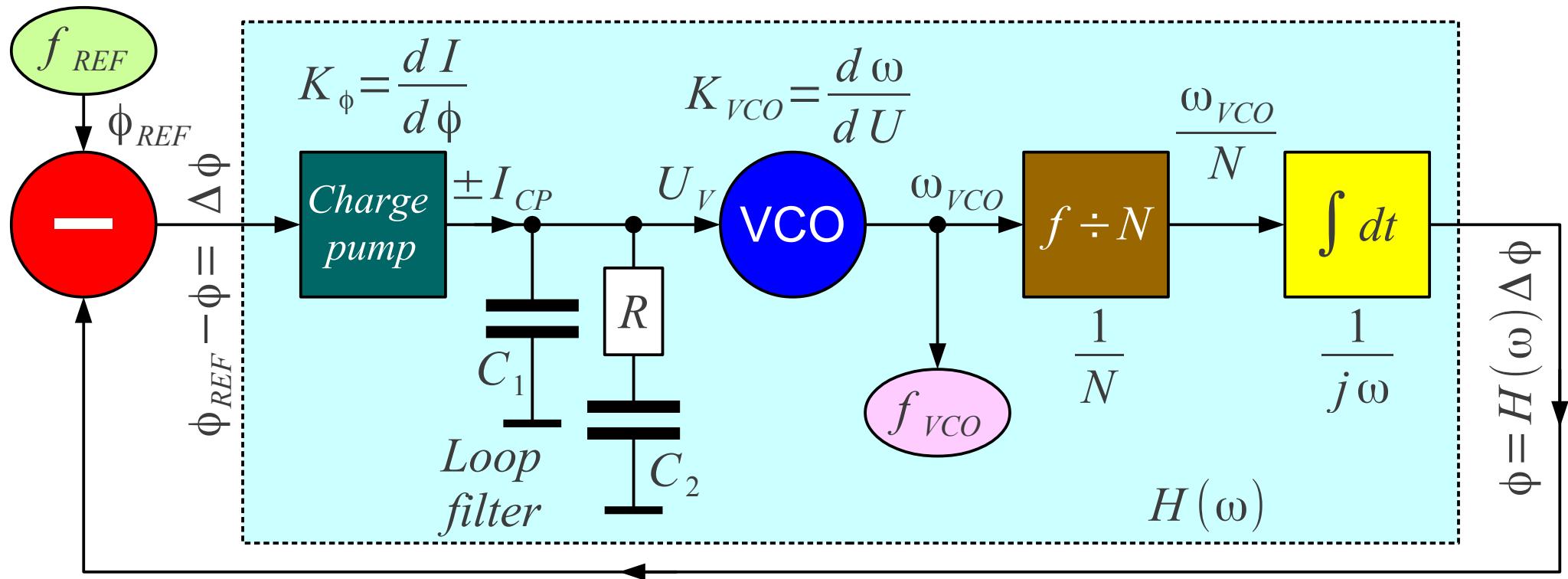

$$H(\omega) = K_\phi \cdot \frac{1}{j\omega C_1 + \frac{1}{R + \frac{1}{j\omega C_2}}} \cdot K_{VCO} \cdot \frac{1}{N} \cdot \frac{1}{j\omega}$$

*Zero:*  $\tau_2 = RC_2$

$$H(\omega) = \frac{-K_\phi K_{VCO}}{\omega^2(C_1 + C_2)N} \cdot \frac{1 + j\omega RC_2}{1 + j\omega R \frac{C_1 C_2}{C_1 + C_2}}$$

$$H(\omega) = \frac{-K_\phi K_{VCO}}{\omega^2(C_1 + C_2)N} \cdot \frac{1 + j\omega \tau_2}{1 + j\omega \tau_1}$$

*Pole:*  $\tau_1 = R \frac{C_1 C_2}{C_1 + C_2}$


*Stable phase-locked loop*

$$H(\omega) = \frac{-K_\phi K_{VCO}}{\omega^2(C_1 + C_2)N} \cdot \frac{1+j\omega\tau_2}{1+j\omega\tau_1}$$

$$\phi_m = \arctan \frac{\omega(\tau_2 - \tau_1)}{1 + \omega^2 \tau_1 \tau_2}$$

*Max phase margin:*
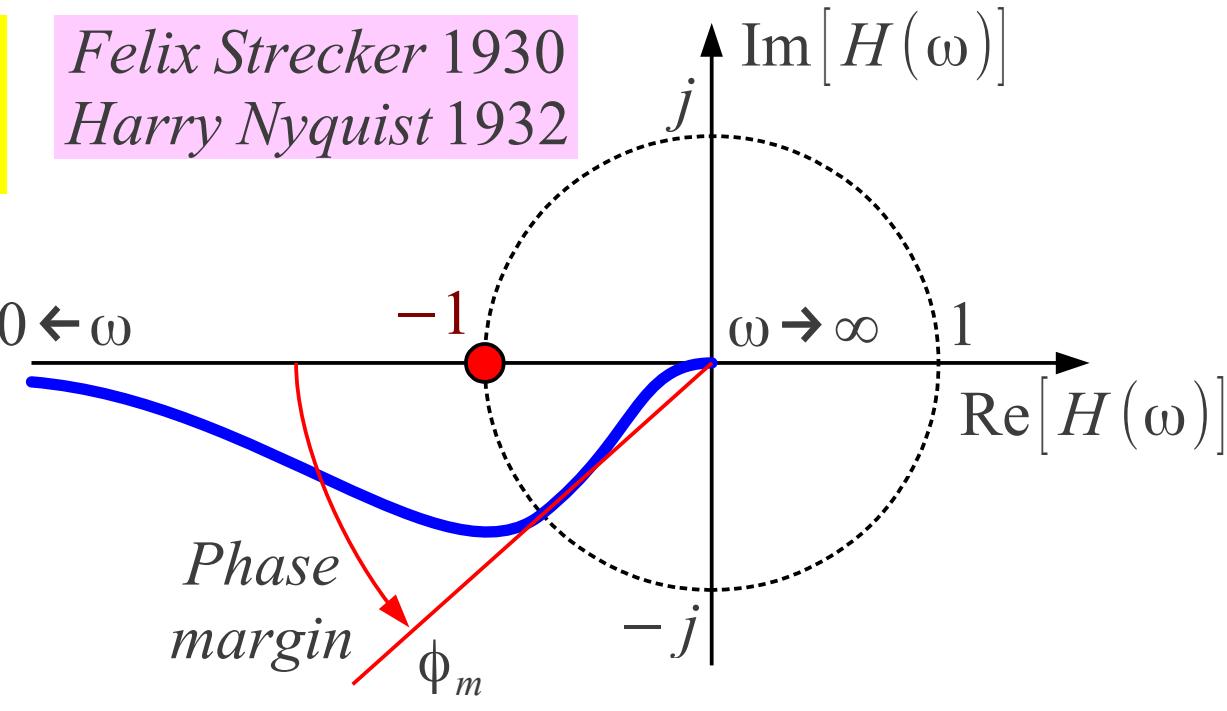
$$\frac{d\phi_m}{d\omega} = 0 \rightarrow \omega_m = \frac{1}{\sqrt{\tau_1 \tau_2}}$$



*zero/pole ratio*  $\equiv m = \frac{\tau_2}{\tau_1} \rightarrow \sqrt{m} = \omega_m \tau_2 = \frac{1}{\omega_m \tau_1} \rightarrow C_1 + C_2 = m C_1$

*Unity circle*  $1 = |H(\omega_m)| = \frac{K_\phi K_{VCO}}{\omega_m^2 m C_1 N} \cdot \sqrt{\frac{1+m}{1+\frac{1}{m}}} = \frac{K_\phi K_{VCO}}{\omega_m^2 C_1 N \sqrt{m}}$

$$\omega_m = \sqrt{\frac{K_\phi K_{VCO}}{C_1 N \sqrt{m}}} \approx 2\pi B_{loop}$$

*Loop-filter calculation*

*Compatible measurement units!*


$$C_1 = \frac{K_\phi K_{VCO}}{\omega_m^2 N \sqrt{m}}$$

$$C_2 = (m-1) C_1$$

$$R = \frac{\sqrt{m}}{\omega_m C_2}$$


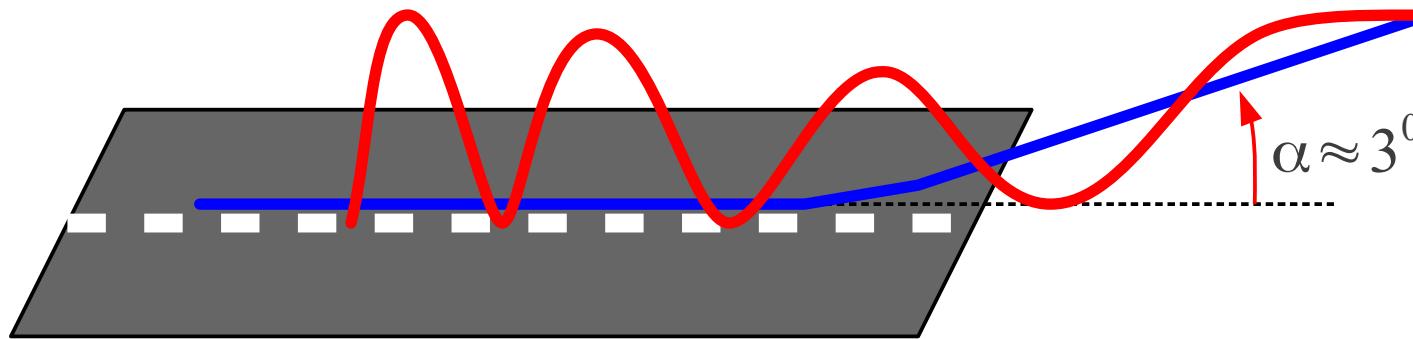
# Landing autopilot

*PIO  $\equiv$  Pilot – Induced Oscillations*




$$\text{Im}[H(\omega)]$$



$$\text{Re}[H(\omega)]$$

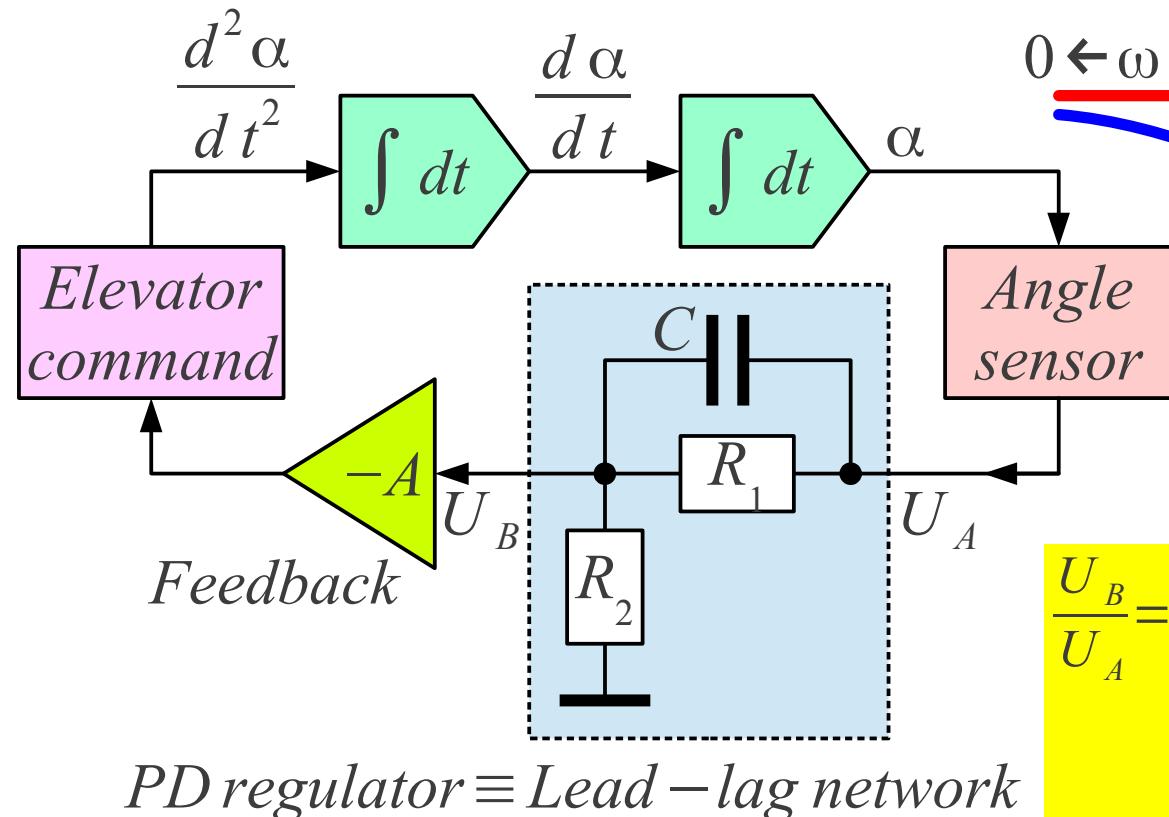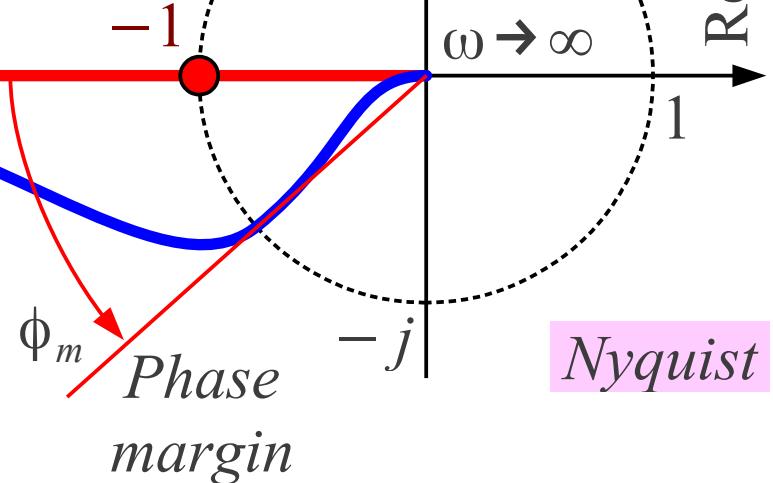

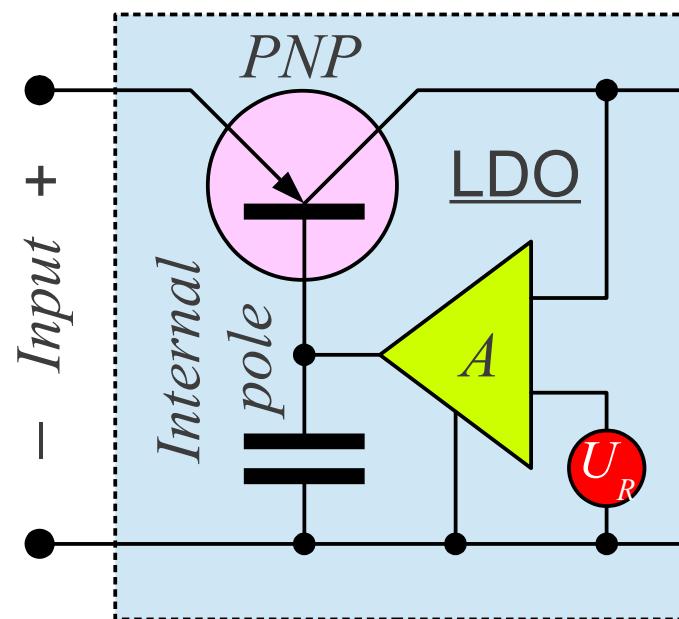
$$\frac{U_B}{U_A} = \frac{R_2}{R_2 + \frac{1}{j\omega C + \frac{1}{R_1}}} = \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\omega R_1 C}{1 + j\omega \frac{R_1 R_2}{R_1 + R_2} C}$$



$LDO \equiv Low\ Drop-Out$

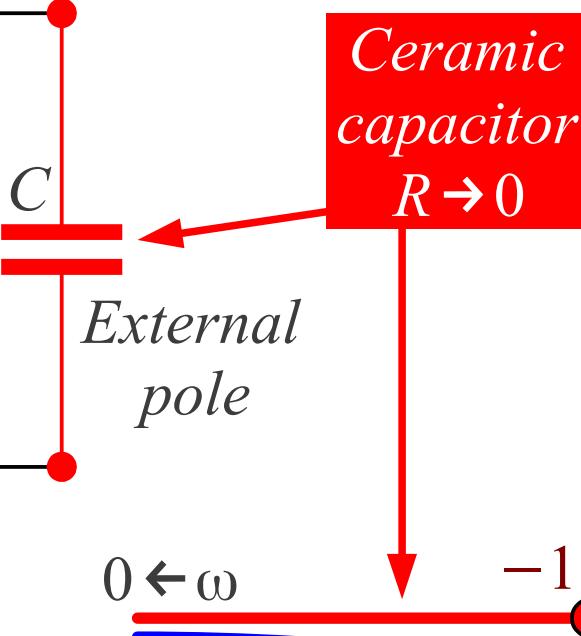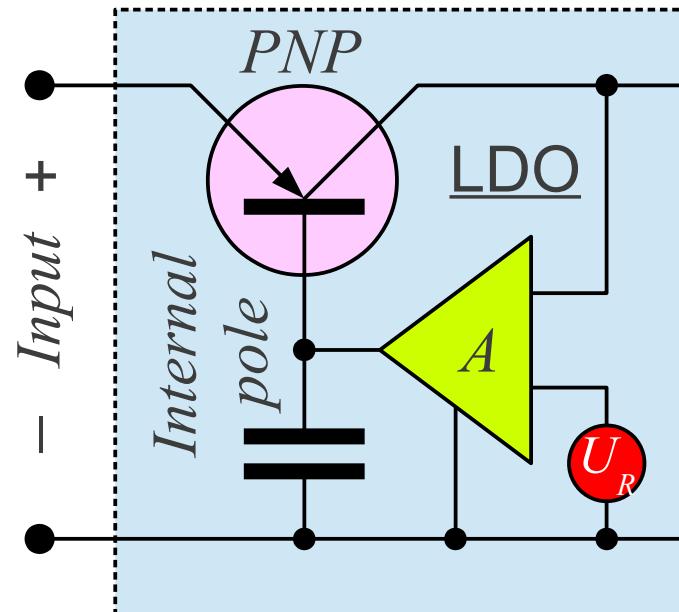

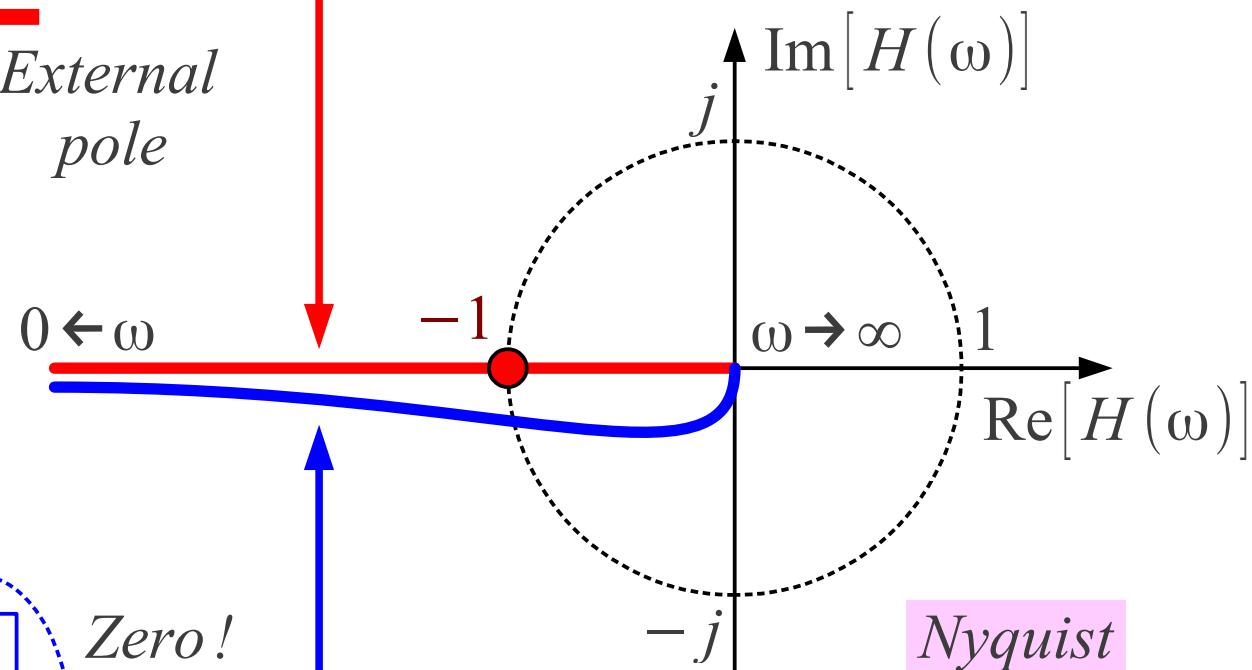*LDO problem:*  
too large  $A$   
*PNP common E*



*Al electrolytic capacitor*  
 $R \neq 0$

*Old regulators:*  
lower  $A$   
*NPN common C*

*Unstable voltage regulator*


Max phase margin:

$$\phi_m = \arctan \frac{m-1}{2\sqrt{m}}$$

Overshoot:  $a_{\text{dB}} \approx -20 \log_{10} \phi_m [\text{rd}]$

$m$	$C_2/C_1$	$\phi_m [^{\circ}]$	$a$
1	0	$0^{\circ}$	$\infty \text{dB}$
1.1	0.1	$2.73^{\circ}$	26.4dB
1.2	0.2	$5.22^{\circ}$	20.8dB
1.5	0.5	$11.5^{\circ}$	13.9dB
2	1	$19.5^{\circ}$	9.4dB
3	2	$30.0^{\circ}$	5.6dB
5	4	$41.8^{\circ}$	2.7dB
10	9	$54.9^{\circ}$	0.4dB
20	19	$64.8^{\circ}$	—
50	49	$73.9^{\circ}$	—
100	99	$78.6^{\circ}$	—
200	199	$81.9^{\circ}$	—

Zero/pole ratio

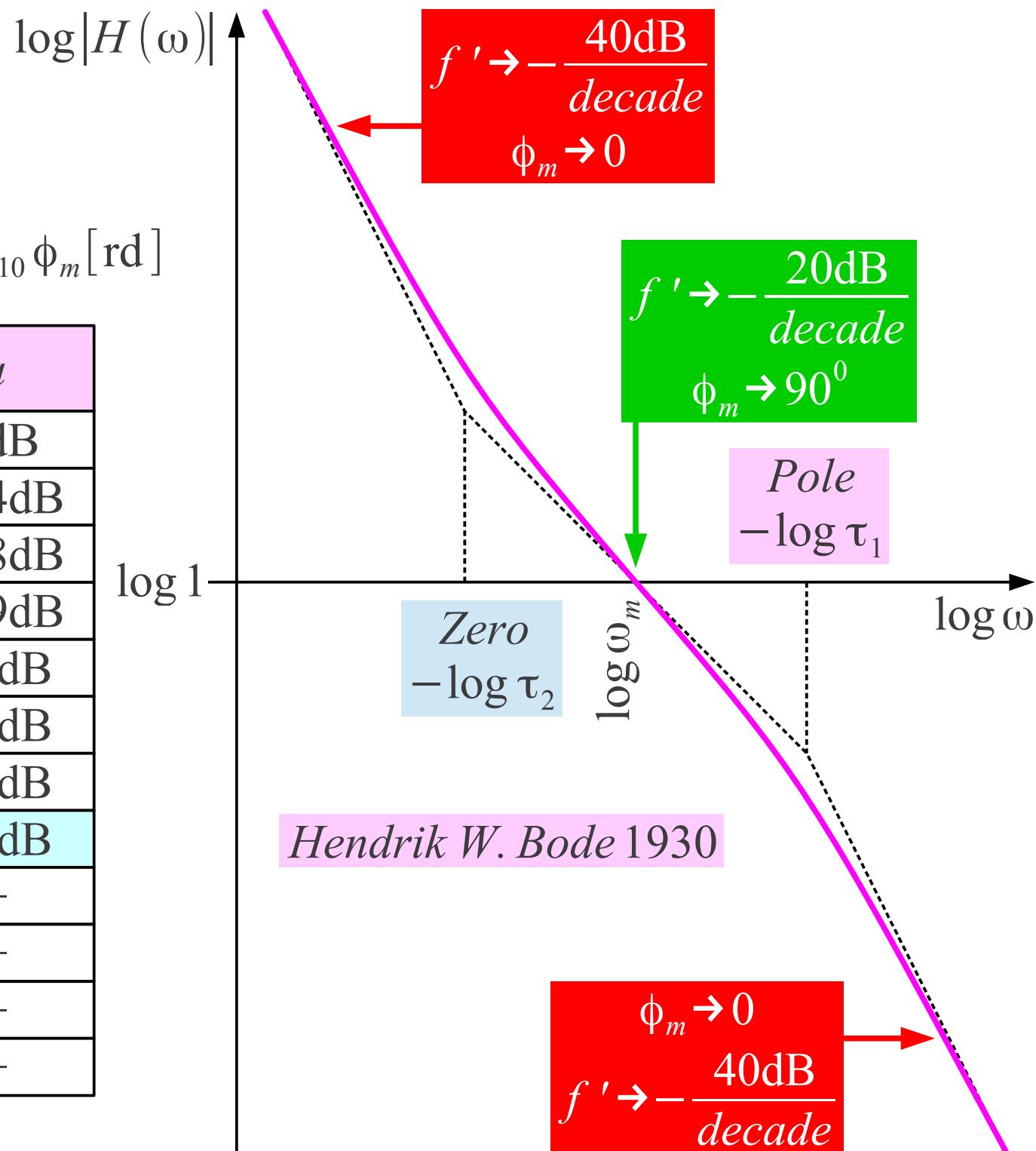

# Phase – noise transfer

Max phase margin :

$$\phi_m = \arctan \frac{m-1}{2\sqrt{m}}$$

Overshoot :  $a \approx \frac{1}{\phi_m [\text{rd}]}$



$$a_{\text{dB}} \approx -20 \log_{10} \phi_m [\text{rd}]$$

SDH regenerator  $a < 0.1 \text{ dB}$


Phase – noise  $\Delta f$  :




$$\omega \rightarrow 2\pi\Delta f$$
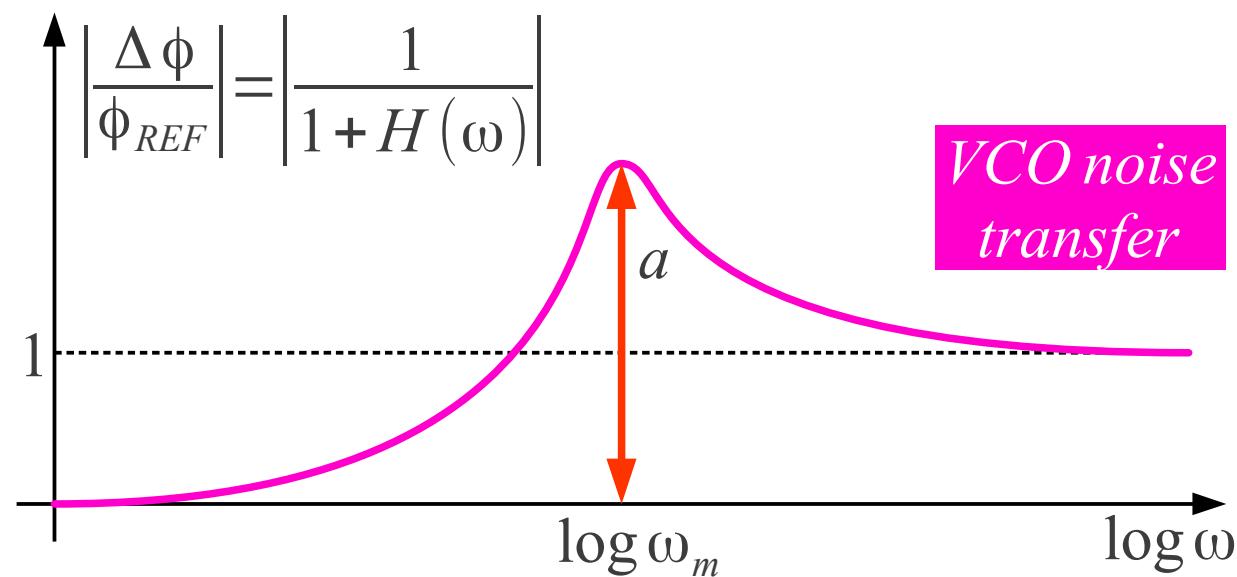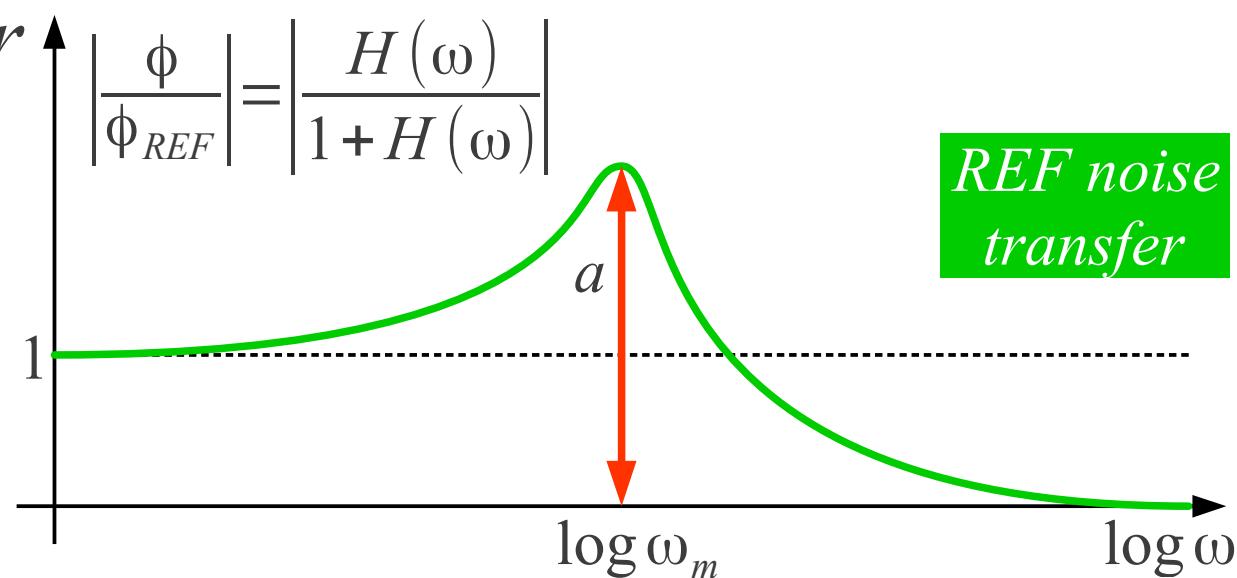
$$H(\omega) \rightarrow H(2\pi\Delta f)$$



$$L(\Delta f) = L(\Delta f)_{REF} \cdot N^2 \cdot \left| \frac{H(2\pi\Delta f)}{1+H(2\pi\Delta f)} \right|^2 + L(\Delta f)_{VCO} \cdot \left| \frac{1}{1+H(2\pi\Delta f)} \right|^2$$

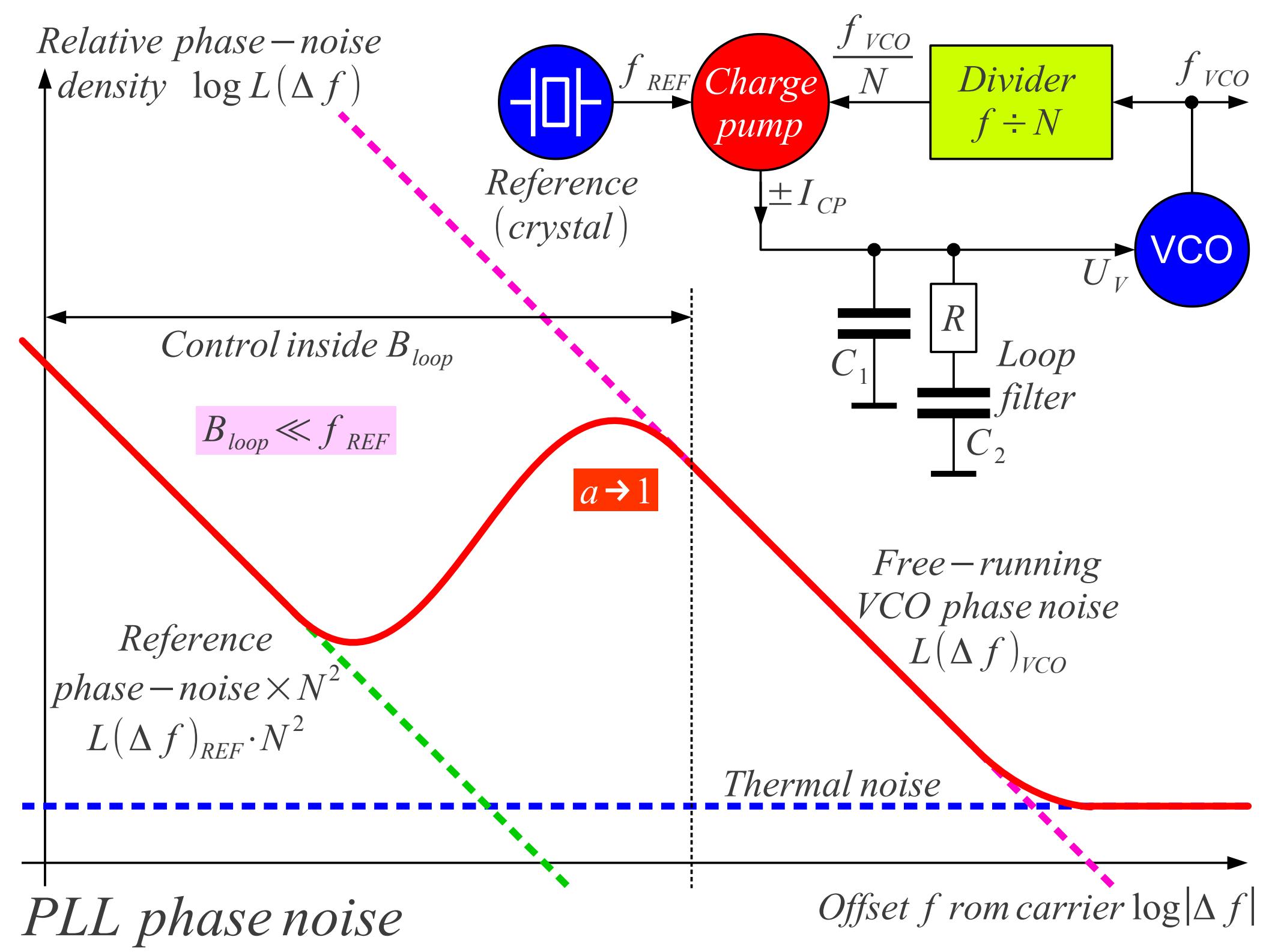


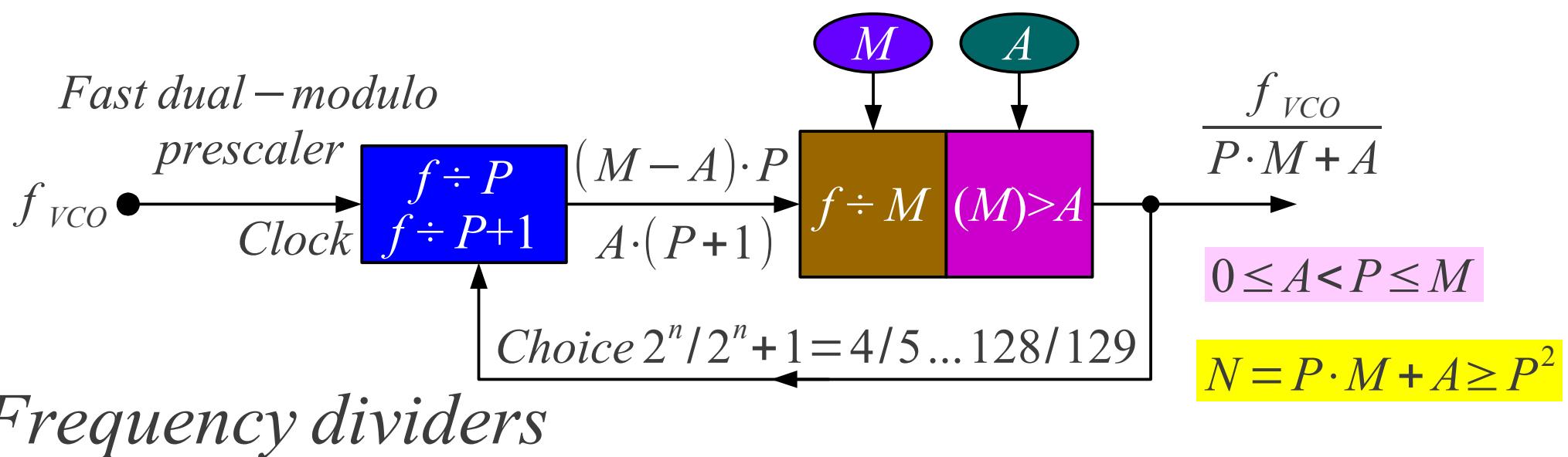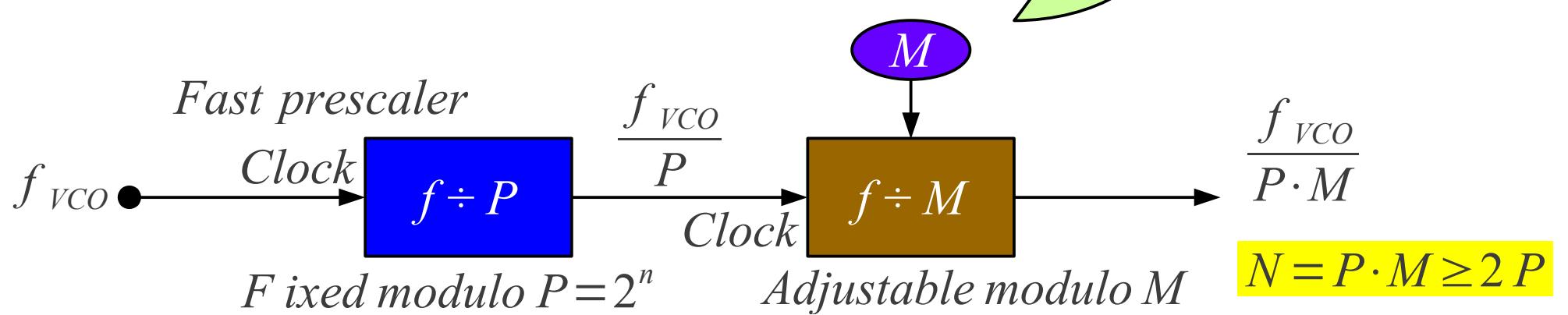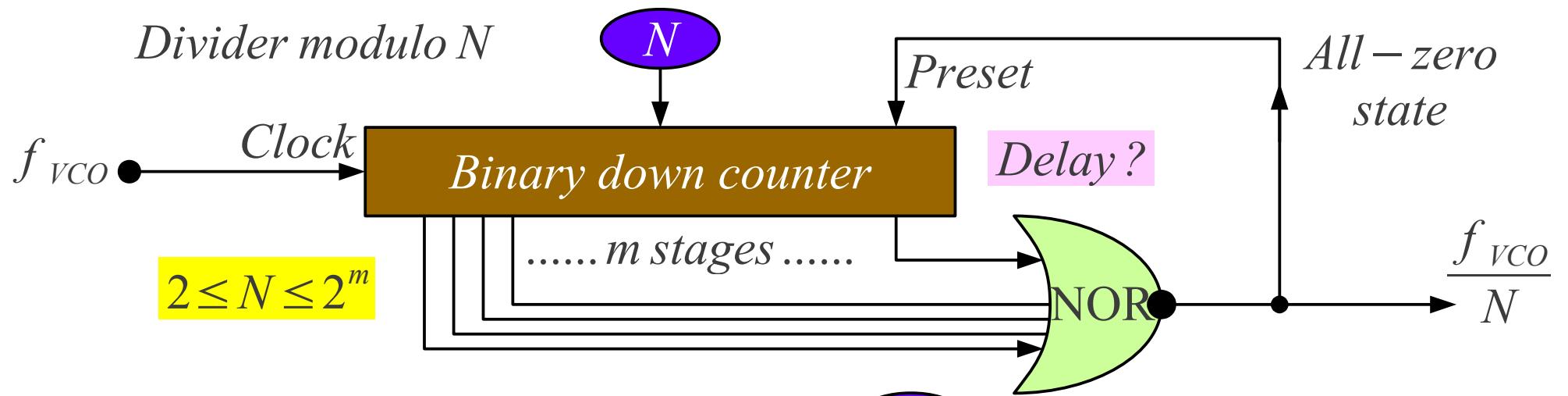

Crystal oscillator



Divider

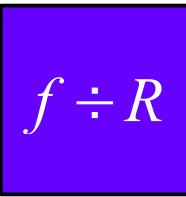

Deviation limit:  
 $-2\pi < \Delta\phi < 2\pi$

PLL only intended  
for long-term  
frequency stability

Example: hand-held  
FM transceiver

$$f_{VCO} \approx 160 \text{ MHz} \text{ (2m band)}$$


$$f_{REF} = 25 \text{ kHz} \text{ (channels)}$$

$$N \approx 6400$$

$$B_{loop} \approx 100 \text{ Hz}$$


$$300 \text{ Hz} < f_{mod} < 3 \text{ kHz}$$
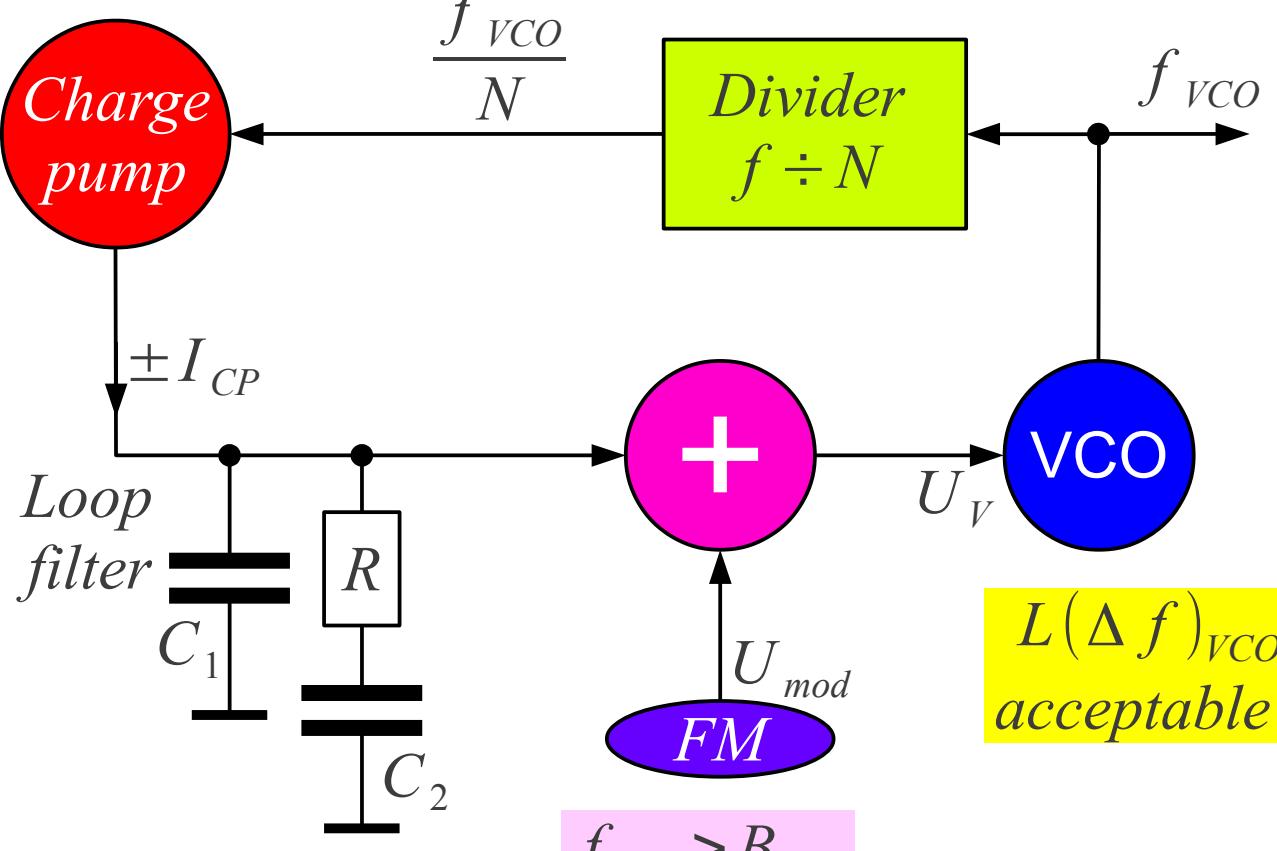
$$\text{deviation } \Delta f = \pm 5 \text{ kHz}$$




Large  $N$  &  $R \rightarrow$  Small  $B_{loop}$

Analog frequency modulation & PLL

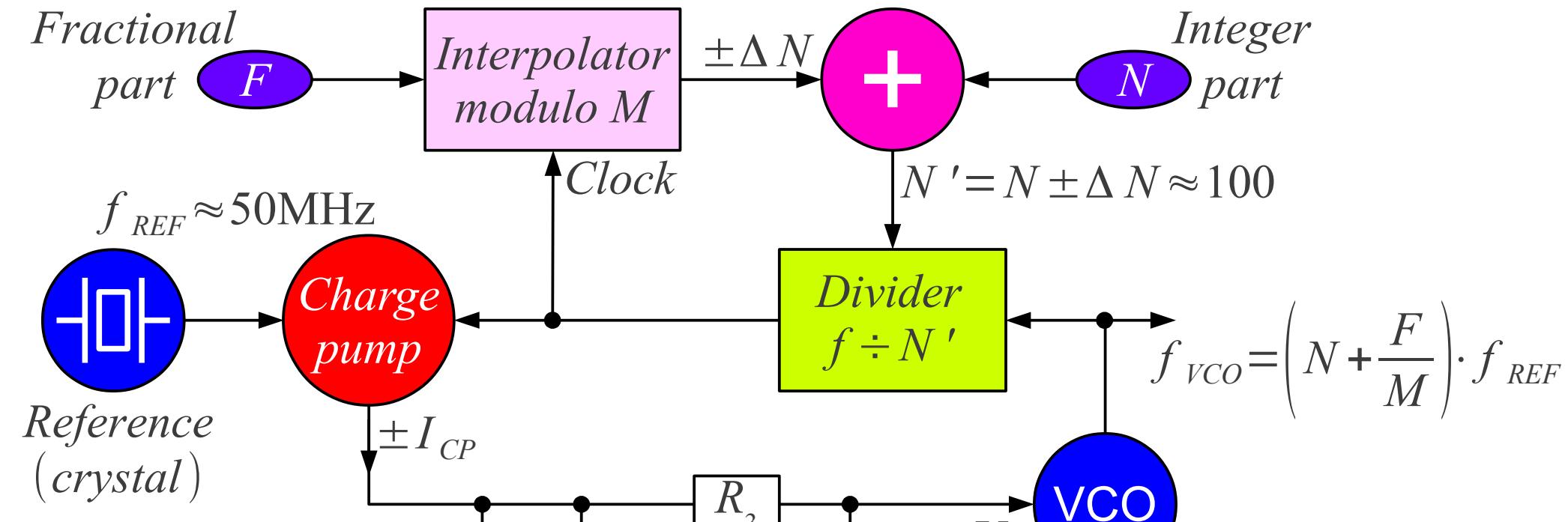

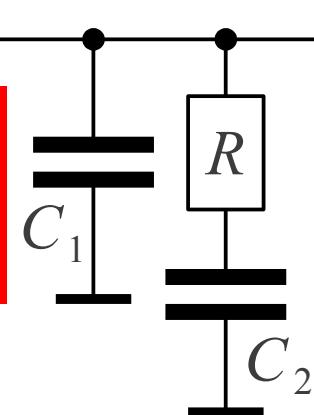
Interpolation noise :  
third-order  
loop filter




Divider  $R$   
usually NOT  
used in  
fractional loops

Low  $N \rightarrow$  Large  $B_{loop}$

Fractional PLL

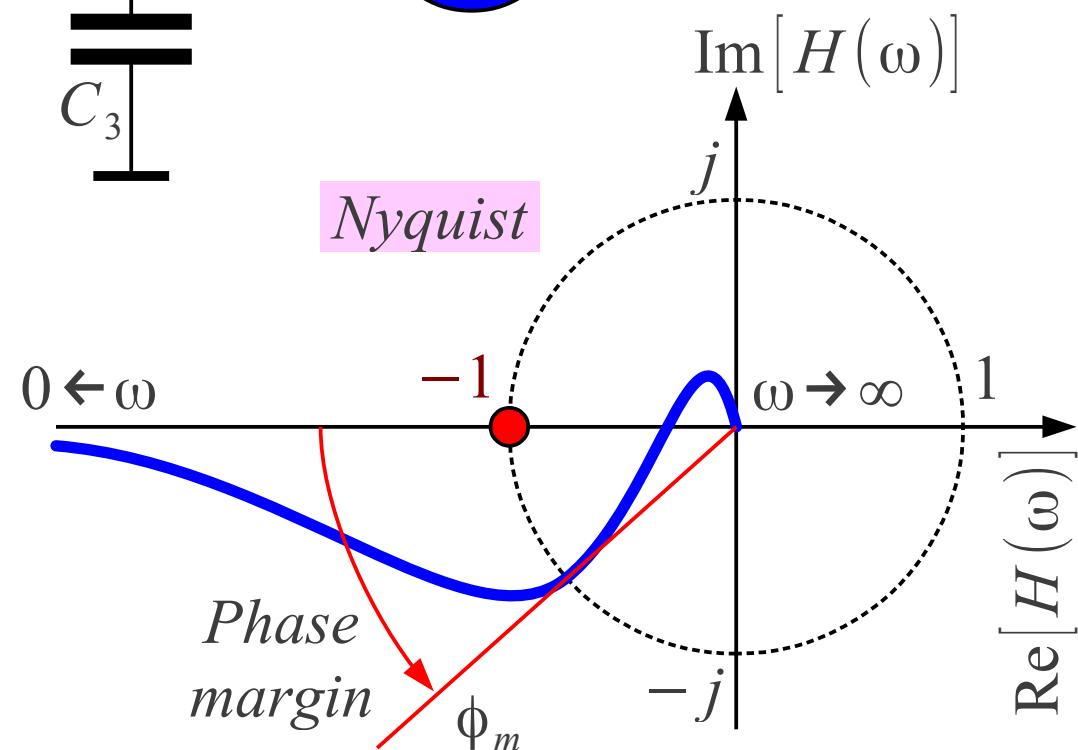

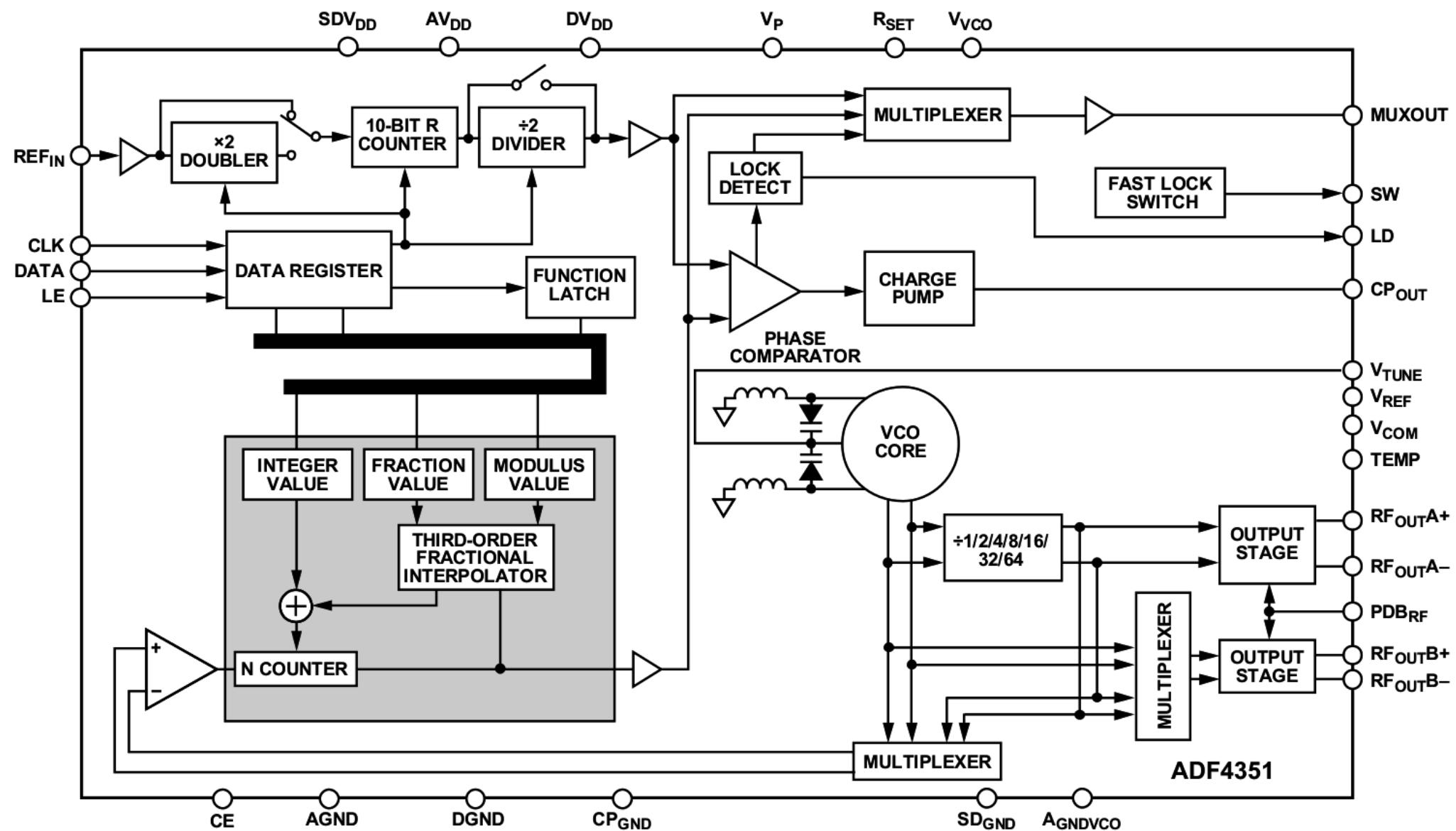Pin-compatible clone MAX2871 (Maxim) better than the original ...



Fractional PLL ADF4351 from Analog Devices

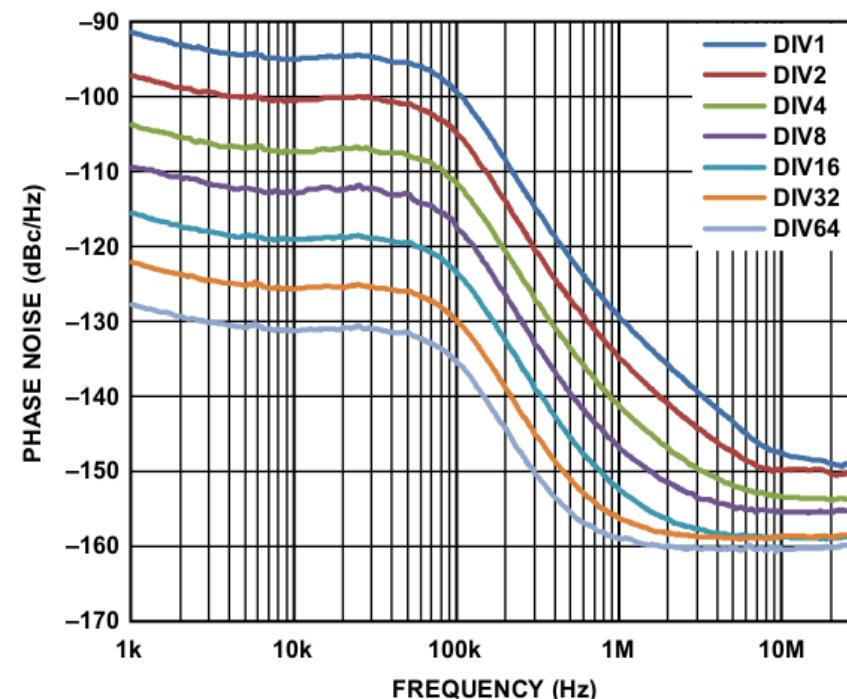


Figure 9. Closed-Loop Phase Noise, Fundamental VCO and Dividers,  
VCO = 4.4 GHz, PFD = 25 MHz, Loop Filter Bandwidth = 63 kHz

$$C_1 = 3.3\text{nF}$$

$$C_2 = 47\text{nF}$$

$$R = 390 \Omega$$

$$\tau_1 = 1.2 \mu\text{s}$$

$$\tau_2 = 18 \mu\text{s}$$

$$R_3 = 1.5\text{k} \Omega$$

$$C_3 = 470\text{pF}$$

$$\tau_3 = 0.7 \mu\text{s}$$

*LO with ADF4351*

