
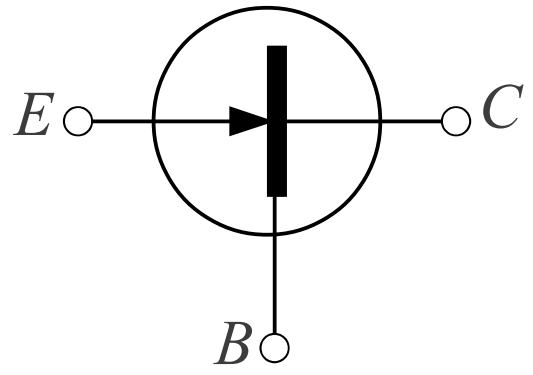
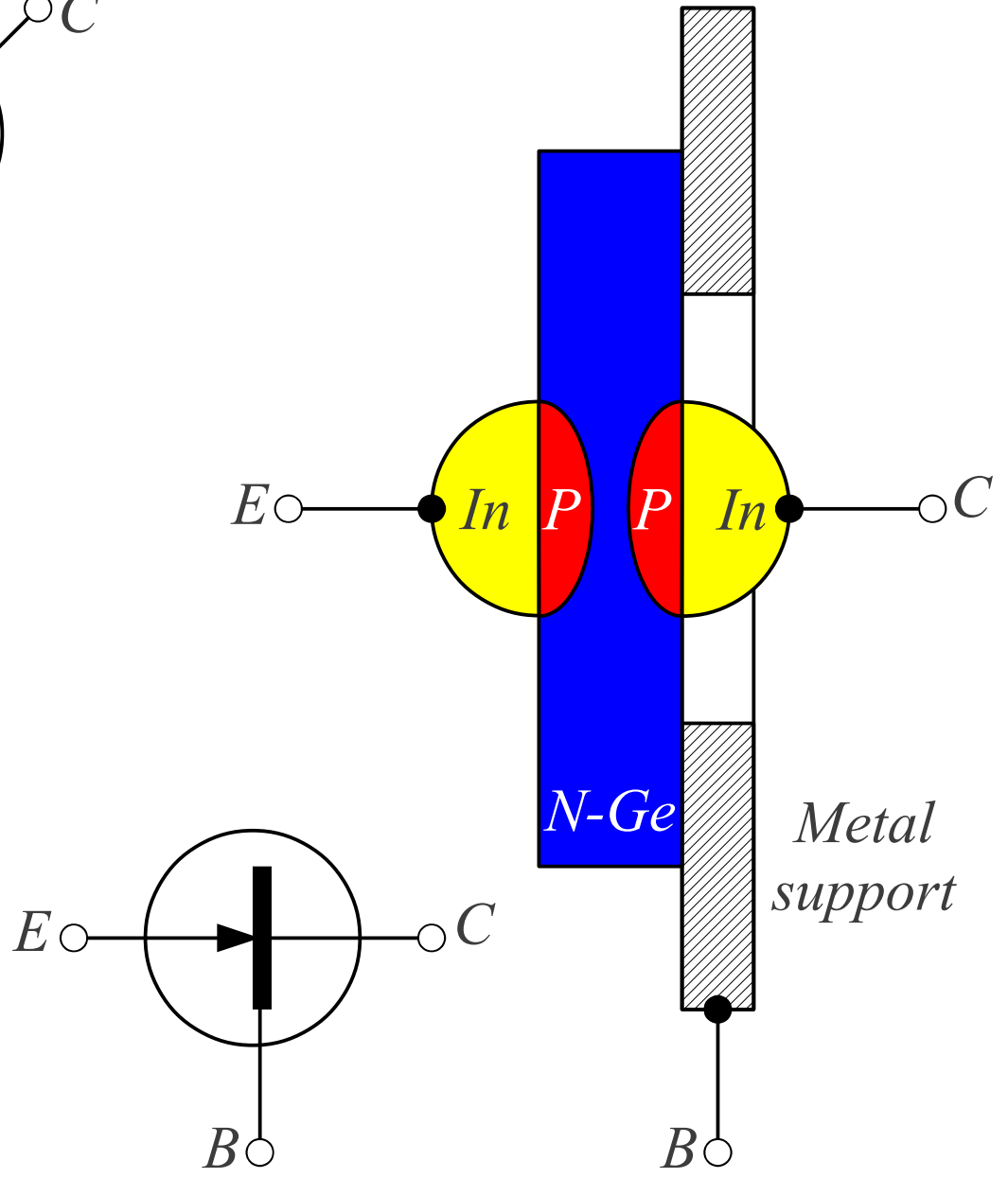
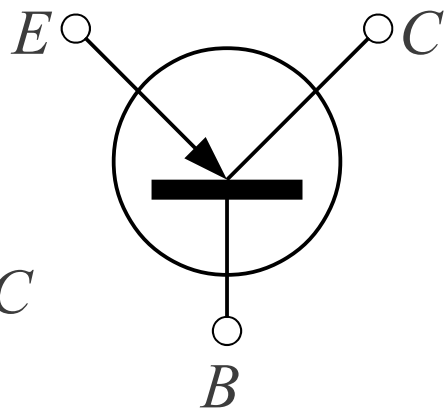


Communication Electronics

Lecture 6:

Semiconductor devices for
communications - transistors

Drawings not to scale

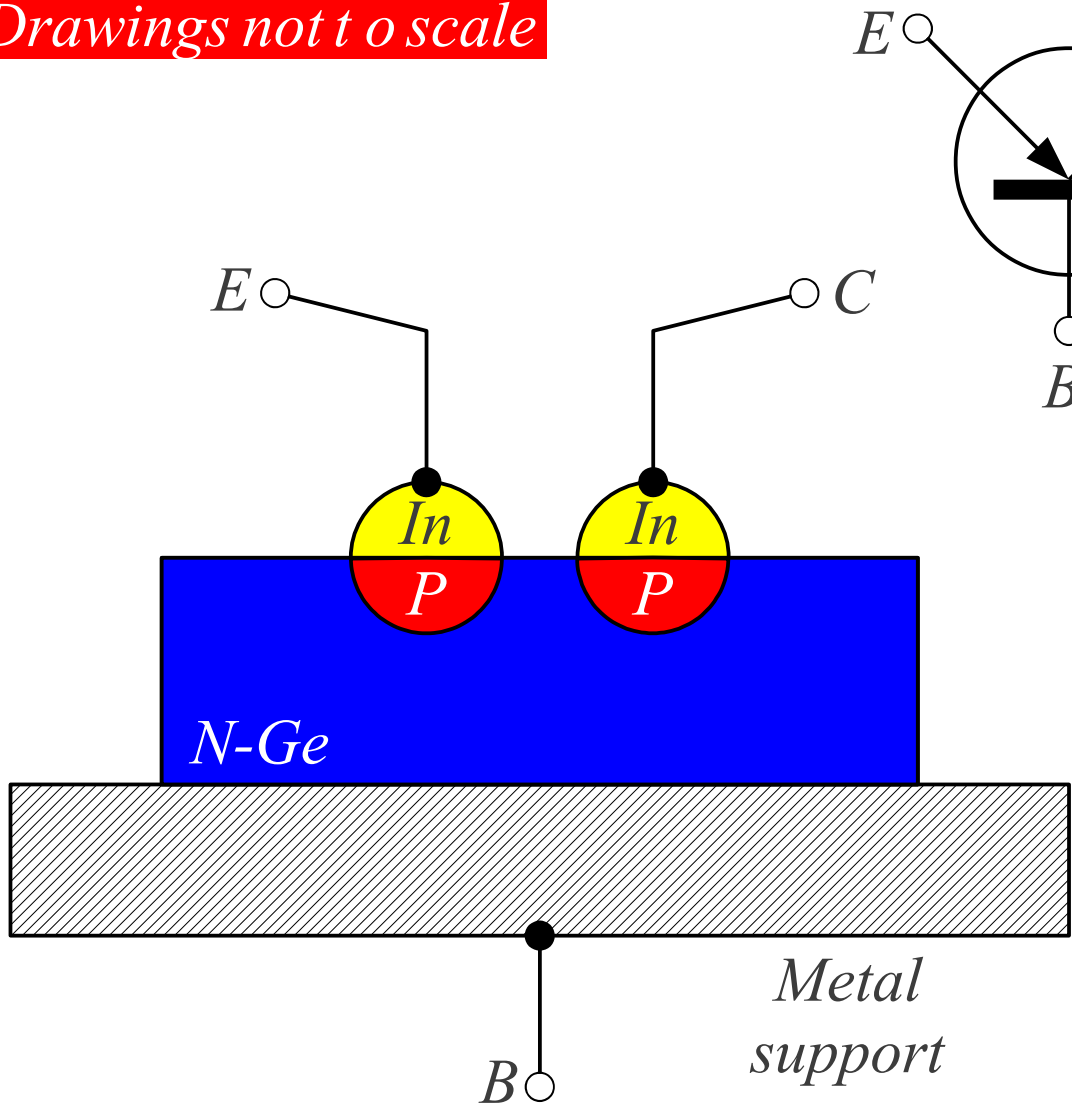


Germanium PNP transistors

$$A_I = \frac{d I_C}{d I_E} = \alpha < 1 \equiv \text{current gain}$$

$$n \approx 1 \quad U_T = \frac{k_B T}{|Q_e|} \approx 25\text{mV}$$

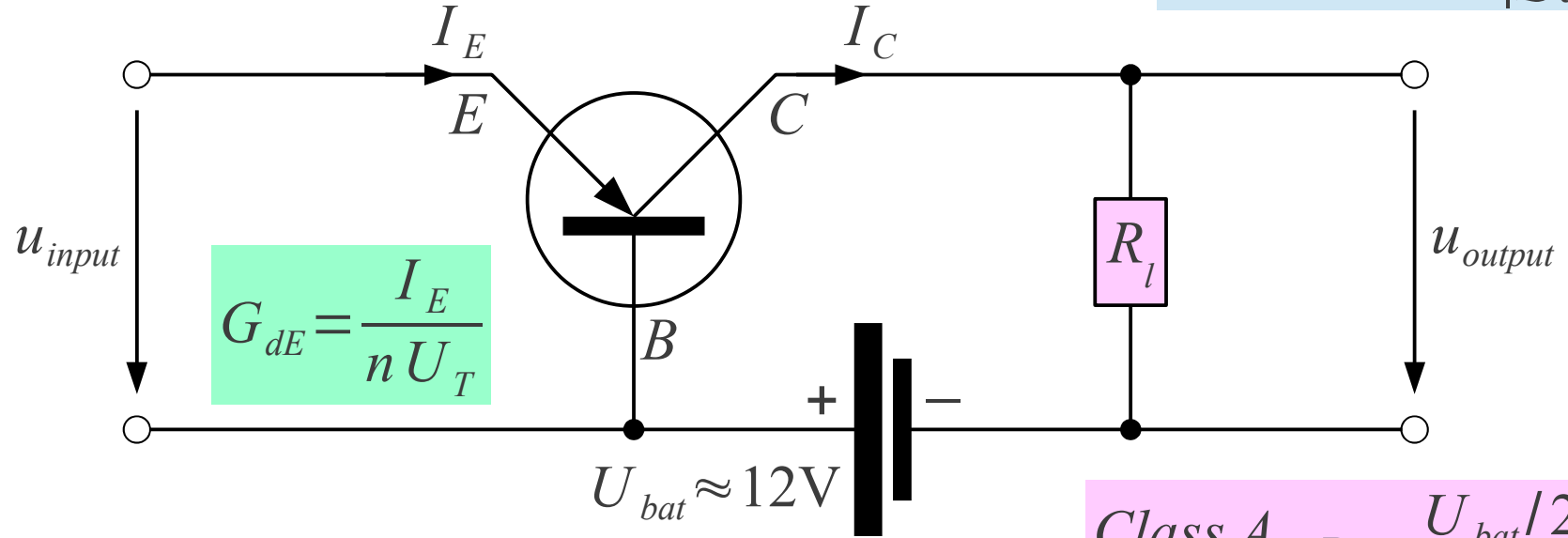Old $\alpha \approx 0.9$
New $\alpha \approx 0.996$



$$G_{dE} = \frac{I_E}{n U_T}$$



Class A bias $R_l \approx \frac{U_{bat}/2}{I_C} = \frac{U_{bat}/2}{\alpha I_E}$

$$A_U = \frac{d u_{output}}{d u_{input}} = \frac{R_l}{R_{dE}} \cdot \frac{d I_C}{d I_E} = \alpha R_l G_{dE} \equiv \text{voltage gain}$$

$$A_U \approx \alpha \cdot \frac{U_{bat}}{2 \alpha I_E} \cdot \frac{I_E}{n U_T} = \frac{U_{bat}}{2 n U_T} \approx 240$$

$$A_P = A_U \cdot A_I \approx 240 \cdot 0.9 = 216 \approx 23.3\text{dB} \equiv \text{power gain}$$

Common – base amplifier

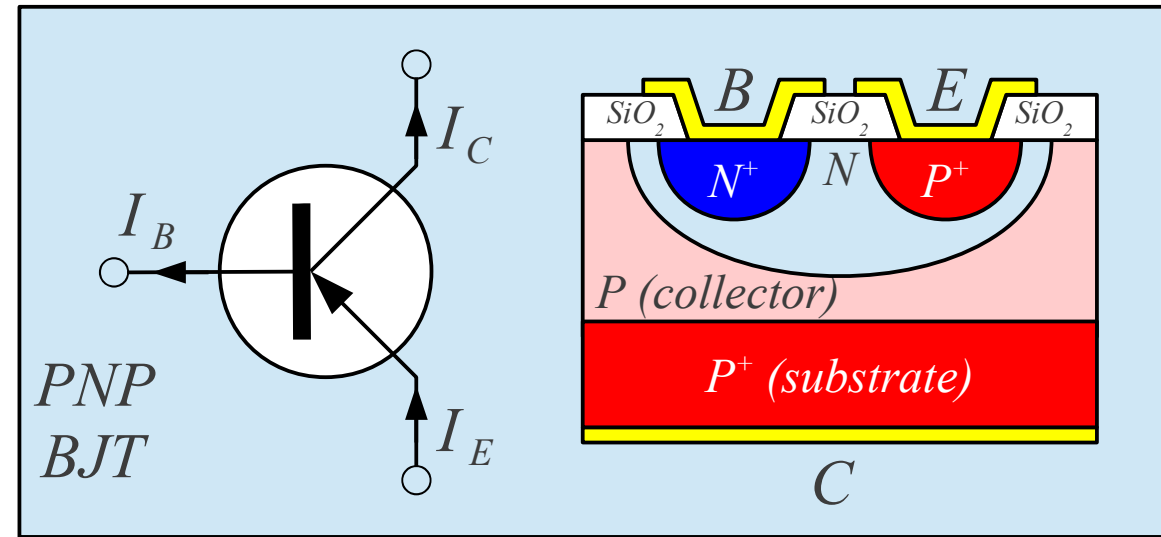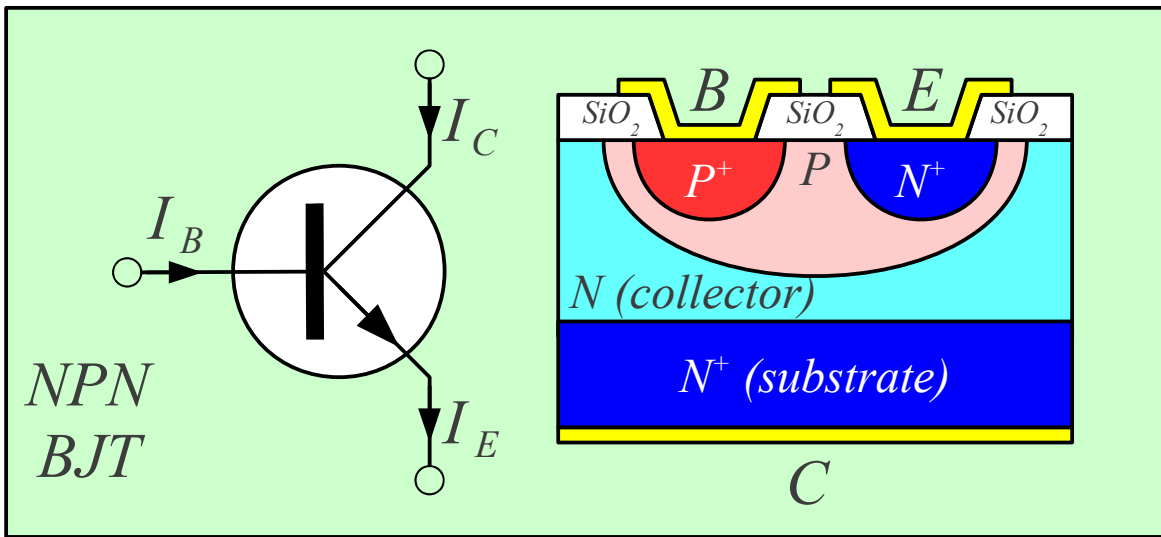

$$\frac{I_C}{I_B} = \beta \approx 250 \quad (30 \dots 1000) \equiv \text{common-emitter current gain}$$

Drawings not to scale

$$\beta = \frac{I_C}{I_B} = \frac{I_C}{I_E - I_C} = \frac{\alpha I_E}{I_E - \alpha I_E} = \frac{\alpha}{1 - \alpha} = \frac{1}{\frac{1}{\alpha} - 1} \leftrightarrow \alpha = \frac{1}{1 + \frac{1}{\beta}} \approx 0.996 \quad (0.98 \dots 0.999)$$

High $\beta \rightarrow$ emitter doping N^+ or $P^+ \gg$ base doping P or N



Planar silicon bipolar transistors

*BE reverse breakdown
3V ... 15V
long-term destructive !*

$$I_B = I_{SB} \left(e^{\frac{u_{BE}}{nU_T}} - 1 \right)$$


$$I_C = \beta I_B$$

$$R_d = \frac{nU_T}{I_B}$$

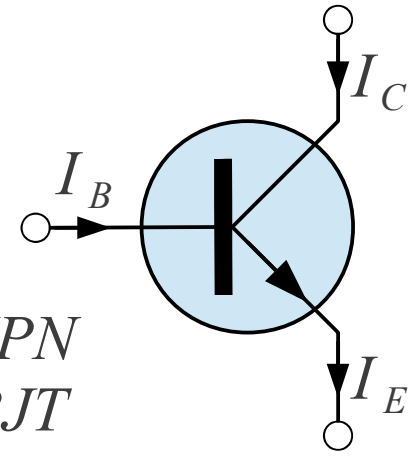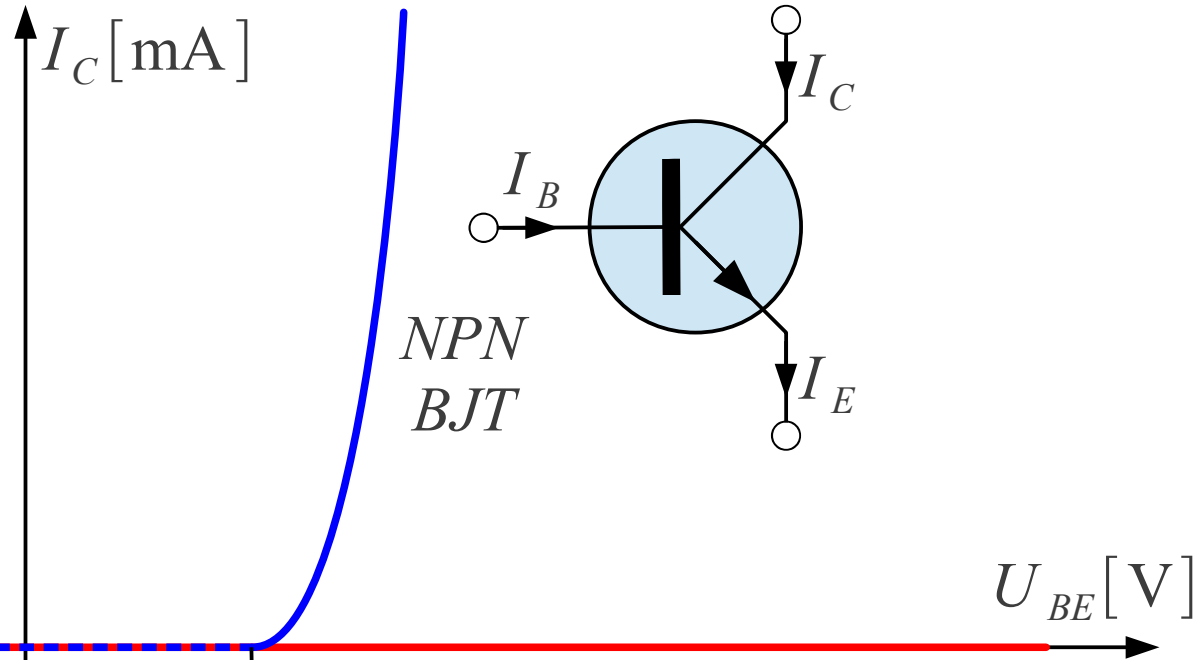

$\sim -0.6V$
Si-PNP

$\sim +0.6V$
Si-NPN

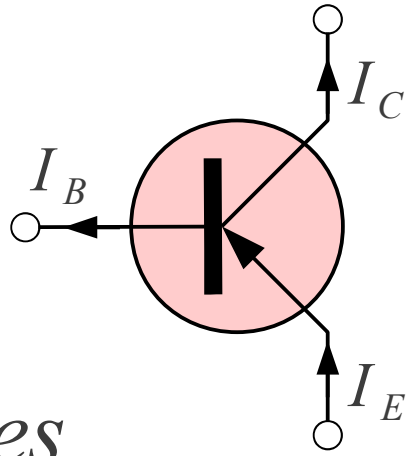


PNP BJT

$$n \approx 1 \quad U_T = \frac{k_B T}{|Q_e|} \approx 25mV$$

BJT curves

$$A_I = \frac{d I_C}{d I_B} = \beta \approx 250 \equiv \text{current gain}$$

$$n \approx 1 \quad U_T = \frac{k_B T}{|Q_e|} \approx 25\text{mV}$$

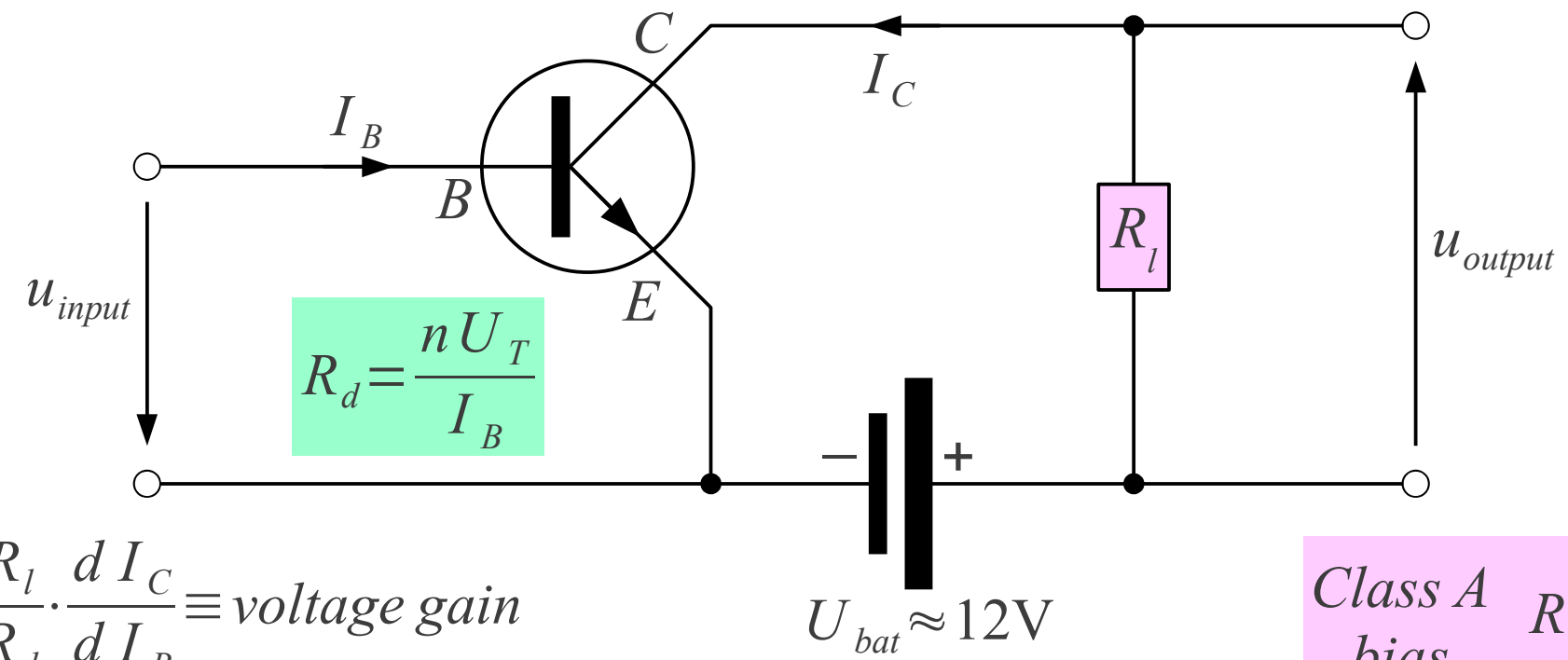

$$A_U = \frac{d u_{output}}{d u_{input}} = \frac{R_l}{R_d} \cdot \frac{d I_C}{d I_B} \equiv \text{voltage gain}$$

$$\text{Class A bias} \quad R_l \approx \frac{U_{bat}/2}{I_C}$$

$$A_U \approx \frac{U_{bat}}{2 I_C} \cdot \frac{I_B}{n U_T} \cdot \beta = \frac{U_{bat}}{2 n U_T} \approx 240$$


$$A_P = A_U \cdot A_I \approx 240 \cdot 250 = 60000 \approx 47.8\text{dB} \equiv \text{power gain}$$

Common-emitter amplifier

$$A_I = \frac{d I_E}{d I_B} = \beta + 1 \approx 251 \equiv \text{current gain}$$

$$n \approx 1 \quad U_T = \frac{k_B T}{|Q_e|} \approx 25\text{mV}$$
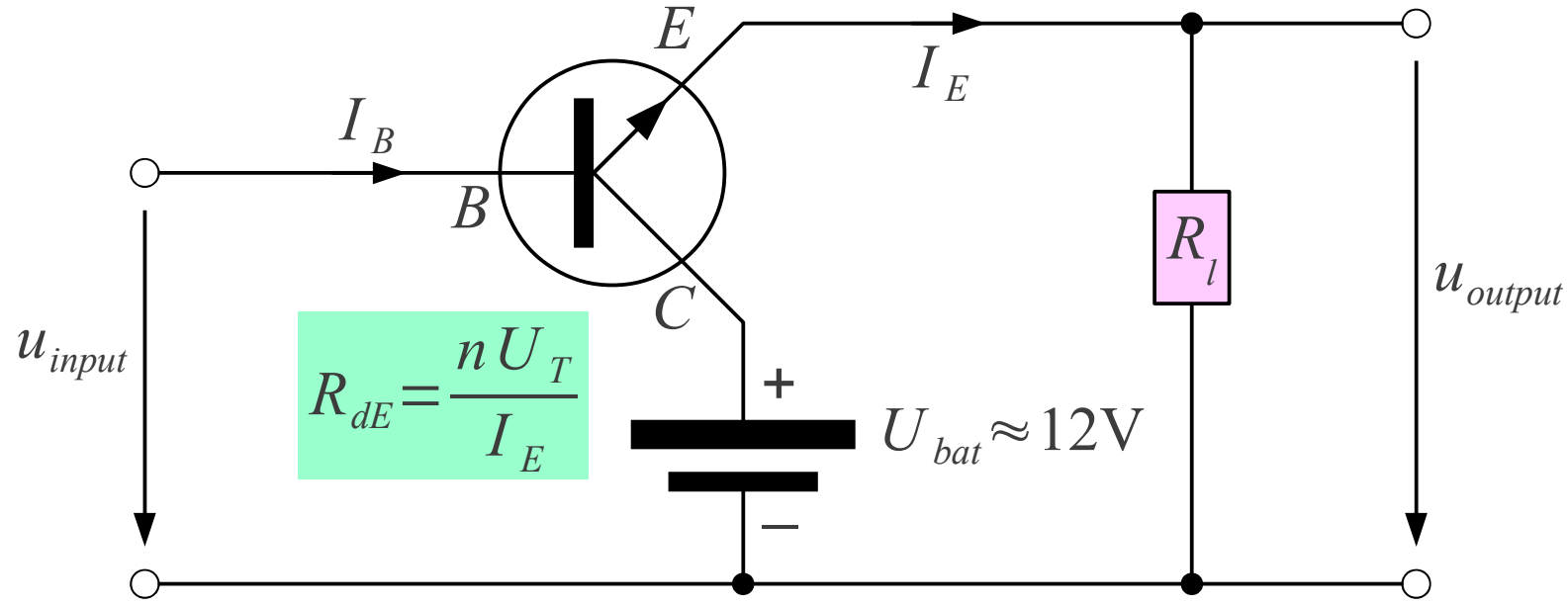
$$\text{Class A bias} \quad R_l \approx \frac{U_{bat}/2}{I_E}$$





$$A_U = \frac{d u_{output}}{d u_{input}} = \frac{R_l}{R_{dE} + R_l} \equiv \text{voltage gain}$$

$$A_P = A_U \cdot A_I \approx 0.996 \cdot 251 \approx 250 \approx 24.0\text{dB} \equiv \text{power gain}$$


$$A_U = \frac{1}{\frac{R_{dE}}{R_l} + 1} = \frac{1}{\frac{2nU_T}{U_{bat}} + 1} \approx \frac{1}{\frac{1}{240} + 1} \approx 0.996$$

Emitter follower


Bias
 $R_b \approx 2\beta R_l$

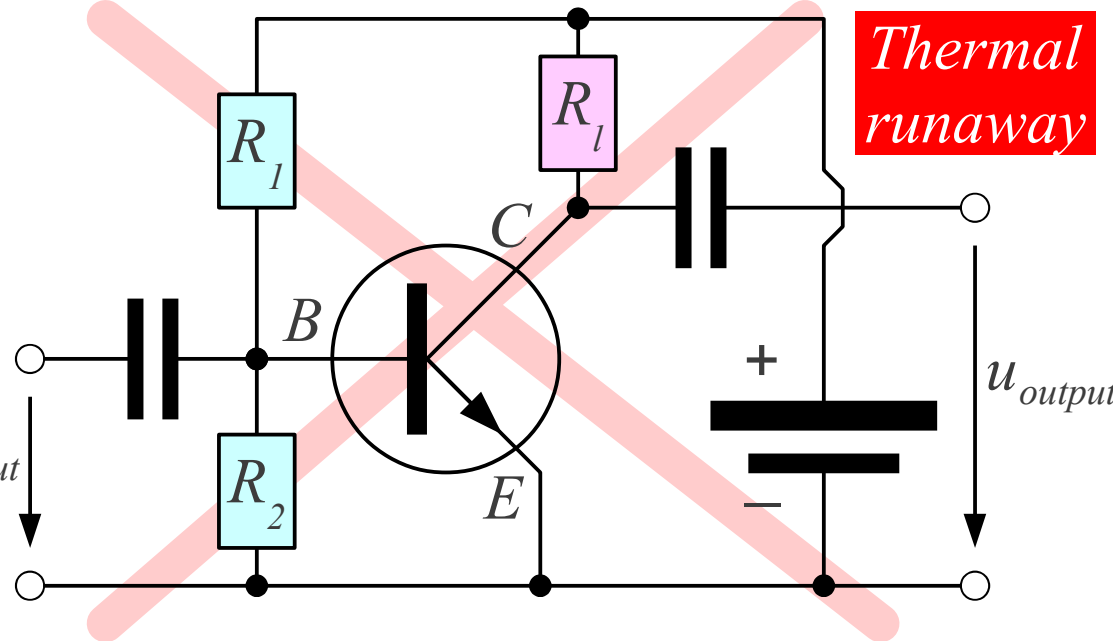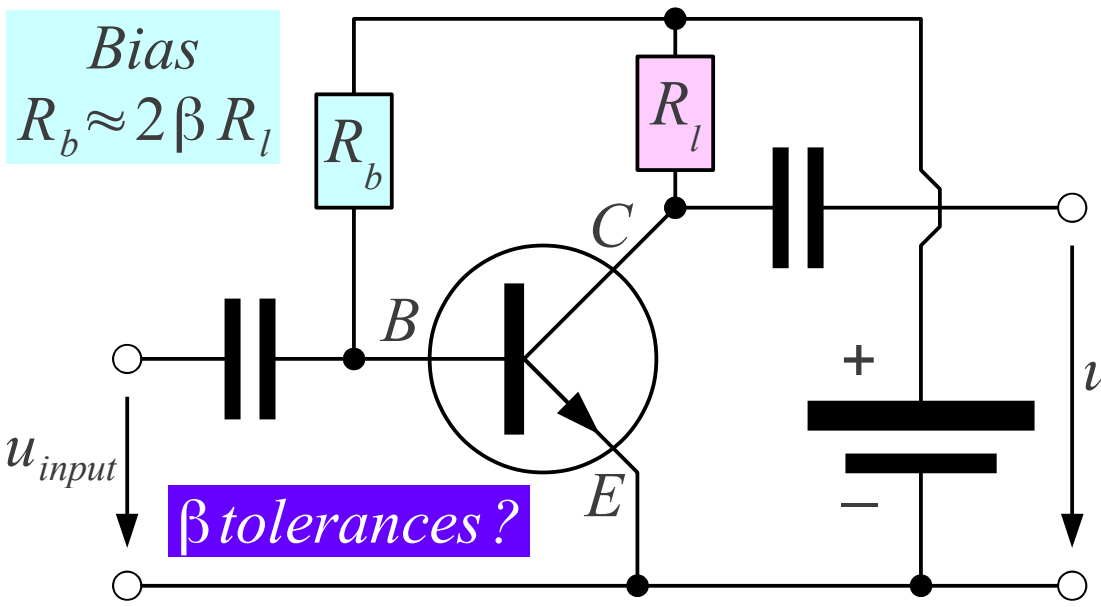


Feedback
 $R_f \approx \beta R_l$

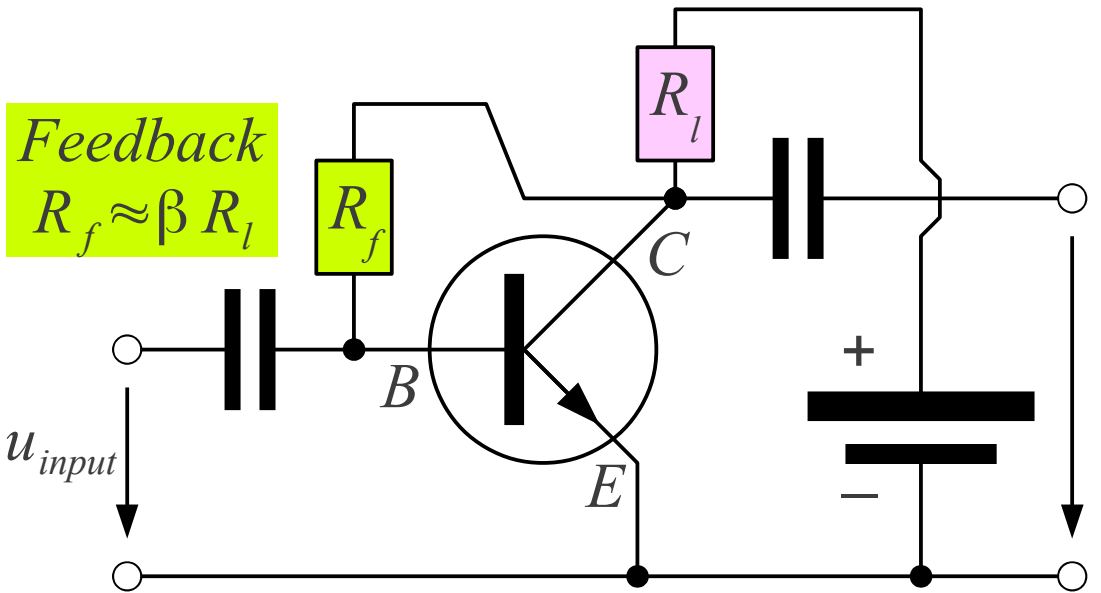


Common-emitter bias

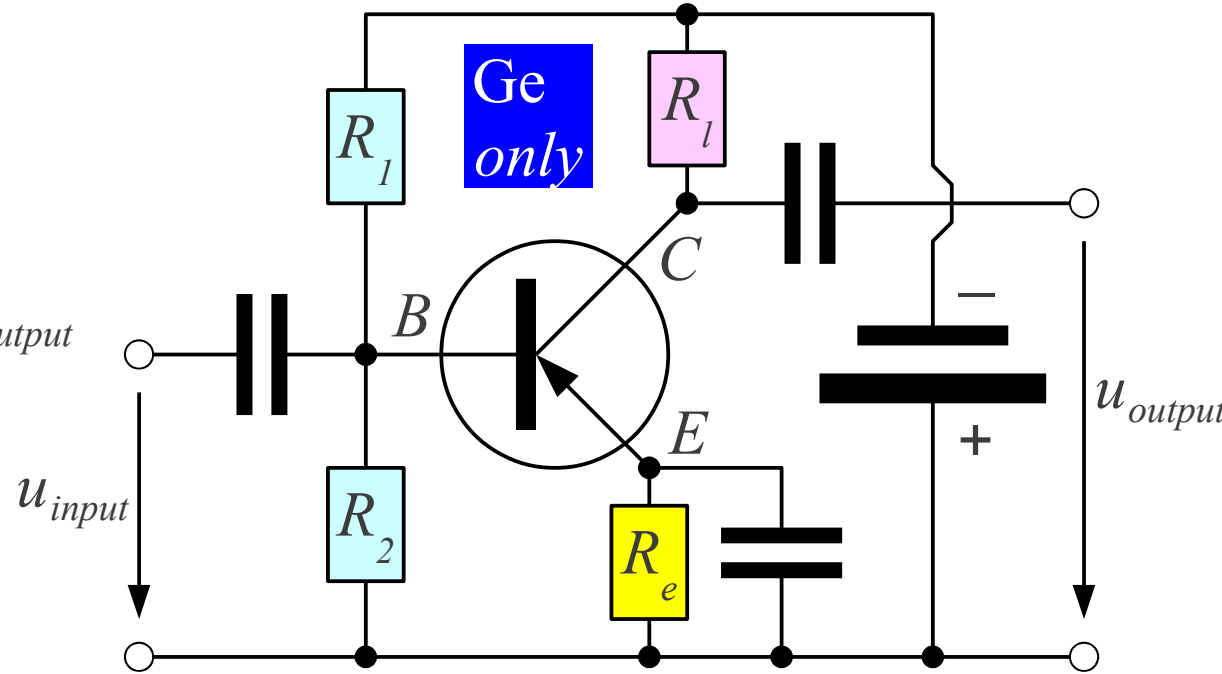

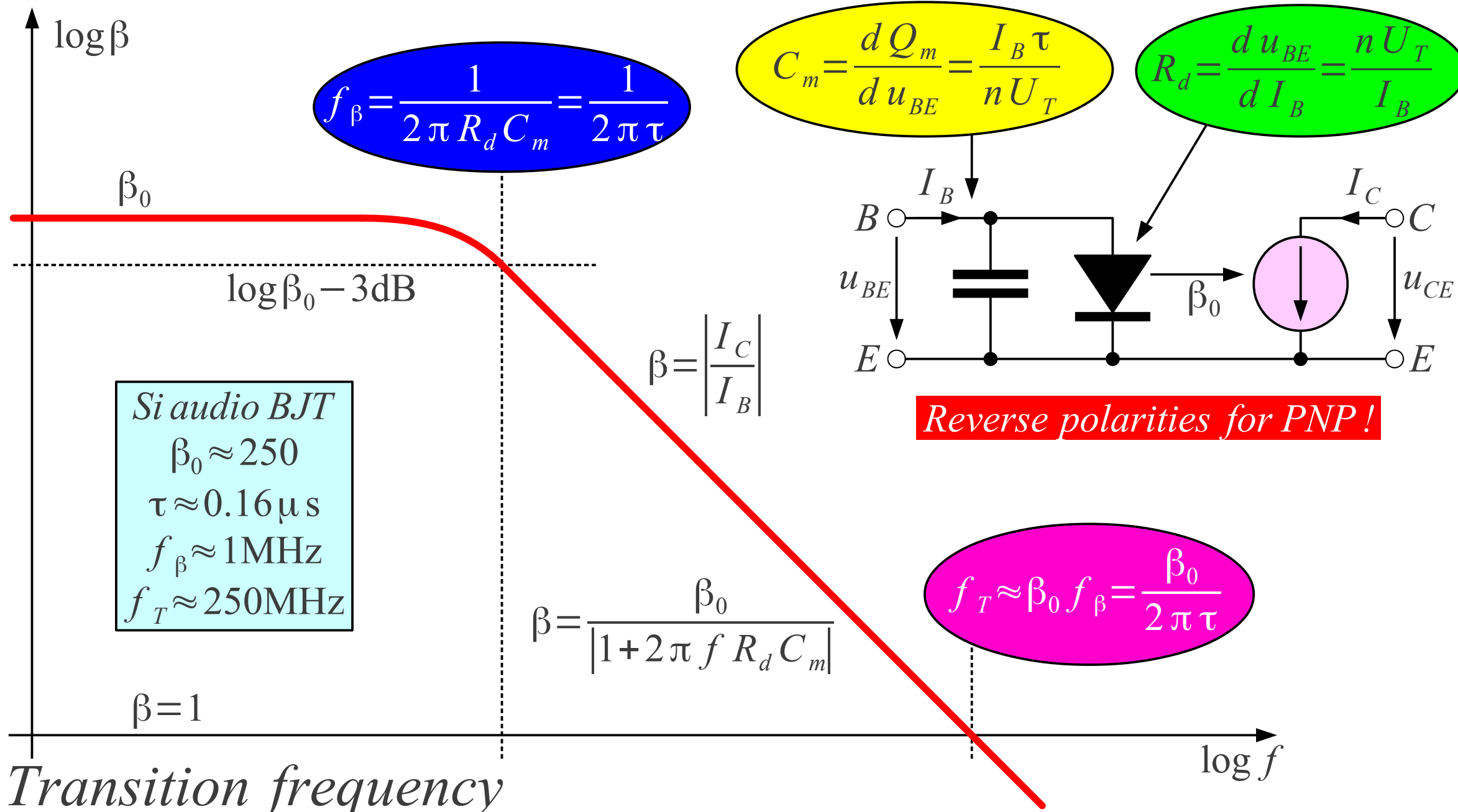



Drawings not to scale

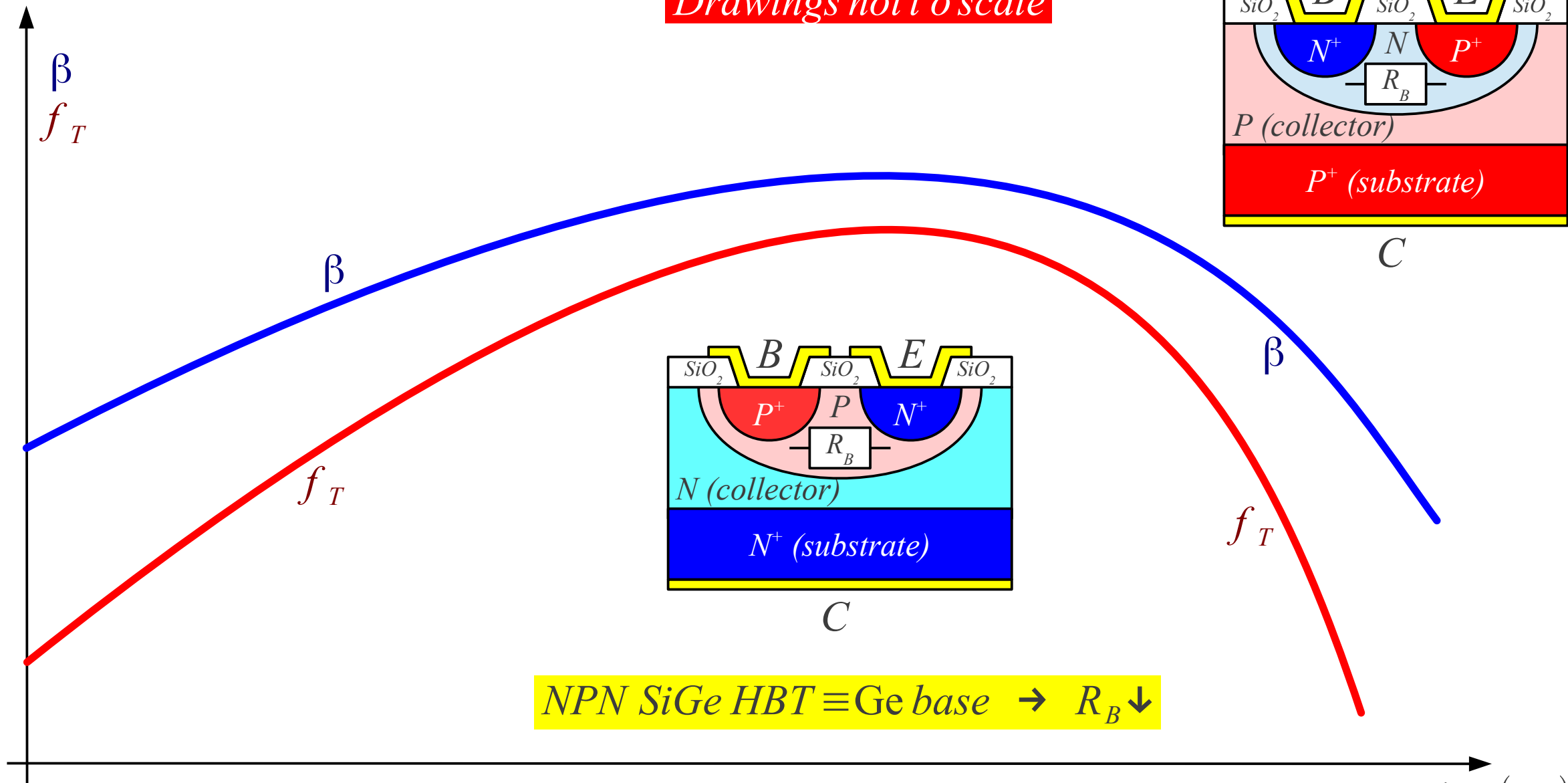

Effects of base resistance

$\log(I_C)$

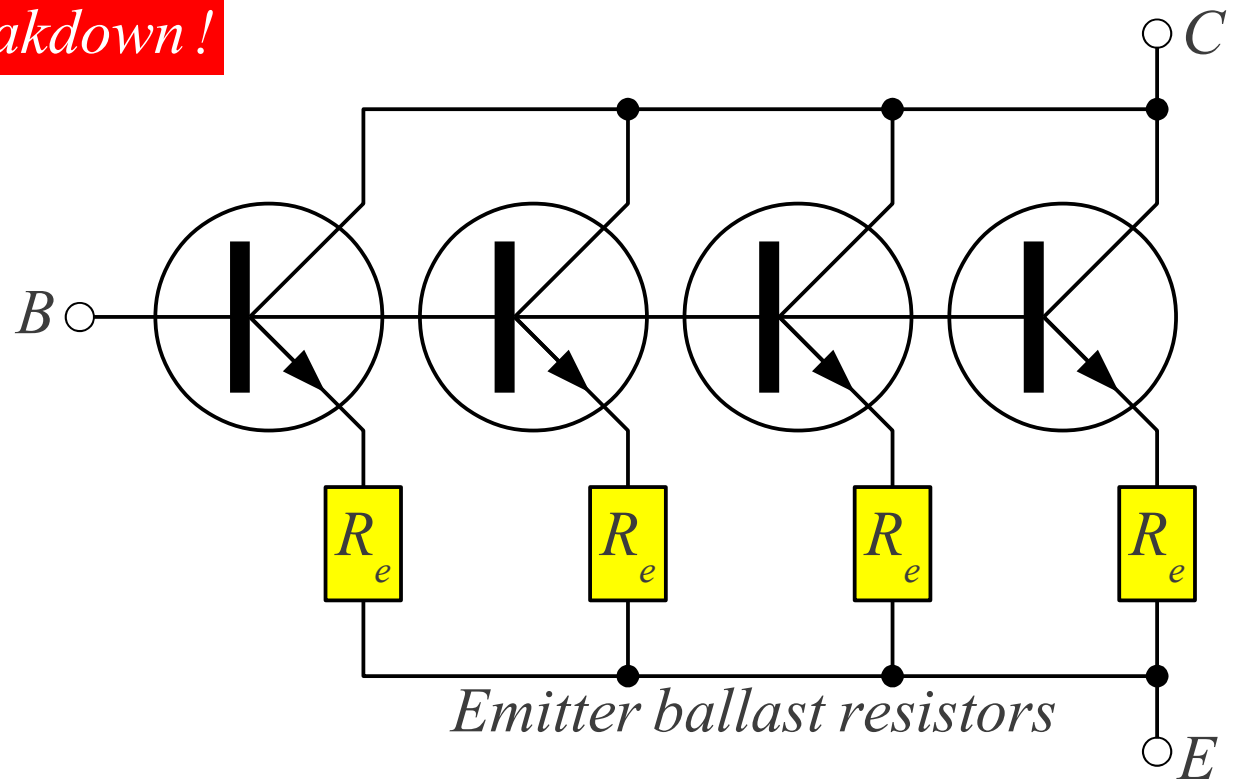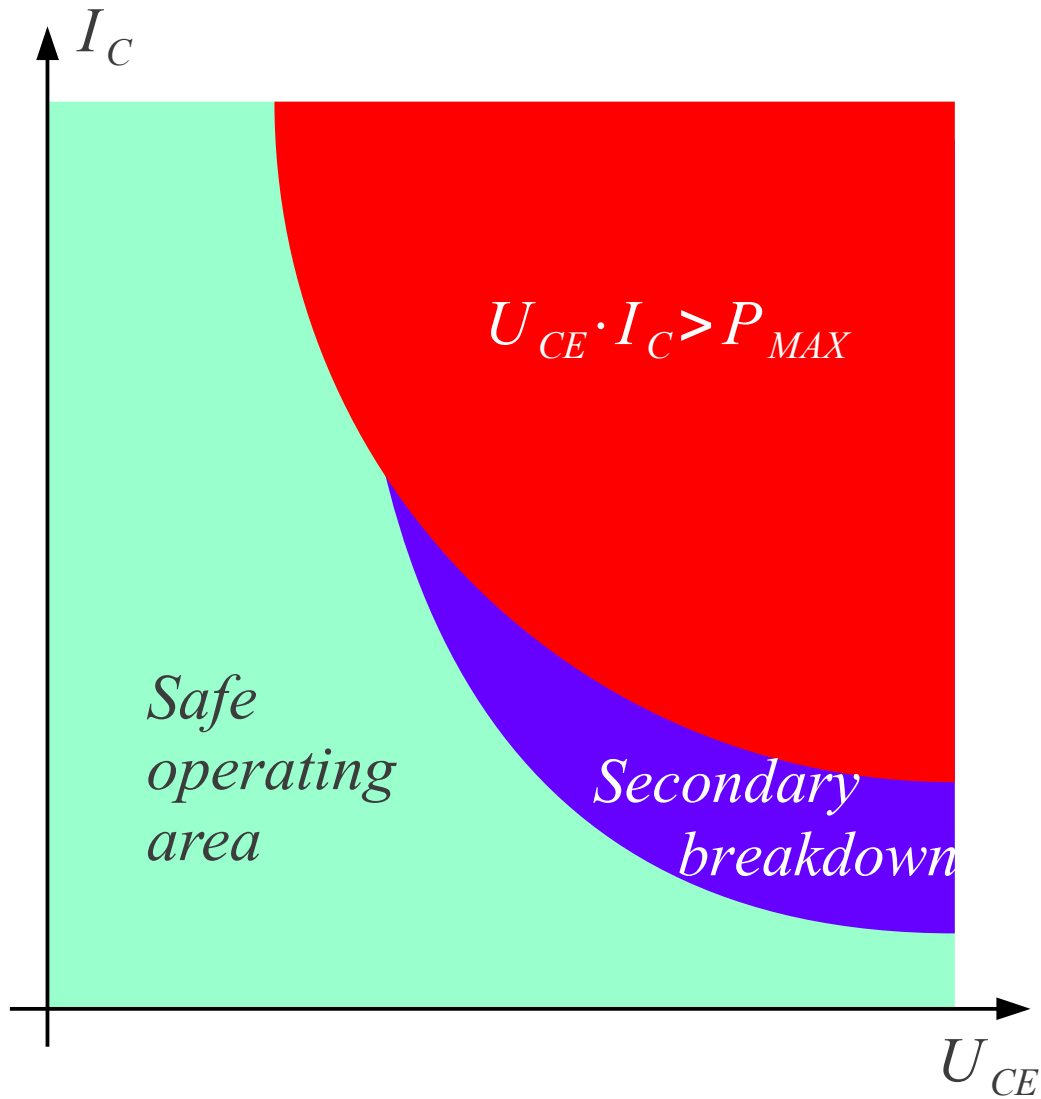$U_{BE} \quad TC < 0 \rightarrow \text{Secondary breakdown!}$




<i>RF transistors $f \sim 1\text{GHz}$</i>	
<i>Small-signal</i>	<i>Power $\sim 10\text{W}$</i>
<i>~ 10 emitters</i>	<i>~ 1000 emitters</i>

Secondary breakdown

RF power transistor


Drawing not to scale

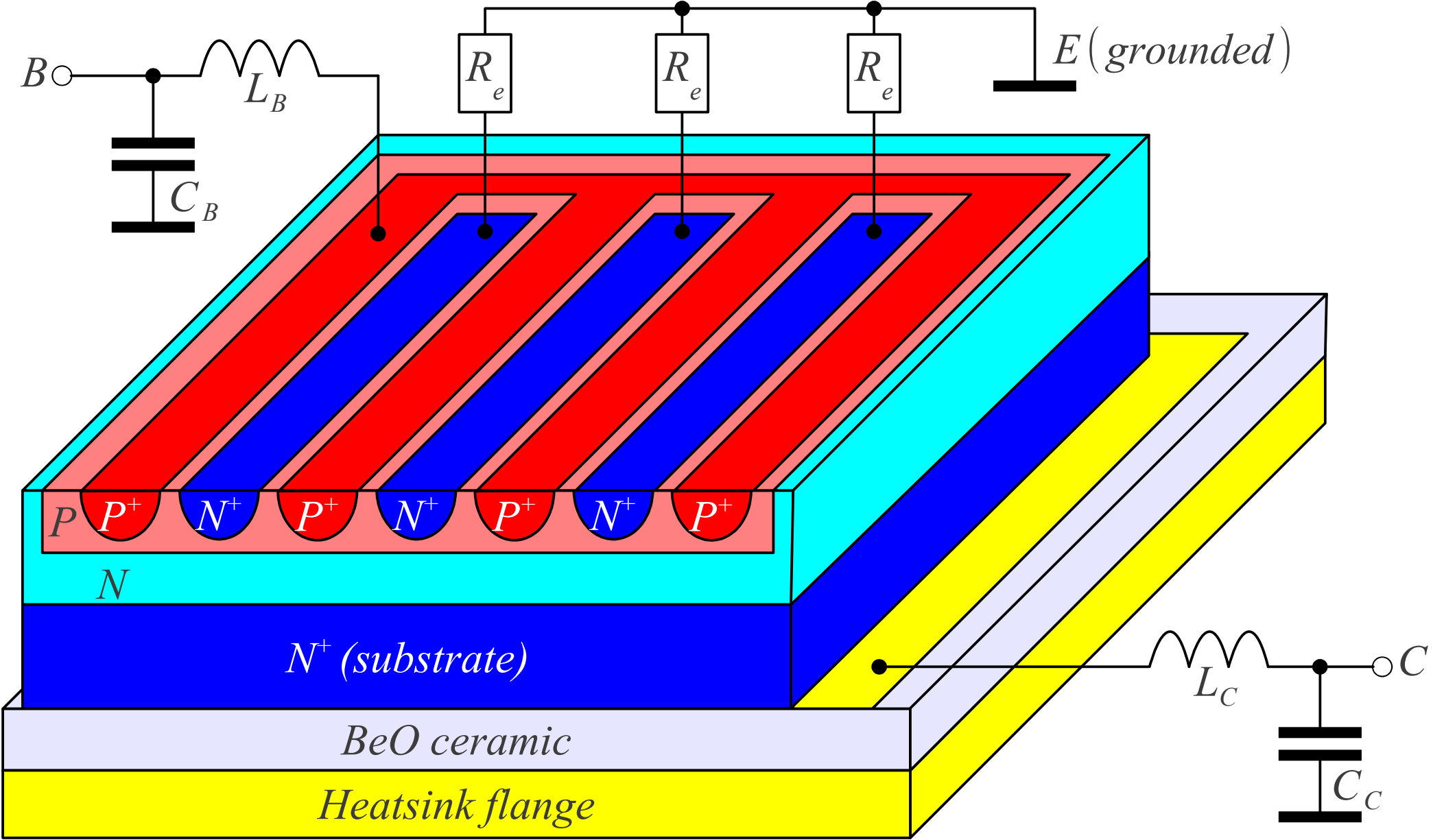

1970: $l_{channel} \approx 10 \mu m \rightarrow f \approx 100 MHz$


2020: $l_{channel} \approx 10 nm \rightarrow f \approx 100 GHz$

Si N-channel JFET

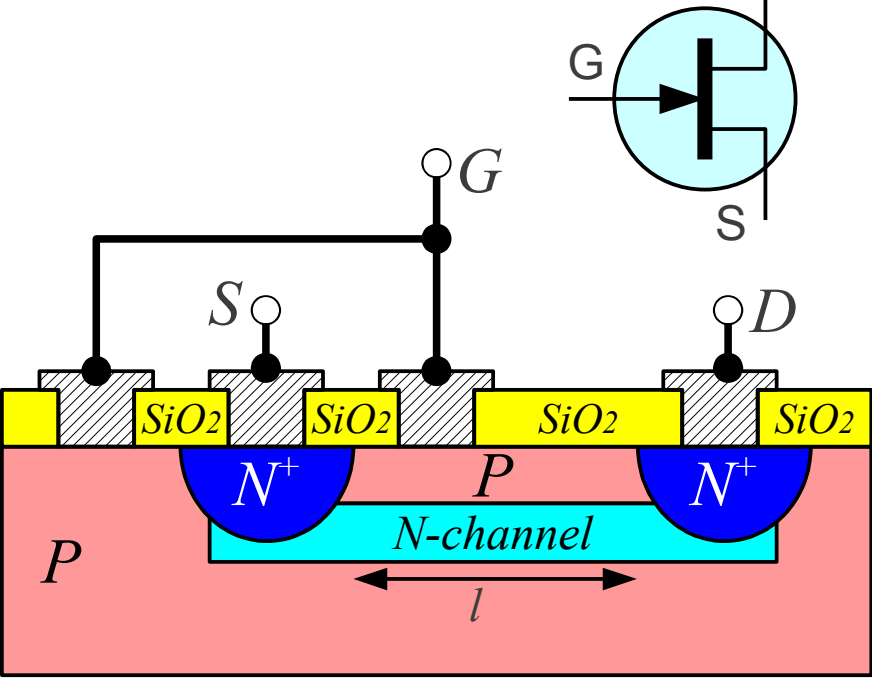

Field-effect transistors


Si MOSFET N-channel

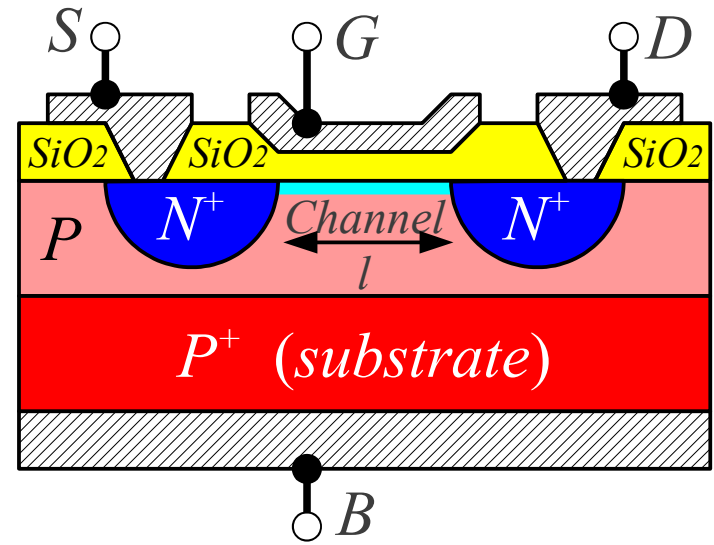


Small-signal transistors

Drawings not to scale


Si MOSFET P-channel

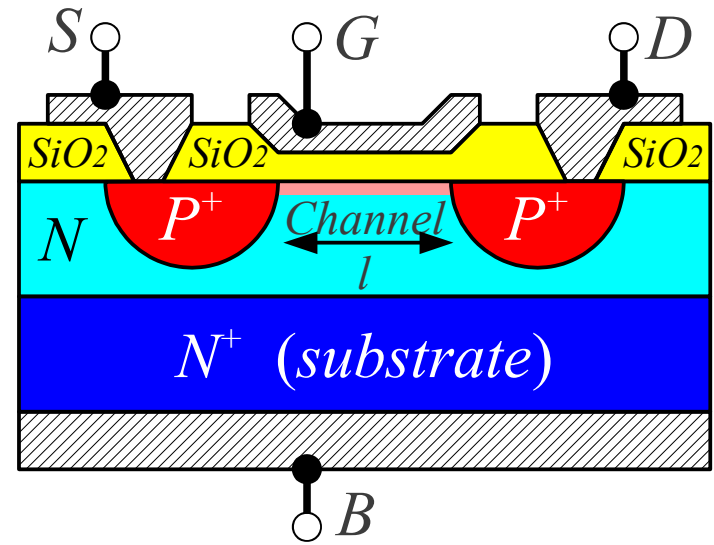


$I_D \neq 0 @ u_{gs} > U_P$

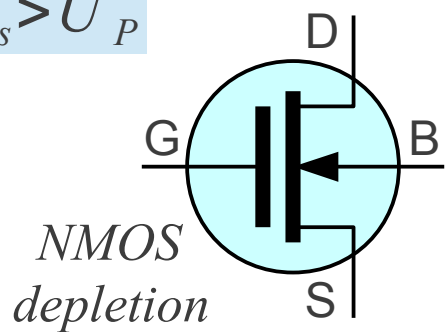

NMOS depletion

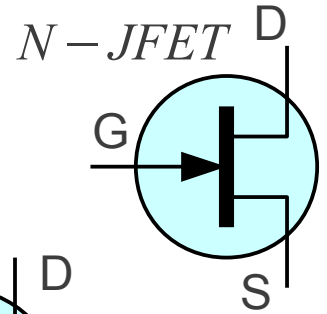


N-JFET

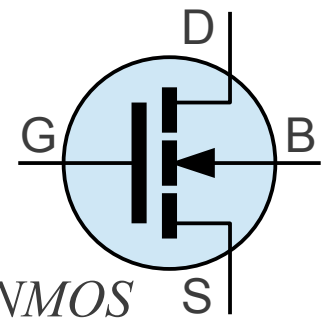


NMOS enhancement

$I_D = \pm k (u_{GS} - U_P)^2$

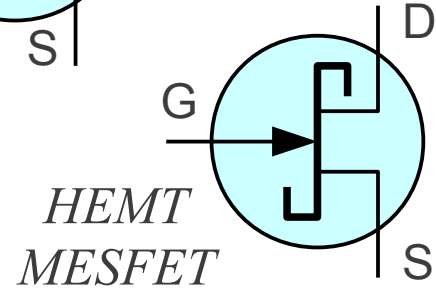


HEMT MESFET

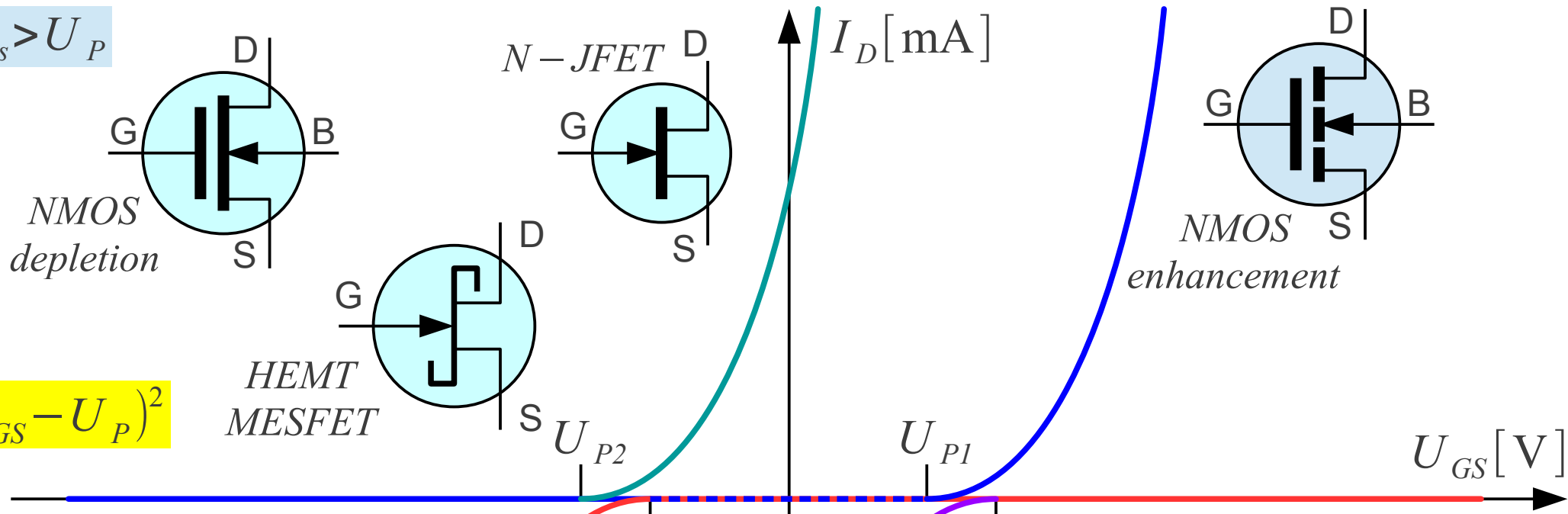


Si: $\mu_N \approx 3\mu_P$


$I_D \neq 0 @ u_{gs} < U_P$

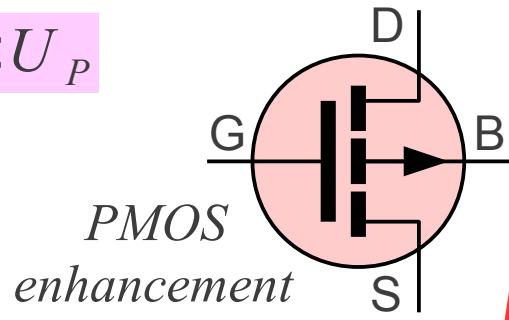

PMOS enhancement

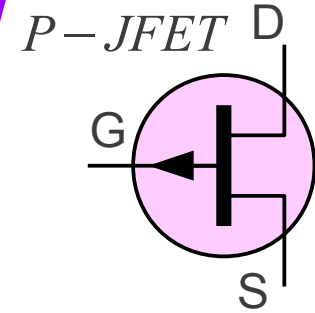




P-JFET

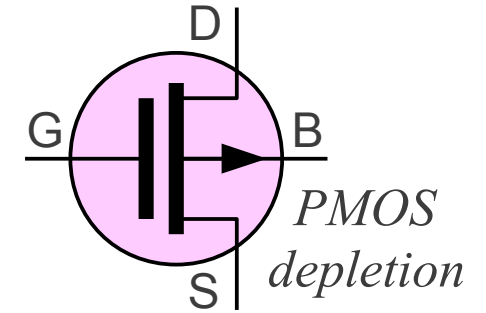

PMOS depletion

FET transfer curves


Reverse polarities for P channel !

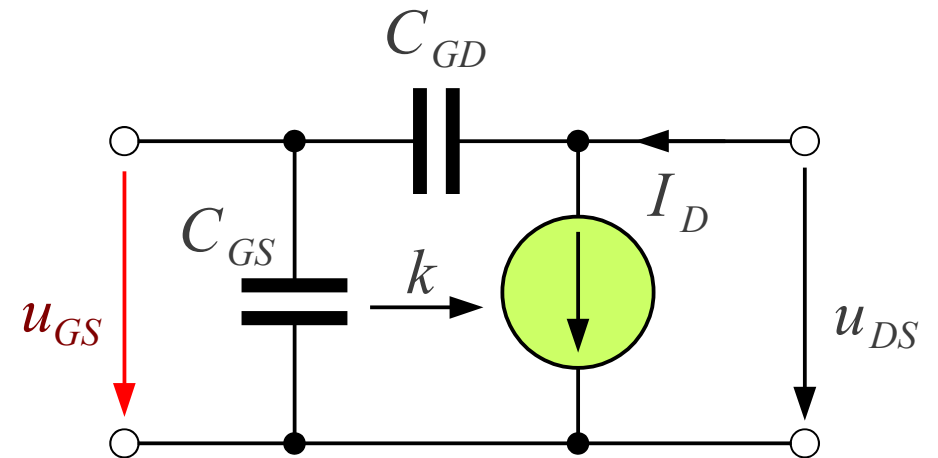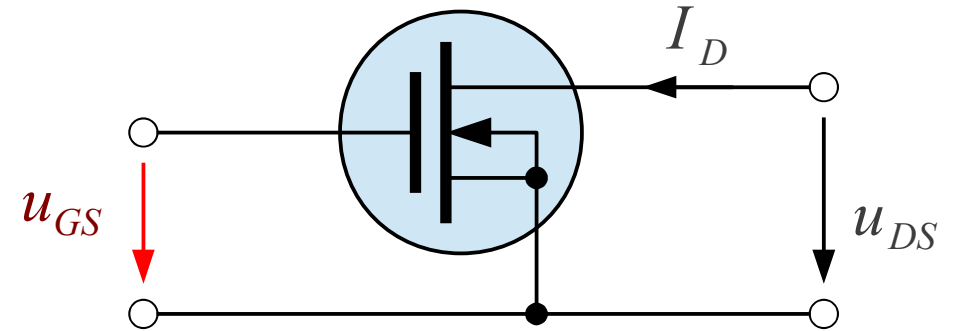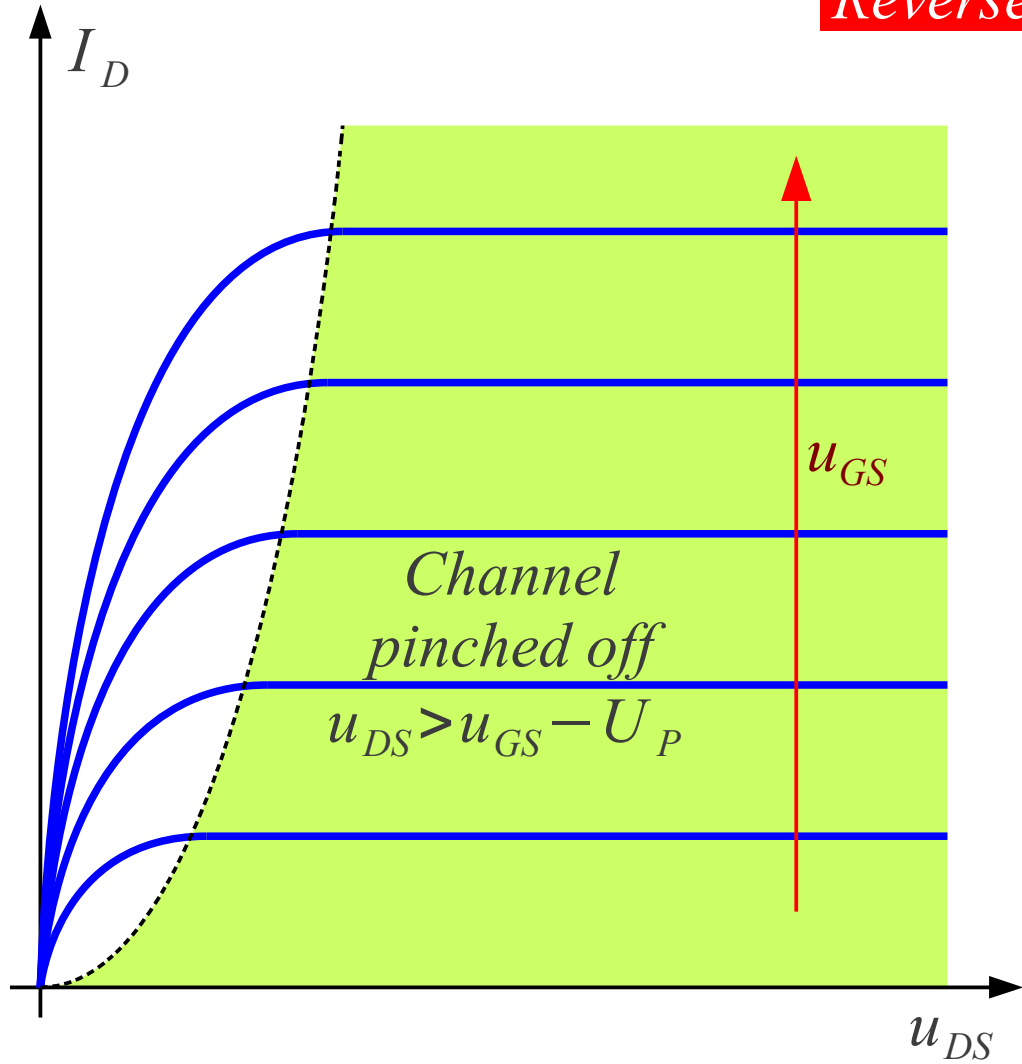


FET output curves

Drawings not to scale


VMOS

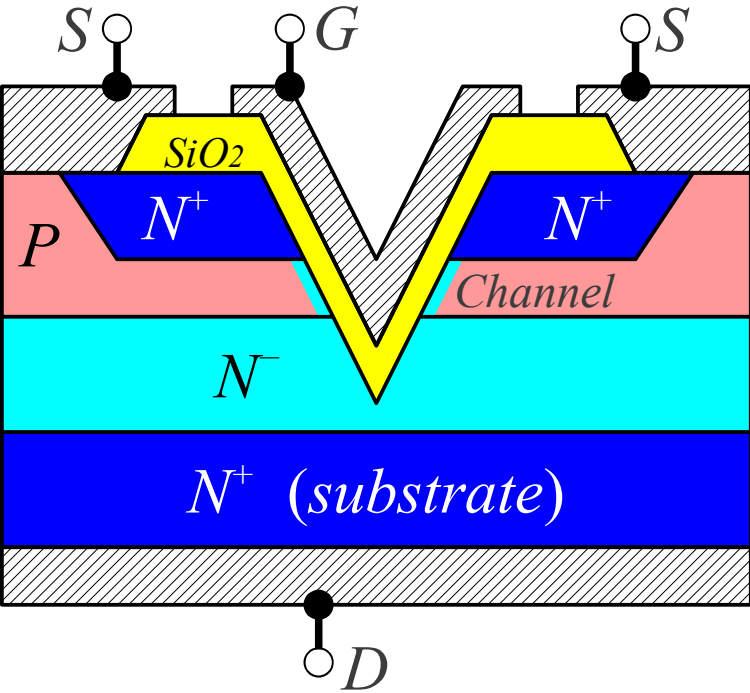

Power MOSFETs

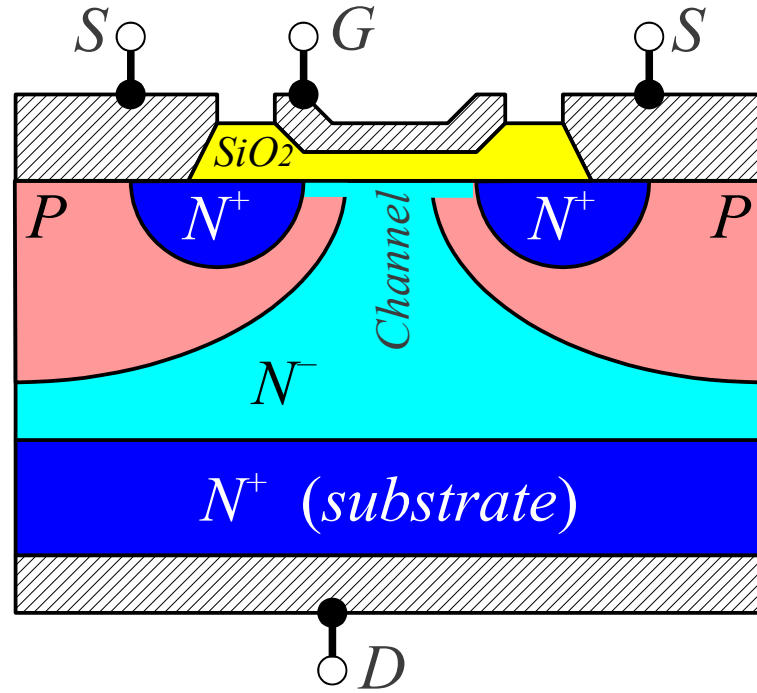


Power MOS

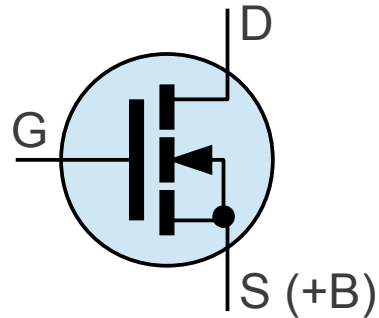



$R_{channel} \quad TC > 0 \rightarrow$
NO secondary breakdown!

*|| operation of
thousands of transistors*

RF LDMOS

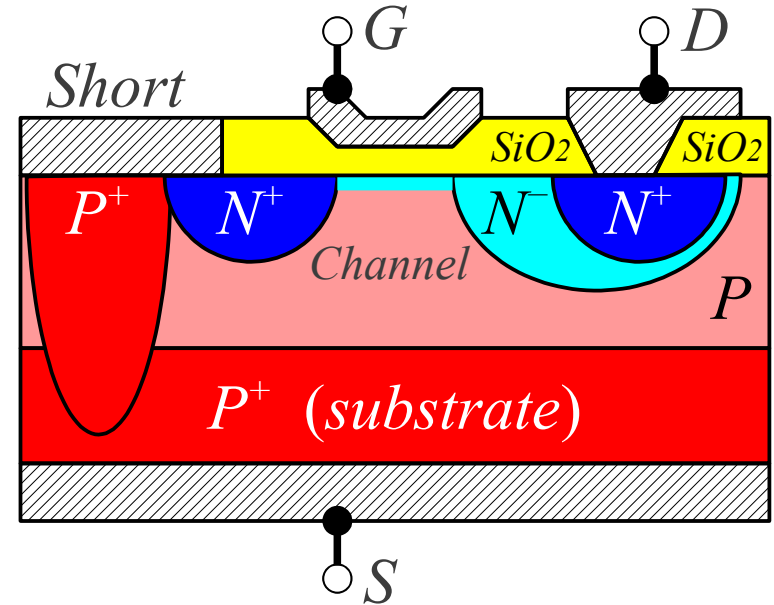

Side effects of protection diodes ?

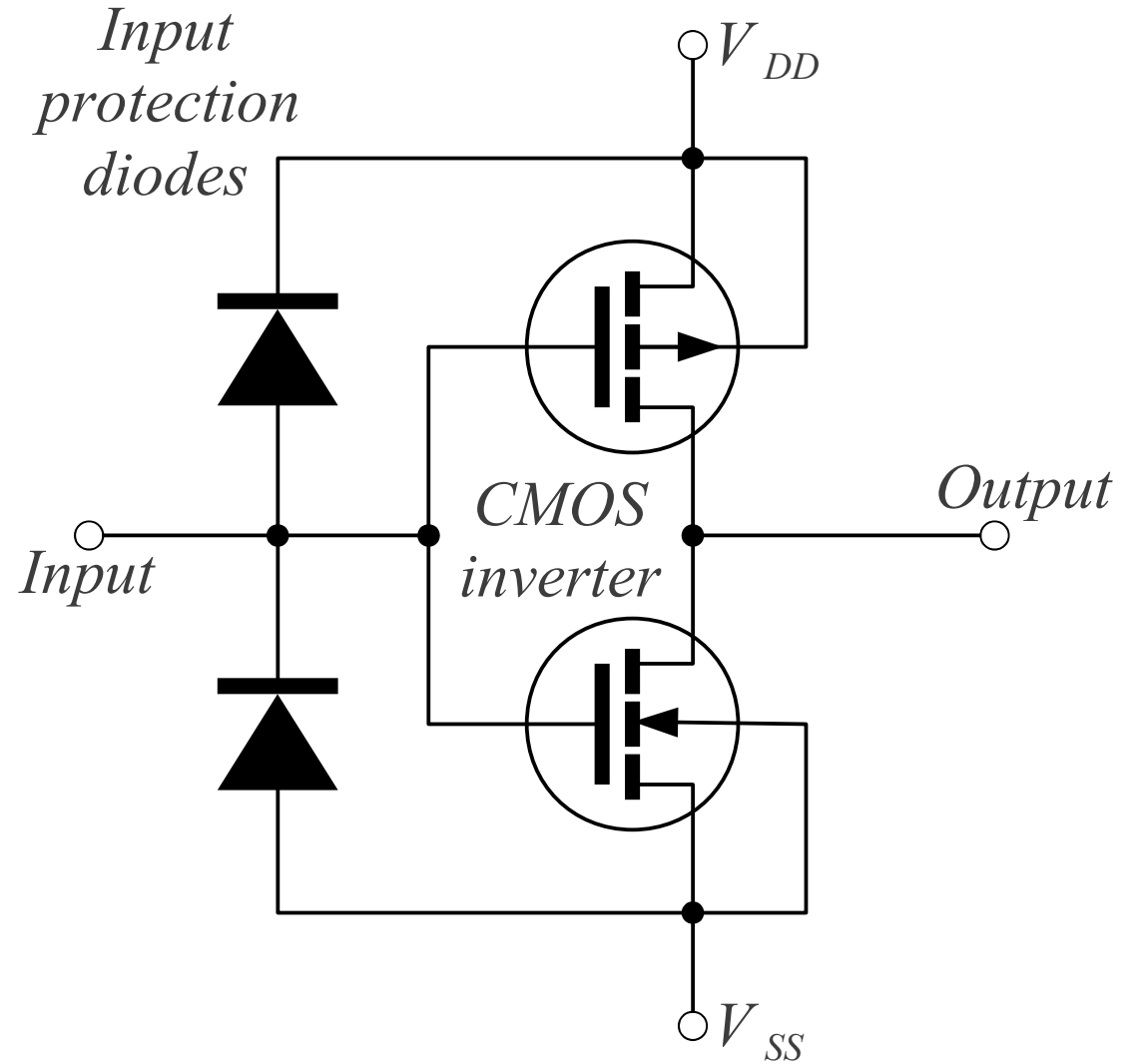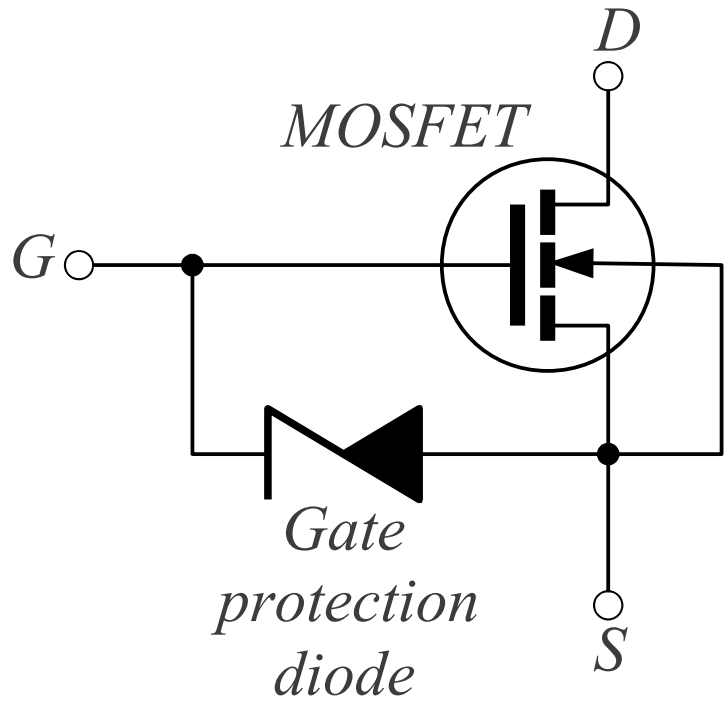


MOSFET protection diodes

$$\mu_N \approx 5000 \text{ cm}^2/\text{Vs}$$

$$l \leq 1 \mu\text{m}$$
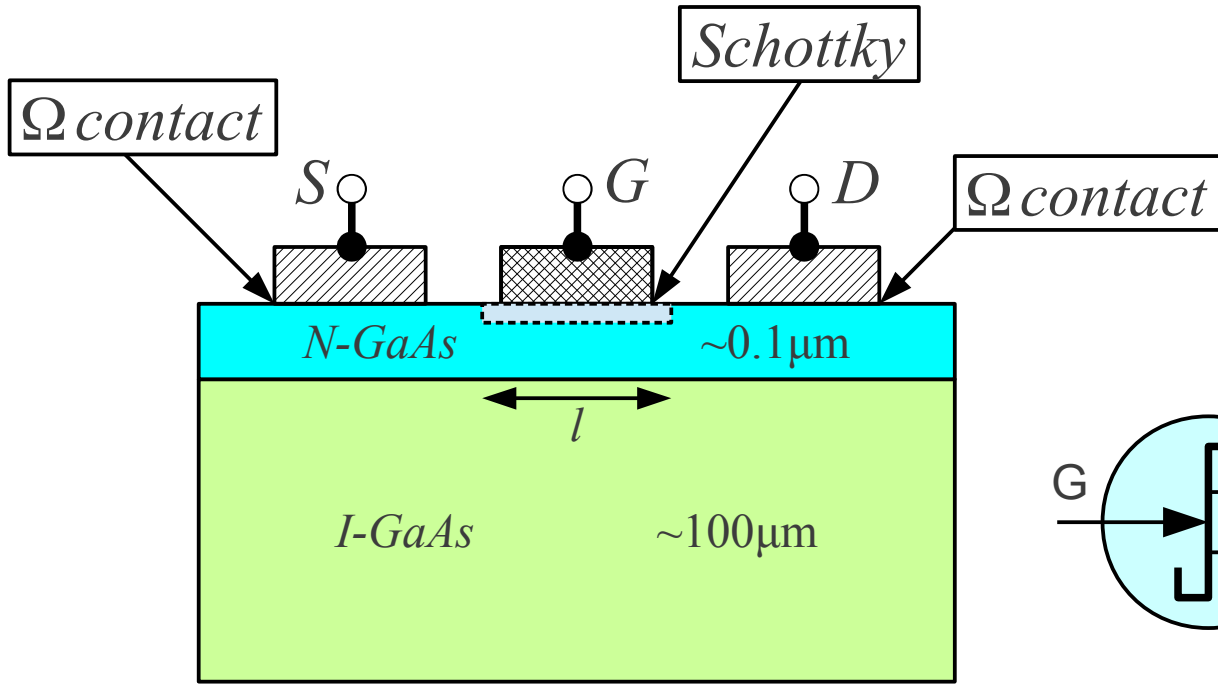
$$f \approx 10 \text{ GHz} \cdot \frac{1 \mu\text{m}}{l_{\text{channel}}}$$






$$U_P \approx -2\text{V}$$

$$U_{DS} \approx 5\text{V}$$

Drawings not to scale

GaAs MESFET

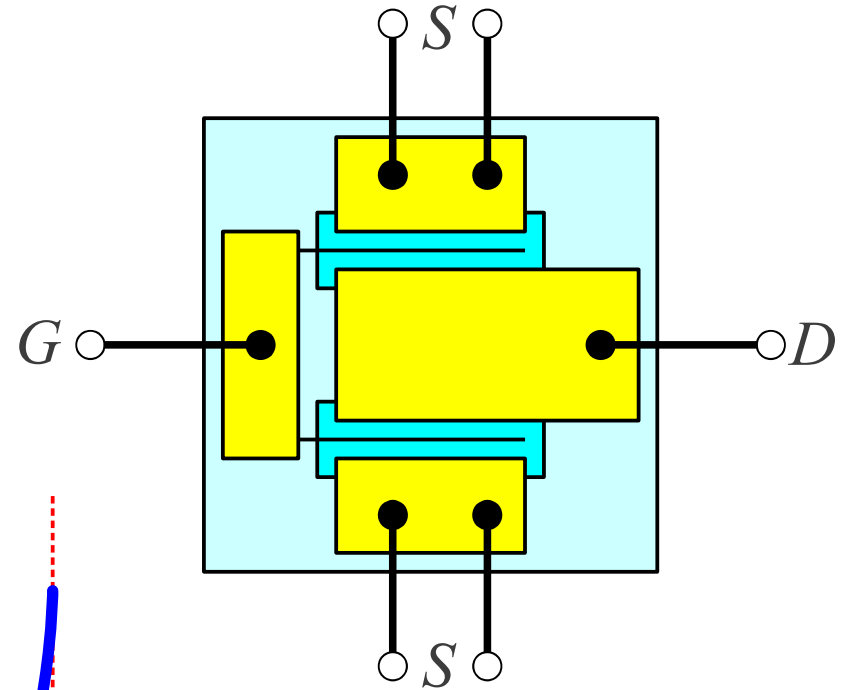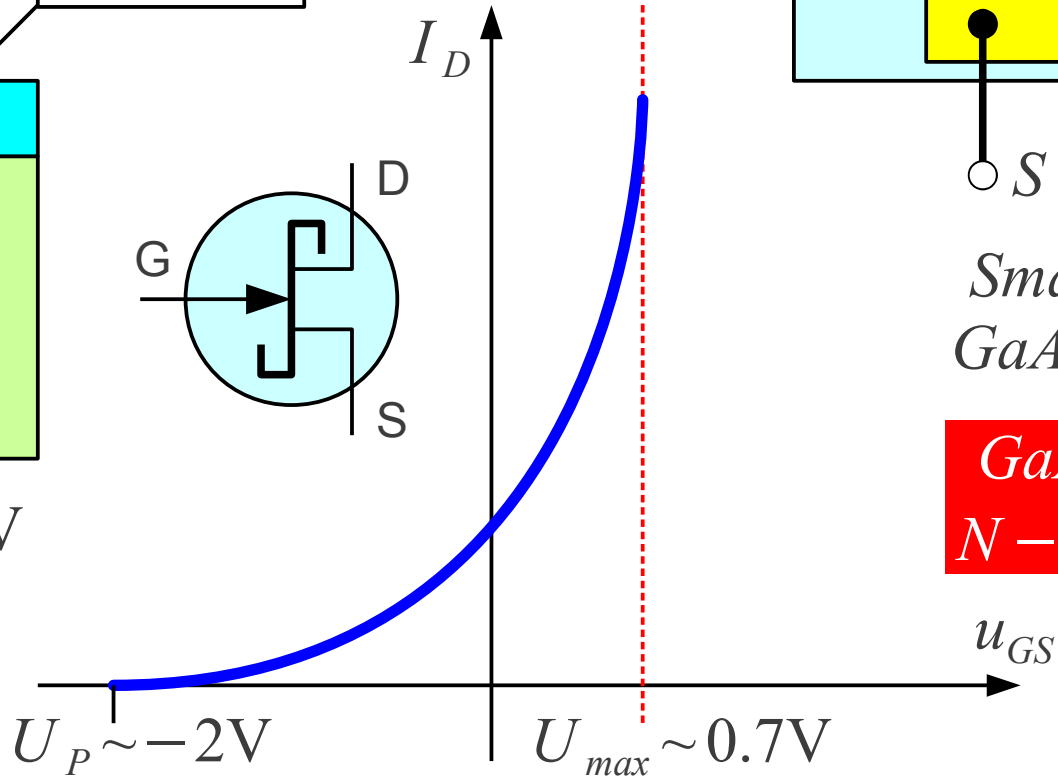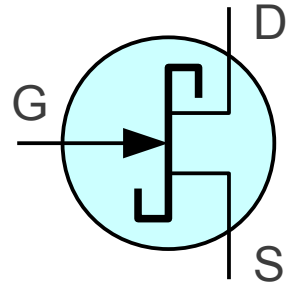


*Small-signal
GaAs MESFET*

*GaAs: $\mu_N \gg \mu_P$
N-channel only!*

$$\mu_N \approx 50000 \text{ cm}^2/\text{Vs}$$

$$l \leq 0.5 \mu\text{m}$$

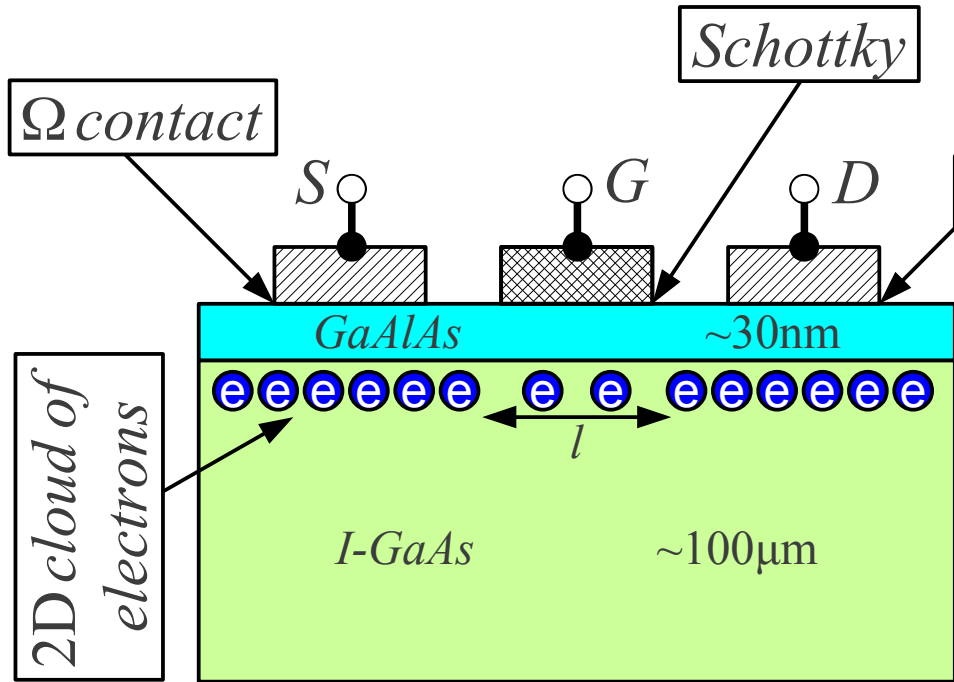


$$U_P \approx -1\text{V}$$

$$U_{DS} \approx 2\text{V}$$


Drawings not to scale

GaAlAs HEMT

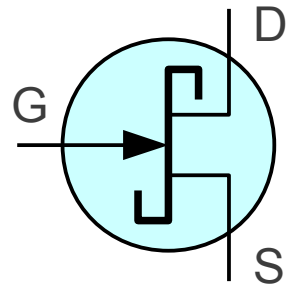


MESFET

HEMT

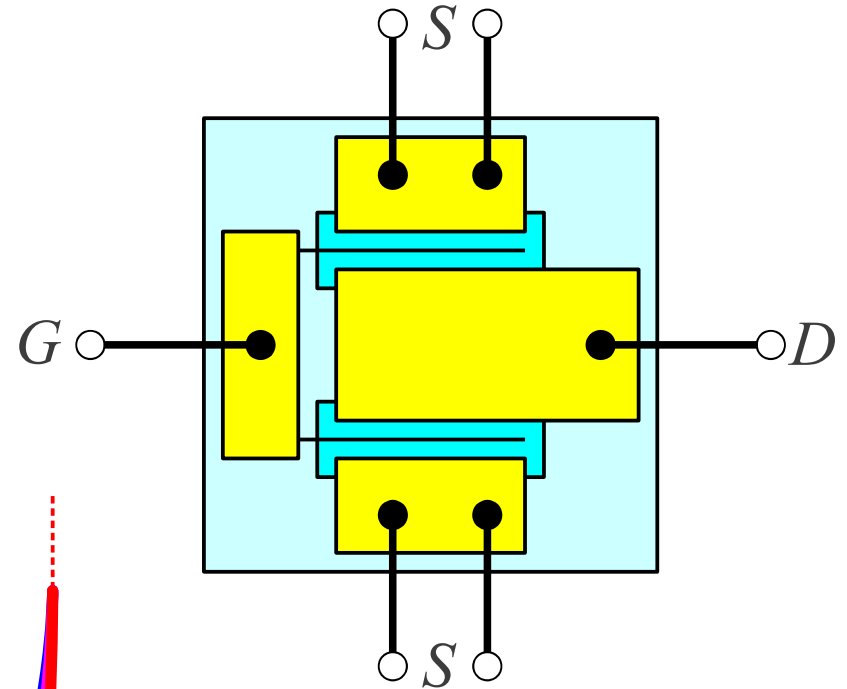

*Small-signal
GaAlAs/GaAs HEMT*


E-HEMT

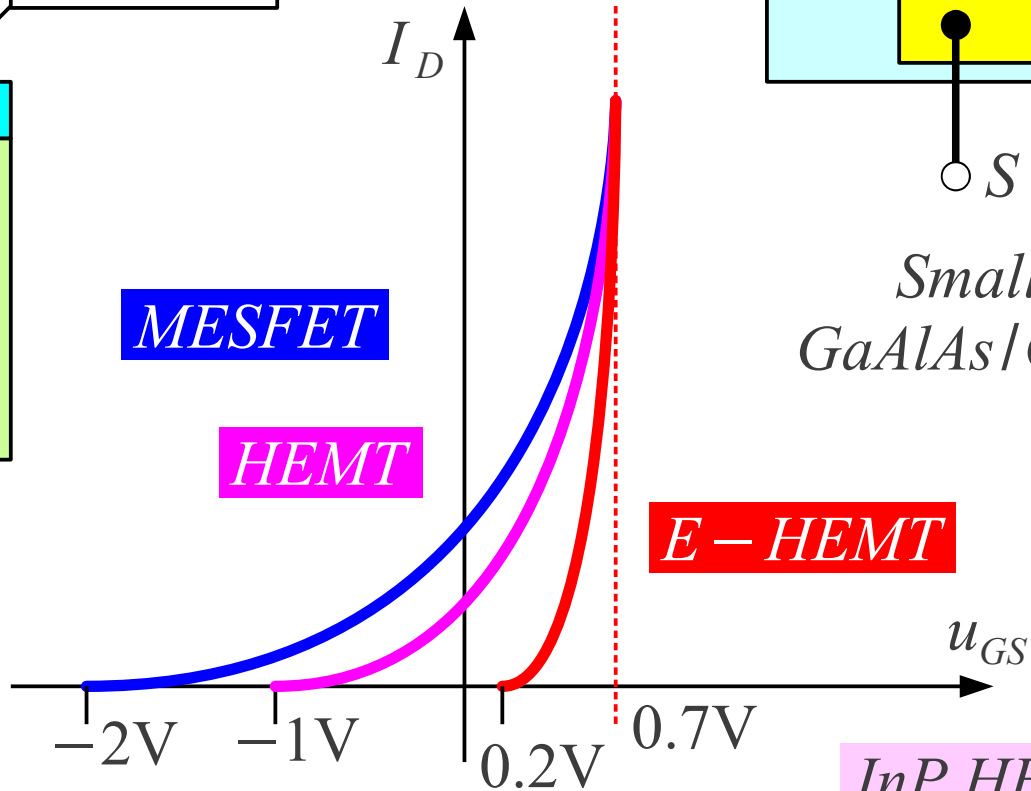



InP HEMT $f \approx 1\text{THz}$

Drawings not to scale

$l \leq 0.5 \mu\text{m}$

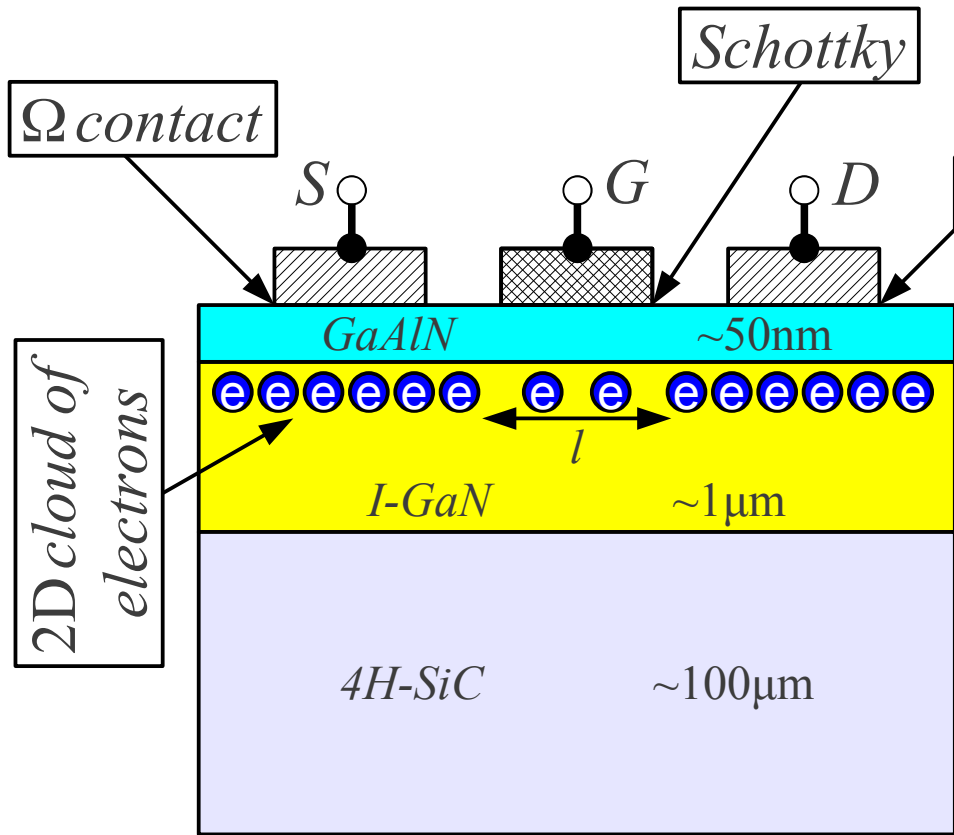

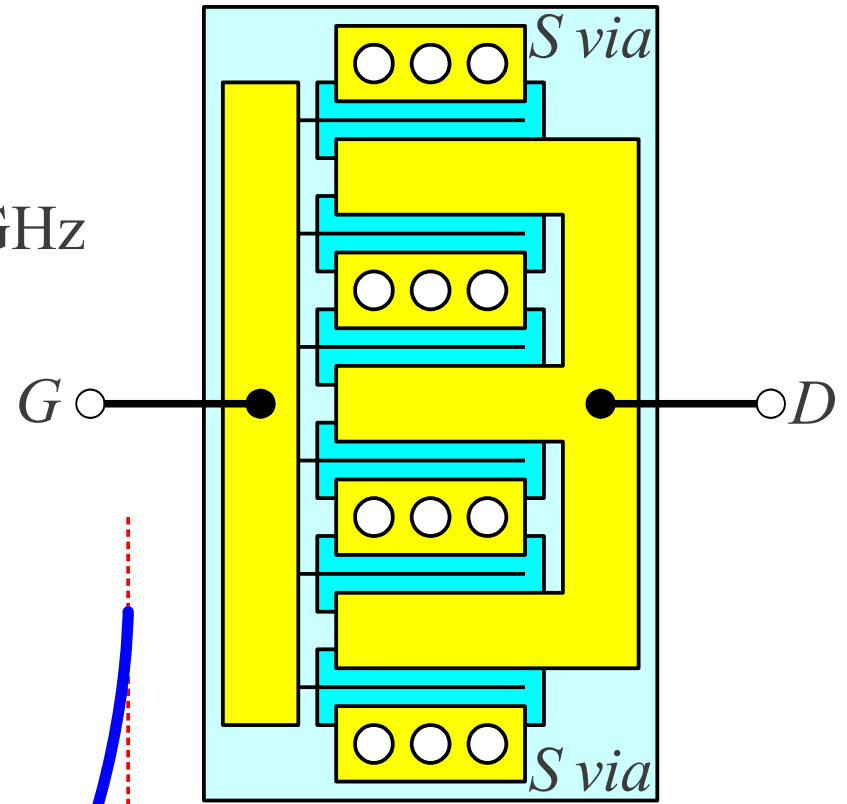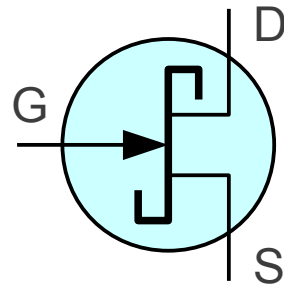$P_{out} \approx 100\text{W} @ 10\text{GHz}$



Power
GaAlN / GaN HEMT

$\text{GaN} : \mu_N \gg \mu_P$
N-channel only!

$U_P \approx -3\text{V}$

$U_{DS} \approx 50\text{V}$

GaN HEMT

