

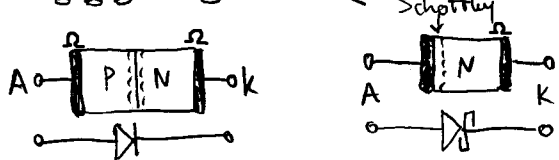
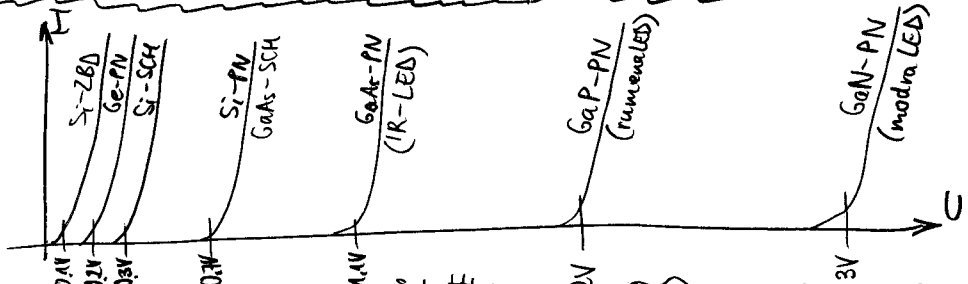
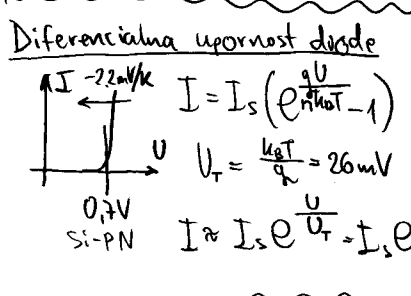
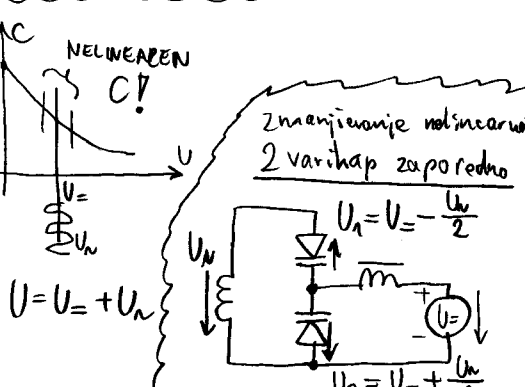
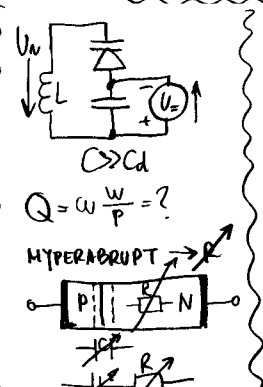
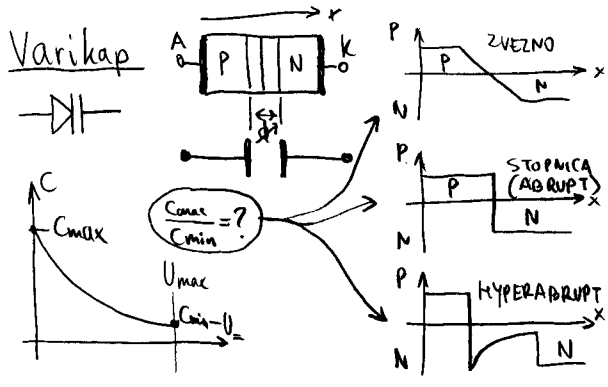
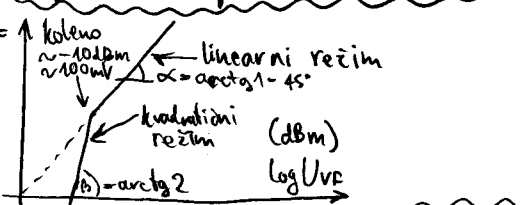
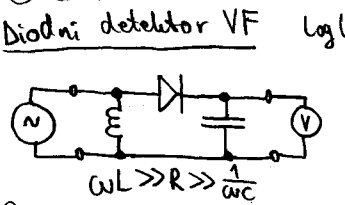
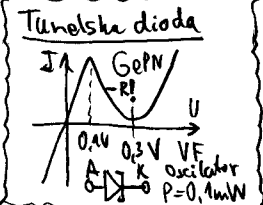
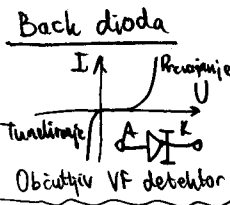
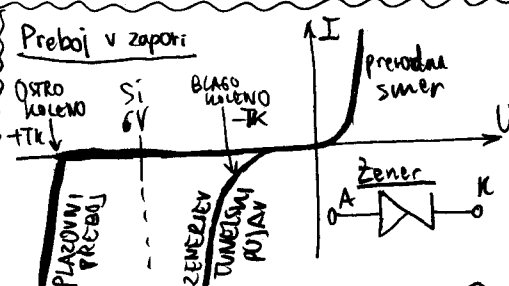


## Visokofrekvenčni gradniki: ojačevalniki, frekvenčno sito, nelinearne naloge

Polprevodnik	$\Delta W = q_0 \Delta U$
Si	1.14eV
Ge	0.67eV
GaAs	1.43eV
InP	1.344eV
InAs	0.354eV
GaP	2.26eV
GaN	3.4eV
6H-SiC	3.05eV
PbS	0.37eV
Diamant(C)	5.5eV


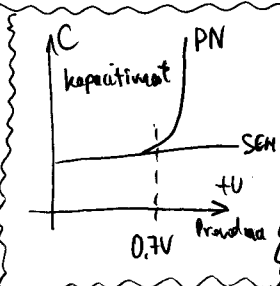


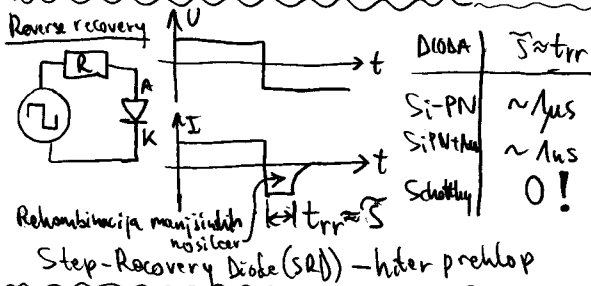Prevodni režim  
 $I = I_s (e^{\frac{qU}{nkT}} - 1)$   
 Schottky PIN  $1 \leq n \leq 2$




Diferencialna uporabnost diode  
 $R = \frac{\Delta U}{\Delta I} = \frac{dU}{dI} = \frac{nU_T}{I} = \frac{n26mV}{I}$   
 $\frac{dI}{dU} = \frac{I_s}{nU_T} e^{\frac{qU}{nU_T}} = \frac{I}{nU_T} = \frac{I}{n26mV}$

I	R
1mA	40Ω
10mA	4Ω

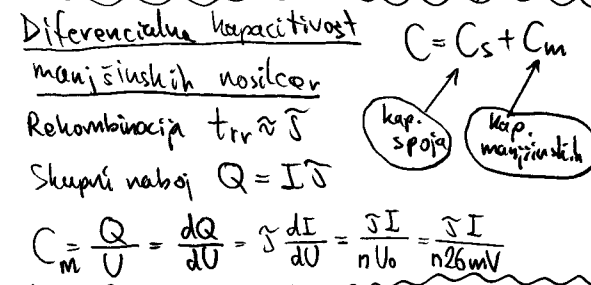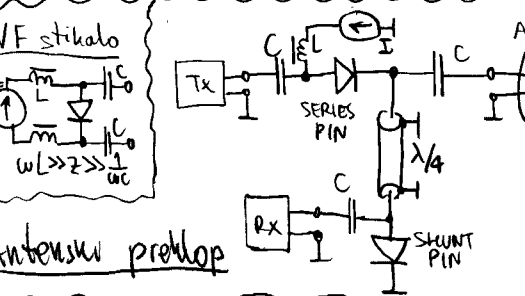


DIOBA	$C_s$	$\tau$	$C_m @ I=1mA$	$\frac{1}{j\omega C} @ 100MHz$
1N4007	30pF	10μs	250nF	-j 6.3mΩ
BAR81	0.3pF	100ns	2.5nF	-j 0.63Ω
1N4148	4pF	5ns	150pF	-j 11Ω

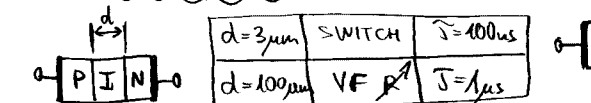

1948 → Bipolarni Ge PNP  
Shockley  
 $\alpha = I_{cE} / I_{cE}$




Ge PNP

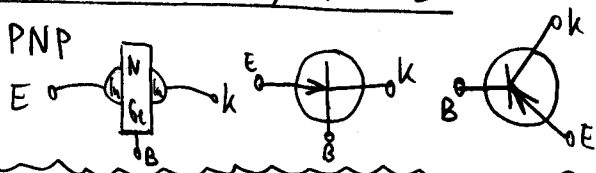


Tranzistorji N/P kanal

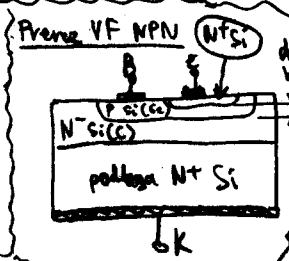bipolarni NPN PNP  
MOSFET  
Elektronov > 300 vrzali v Si!




Nadomestno vezje  $h_{FE} = \beta \approx$  toliko ojačanje  
 $\beta = 10 \dots 1000 < \frac{|N+|}{|P|}$   
 $I_B = I_E (e^{-U_{BE}})$   
 $I_K = I_E \beta$



VF ojačevalnik

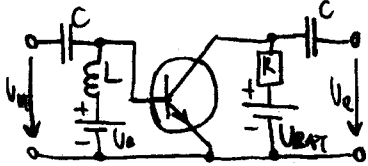


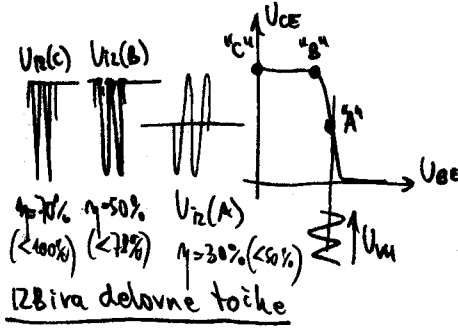
BAZNI TOK = ?  $T_{KBE}$   
TOPLOTNI POREG?  $-2mV/K$   
(THERMAL RUNAWAY)



Tloris VF NPN

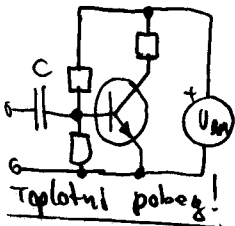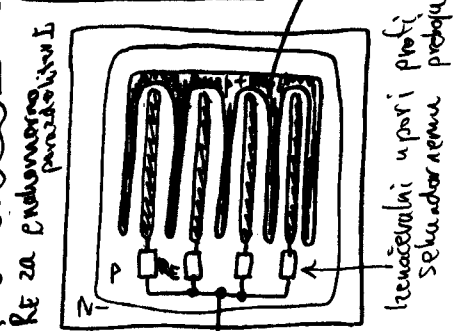


Razred "A"

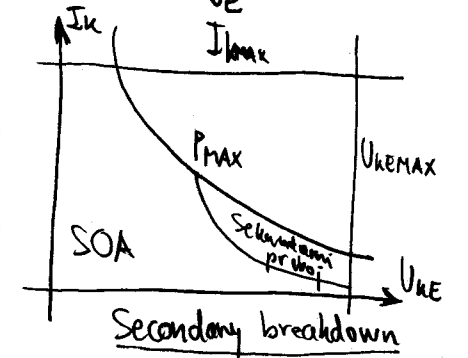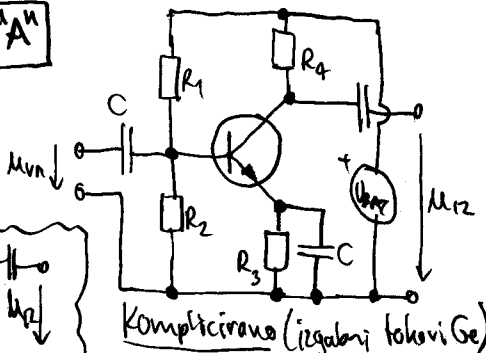








Povratna vezava preprosto!

VF bipolarni


NPN  $\beta = \frac{I_c}{I_b} = \beta = h_{FE}$   
 $\frac{|N+|}{|P|} > \beta \gg \beta_{potencialni}$   
 $U_{BREB} \approx 10-100V > U_{BREB} \approx 2-6V$

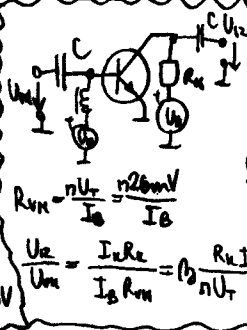

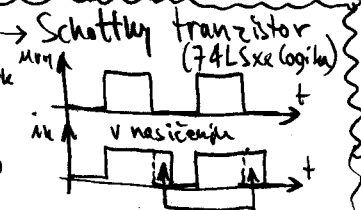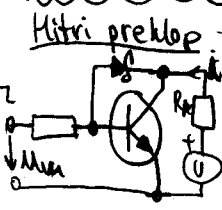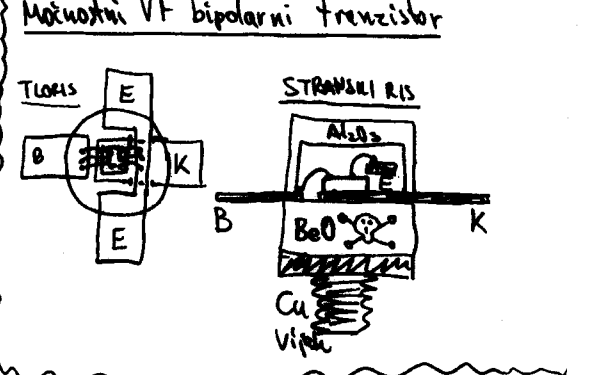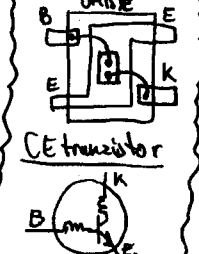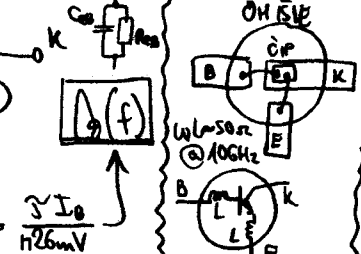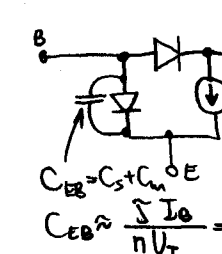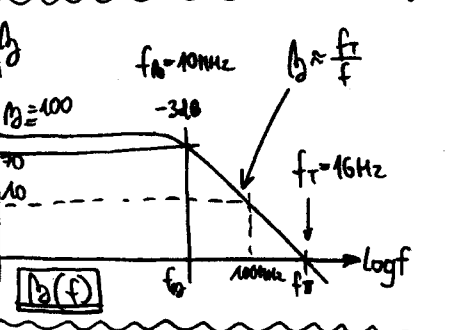
Zagled: razred "A"  
 $I_{Kc} = \frac{U_c}{R_L}$   
 $\frac{U_{vz}}{U_m} = \frac{U_c}{2nU_T}$   
 $U_c = 12V \rightarrow \frac{U_{vz}}{U_m} = 200$   
 $f_{\beta} = \frac{1}{2\pi R_{in} C_{in}} = \frac{1}{2\pi \cdot 200 \cdot 10^{-12}} \approx 400 \text{ MHz}$



Učinki uporabi baze


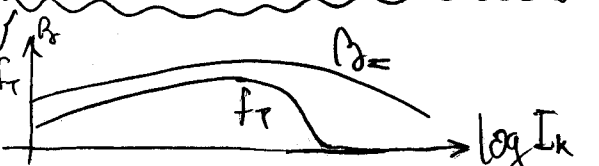


Zgodovina:  
1907 - TRIODA

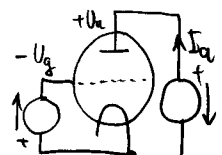


1912 - sprejemnik!



Spojini FET = JFET

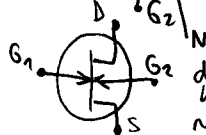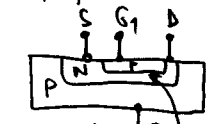

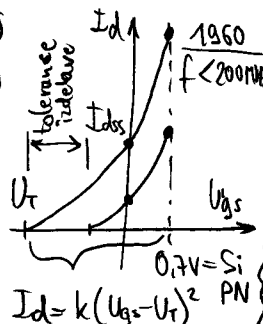$G_1, G_2$  vezana skupaj  
P-kanal  
N-kanal debelina kanala  $n/\mu\text{m}$




N-kanalni MOSFET (1970: f < 200MHz)

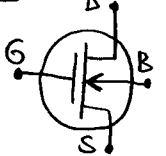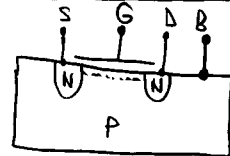

P-kanalni MOSFET





Vrste MOSFETov

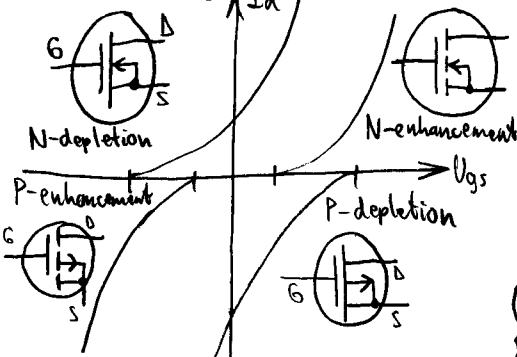

Razvoj 1970 → 2010


$l = 20\mu\text{m} \rightarrow l = 20\text{nm}$   
 $f = 100\text{MHz} \rightarrow f = 100\text{GHz}$

Ojačevalnik

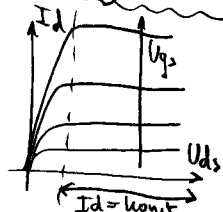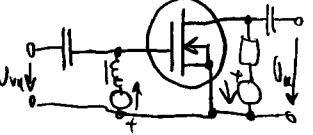


$R_{kanala} = +\alpha T!$


VMOS

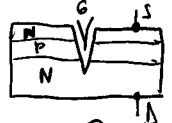


LFMOS

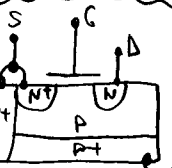


Zaščita pred statiko

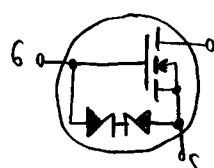

CMOS + Uq (Vdd)

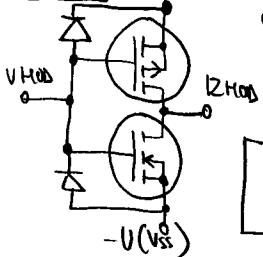


P-N-P-N!

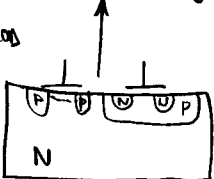


Polprevodniki 3-5?

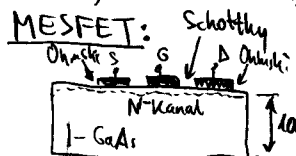
Si:  $\mu_e = 1300\text{cm}^2/\text{Vs}$   
GaAs:  $\mu_e = 5000\text{cm}^2/\text{Vs}$



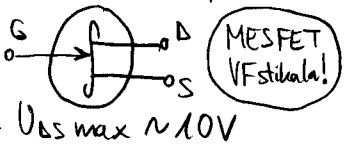Dolžina kanala (vrat):  
1975 → 1 $\mu\text{m}$ , 100GHz  
2013 → 0,1 $\mu\text{m}$ , 100GHz




HEMT:

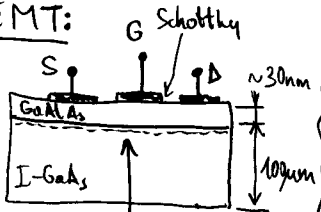

2D oblake elektronov  
 $\mu > 10000\text{cm}^2/\text{Vs}$

GaAs → nizek šum  
InP → visoka frekvenca

Tloris nizkošumni HEMT:

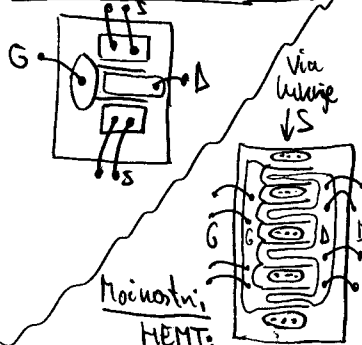


SiC:

250 kristalnih oblik  
3 uporabljene za polprevodnike  
4H-SiC  $\mu_e = 260\text{cm}^2/\text{Vs}$   
 $E_{max} = 3.5 \cdot 10^6\text{V/cm} = 12E_{Si}$   $\Delta W = 3\text{eV}$   
SiC MESFET (2005):  
10W, 2GHz, 28V



GaN:  $\Delta W = 3\text{eV}$

$\mu_e = 1500\text{cm}^2/\text{Vs}$   
 $E_{max} = 2 \cdot 10^6\text{V/cm} = 7E_{maxSi}$   
 $T_{max} = 700^\circ\text{C}$   
 $U_{DSmax} > 100\text{V}$


GaN/GaAlN HEMT:

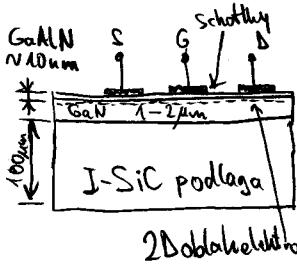


GaN/GaAlN ojačevalnik:

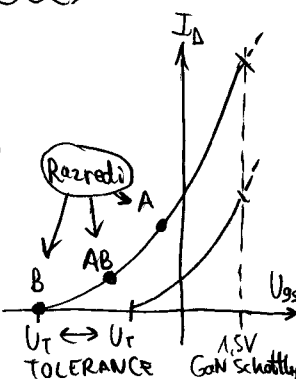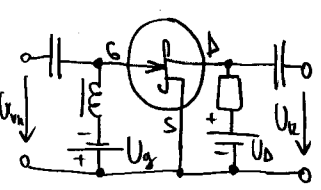

Primerjava:  
BaAs MESFET/HEMT/HEMT

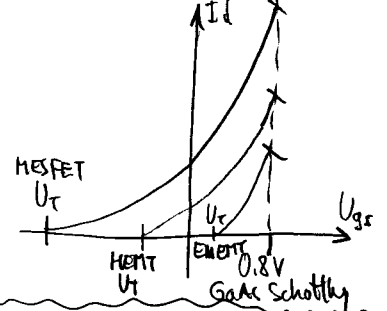

SiGe HBT

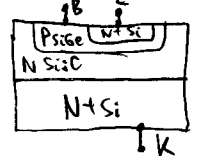


GaAsP HBT

InP HBT



GaAs MESFET stikalo

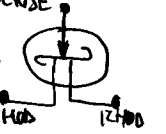- dolga kanal - preklop VF signalov  
- široka vrata  $P_{max} < 10\text{W}$



**Koaksialni kabel:**  $Z_u = \sqrt{\frac{L_0}{C_0}}$

$f \sim 7 \mu\text{m} @ 100 \text{ MHz}$

$Z_u = \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon_0 \epsilon_r}} \ln \frac{R_o}{R_i}$

$Z_u = \frac{60 \Omega}{\sqrt{\epsilon_r}} \ln \frac{R_o}{R_i}$

$(\frac{R_o}{R_i})_{opt} = 3,511 \dots \rightarrow Z_u = 50 \Omega (60 \Omega)$

$20 \Omega < Z_u < 93 \Omega$

**Žični dvovod:**

$(Z_u)_{max} \sim 600 \Omega$

UTP:  $Z_u = 100 \Omega$

**Ploskati dvovod:**

$Z_u = \frac{d}{w} \sqrt{\frac{\mu_0}{\epsilon_0 \epsilon_r}}$

$Z_u > 10 \Omega$

$Z_u = \frac{U_N}{I_N} = - \frac{U_o}{I_o}$

$\Gamma = \frac{Z - Z_u}{Z + Z_u}$

$Z = Z_u \frac{1 + \Gamma}{1 - \Gamma}$

**Smithov:**

①  $\Gamma = \frac{Z - Z_u}{Z + Z_u}$

②  $\Gamma' = \Gamma e^{-j2\beta l}$

③  $Z' = Z_u \frac{1 + \Gamma'}{1 - \Gamma'}$

**S-parametri:**

Cetveropol [S]

Dvovodno v.  $Z_u$

$U_{N1}, U_{N2}, U_{O1}, U_{O2}$

$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} U_{N1} \\ U_{N2} \end{bmatrix} = \begin{bmatrix} U_{O1} \\ U_{O2} \end{bmatrix}$

$S_{11} \approx \Gamma_{in, opt}$

$S_{21} \approx \frac{U_{N2}}{U_{N1}}$  nojačanje

**Simetrija:**  $S_{11} = S_{22}$

**Recipročnost:**  $S_{21} = S_{12}$

**Prilagojenost:**

$S_{11} \rightarrow 0$

$S_{22} \rightarrow 0$

$\Gamma_{VH} = S_{11} + S_{21} \Gamma_b S_{12} + S_{21} \Gamma_b S_{22} \Gamma_b S_{12} + \dots$

$\Gamma_{VH} = S_{11} + S_{21} \Gamma_b S_{12} (1 + \Gamma_b S_{22} + \Gamma_b^2 S_{22}^2 + \dots)$

$\Gamma_{VH} = S_{11} + \frac{S_{21} \Gamma_b S_{12}}{1 - \Gamma_b S_{22}}$

**Verižna vezava:**

$S_{11} = S_{11}^I + \frac{S_{21}^I S_{11}^{II}}{1 - S_{11}^{II} S_{22}^I}$

$S_{22} = S_{22}^{II} + \frac{S_{12}^{II} S_{21}^I}{1 - S_{11}^{II} S_{22}^I}$

$S_{21} = \frac{S_{21}^I S_{11}^{II}}{1 - S_{11}^{II} S_{22}^I}$

$S_{12} = \frac{S_{12}^{II} S_{11}^I}{1 - S_{11}^{II} S_{22}^I}$

**Zaporedna impedanca Z:**

$S_{11} = S_{22} = \frac{Z}{Z + 2Z_u}$

$S_{21} = S_{12} = \frac{2Z_u}{Z + 2Z_u}$

**Sklepek:**

$S_{11} = \frac{Z_{u2} - Z_{u1}}{Z_{u2} + Z_{u1}}$

$S_{22} = \frac{Z_{u1} - Z_{u2}}{Z_{u1} + Z_{u2}}$

**Moči:**  $P_{N2} = P_{in} - P_{out} = P_{in}(1 - |\Gamma|^2)$

$S_{21} = \frac{U_{N2}}{U_{N1}} = \sqrt{\frac{P_{N2}}{P_{N1}}} = \sqrt{1 - |\Gamma|^2} = \sqrt{1 - S_{11}^2}$

$S_{11} = S_{21}$

**Vstavitveno ojačanje G:** (insertion gain)

$G = \frac{P_{N2}}{P_{N1}} = \frac{|U_{N2}|^2}{|U_{N1}|^2} = |S_{21}|^2$

$G_{dB} = 10 \log G = 20 \log |S_{21}|$

**Rollett-ova stabilnost: (1962)**

$|S_{11}| < 1; |S_{22}| < 1 \equiv$  predpogoj

$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{21} S_{12}|} > 1$

$\Delta = S_{11} S_{22} - S_{21} S_{12}; |\Delta| < 1$

**Brezpogojno stabilni ojačevalnik:**

$K > 1; |\Delta| < 1 \equiv$  Unconditional Stability

**Maximum Available Gain: MAG =  $(K - \sqrt{K^2 - 1}) \frac{|S_{21}|}{|S_{12}|}$**  (razpoložljivo ojačanje)

**Pogojno stabilni ojačevalnik:**

$K < 1$

**Maximum Stable Gain: MSG =  $\frac{|S_{21}|}{|S_{12}|}$**  (stabilno ojačanje)

**Glavni vzrok  $K < 1$  je  $S_{12} \neq 0$ !**

$C_{MILLER} \rightarrow S_{12}$

**Protikulrep #1: znižanje  $C_{MILLER}$**

**Tetroda: W. Schottky 1915**

**MOS-tetroda**

**Protikulrep #2: obramenitev**

$V_{HOD}, R, V_{MOS}$

**Protikulrep #3: povratna vezava**

**IZGUBENA** (with feedback network)

**BREZIZGUBNA** (without feedback network)

**Ozemljena baza**

**Kaskada**

**Protikulrep #4: nevtralizacija**

$C_N, U_B, U_K$

**Močestni ojačevalnik:**


$G_{max} / P_{max} / \eta_{max}$

**Prilagoditev harmonikov:  $\uparrow$**


$\lambda/8 @ f_{1/2}$

$\lambda/4 @ 2f$

### Radijska zveza:

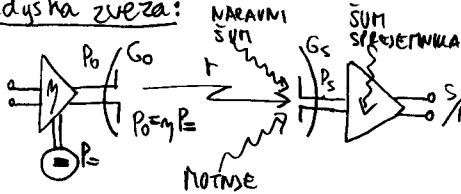



### Toplotno ravnovesje

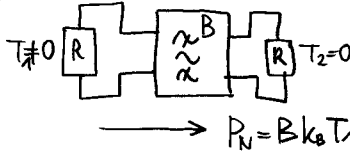

$$k_B = 1.3806488 \cdot 10^{-23} \text{ J/K}$$

$$T [K] \quad T_0 = 293K = 20^\circ C$$
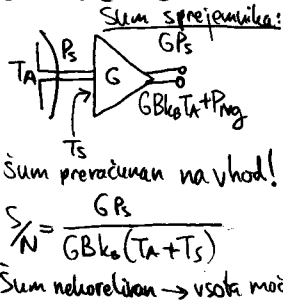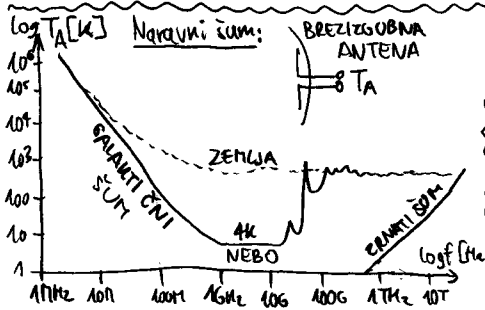
$$P_N = B k_B T \quad B [Hz] \quad k_B T_0 = -173.93 \text{ dBm/Hz}$$



### Šum verige:

$$P_{i1} = G_1 G_2 G_3 P_s$$

$$P_{N1} = B k_B (G_1 G_2 T_1 + G_2 G_3 T_2 + G_3 T_3)$$

$$\left(\frac{S}{N}\right)_{izhod} = \frac{P_s}{B k_B (T_A + T_1 + \frac{T_2}{G_1} + \frac{T_3}{G_1 G_2})}$$

$$T_s = T_1 + \frac{T_2}{G_1} + \frac{T_3}{G_1 G_2} + \frac{T_4}{G_1 G_2 G_3} + \dots$$

### Nesmiselna definicija F:

$$F = \frac{(S/N)_{izhod}}{(S/N)_{vhod}} = 1 + \frac{T_s}{T_A}$$

### Smiselna definicija F:

$$F = 1 + \frac{T_s}{T_0}; \quad T_0 = 293K (= T_A)$$

$$F_{dB} = 10 \log F = 10 \log (1 + \frac{T_s}{T_0})$$

$$T_s = T_0 (10^{\frac{F_{dB}}{10}} - 1) = T_0 (F - 1)$$


### F verige:

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \dots$$

$$F_\infty = 1 + (F - 1) (1 + \frac{1}{G} + \frac{1}{G^2} + \dots) = 1 + \frac{F - 1}{1 - 1/G}$$

$$Zgled: G = 10 \text{ dB} = 10, F = 2.5 \rightarrow F_\infty = 1 + \frac{2.5 - 1}{1 - 1/10} = 2.64 = 4.3 \text{ dB}$$

### Stabilizator (izgubni koef.):

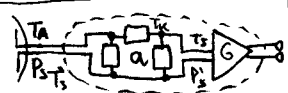


- Večini: ① slabi signal  $P_s' = P_s a$
- ② slabi  $T_A' = T_A a$
- ③ seva lasten šum  $T_c \neq 0$

$$T_s' = (\frac{1}{a} - 1) T_c + \frac{T_s}{a}$$

$$F' = 1 + (\frac{1}{a} - 1) \frac{T_c}{T_0} + \frac{F - 1}{a}$$
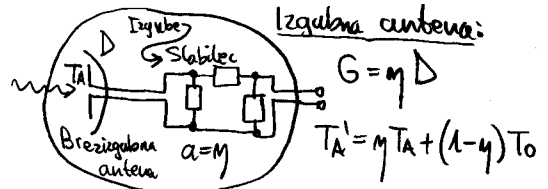
$$T_c = T_0 \rightarrow F' = \frac{F}{a}; F'_{dB} = F_{dB} - 0.5 \text{ dB}$$



$T_A = 200K$

REF

$F'_{dB} = F_{dB} - 0.5 \text{ dB}$

$F'_{dB} = 15 \text{ dB}$

$T_s' = 8973K$

$T = T_A + T_s' = 9173K$

$T_A = 200K$

(A)

$G = 25 \text{ dB} = 316$

$F_1 = 3 \text{ dB} = 2$

$F = 10 \text{ dB} = 10$

$F' = F_1 + \frac{F - 1}{G} = 2.03 = 3.07 \text{ dB}$

$F'_{dB} = F_{dB} - 0.5 \text{ dB} = 8.07 \text{ dB}$

$T_s'' = 1587K$

$T = T_A + T_s'' = 1787K$

$T_A = 200K$

(B)

$T_s'' = F_1 + \frac{F - 1}{G} = 2.1 = 3.2 \text{ dB}$

$T_s'' = 321K$

$T = T_A + T_s'' = 521K$

Primerjava	$\Delta F_{dB}$	$\Delta (S/N)_{dB} = 10 \log \frac{T_1}{T_2}$
REF $\rightarrow$ (A)	$15 \text{ dB} - 8.07 \text{ dB} = 6.93 \text{ dB}$	$10 \log \frac{9173}{1787} = 7.12 \text{ dB}$
REF $\rightarrow$ (B)	$15 \text{ dB} - 3.2 \text{ dB} = 11.8 \text{ dB}$	$10 \log \frac{9173}{321} = 12.5 \text{ dB}$

$T_N = 20K$

$F_1 = 1 \text{ dB} \rightarrow T_1 = 76K$



$F_2 = 0.5 \text{ dB} \rightarrow T_2 = 36K$

$T_1 + T_N = 96K$

$T_2 + T_N = 56K$

$\Delta F = 0.5 \text{ dB} \rightarrow 10 \log \frac{T_1 + T_N}{T_2 + T_N} = 2.3 \text{ dB}$

### Satelitski sprejemnik:

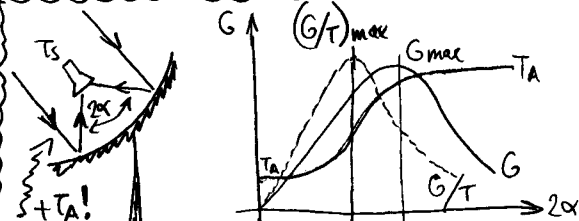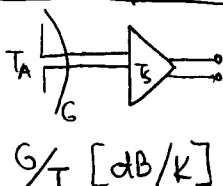

### Osvetlitev zrcal


$G_{max} \rightarrow \sim -10 \text{ dB}$  na robu

$(G/T)_{max} \rightarrow \sim -15, \dots -20 \text{ dB}$  na robu


# Visoko frekvenčna tehnika # 6

15/11/2013

## Ponovitev:

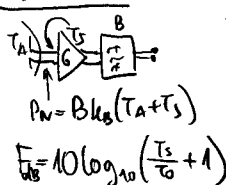


## Veriga:

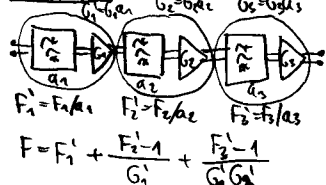


Opacovalnik	G [dB]	T [K]	F [dB]
Trioda	15	2000	8
Klystron, TWT	50	3000-30000	10-20
Si NPN	15	100-300	1.5-3
GaAs HEMT	15	30-100	0.5-1.5
Parametrični	15	30-100	0.5-1.5
Klasični HEMT	20	10-30	0.15-0.5
MMIC	10-20	1000-2000	5-8
OP.AMP.	~80	10^4-10^7	15-55


## Parametrični:

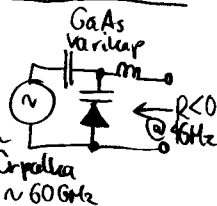


## Šum 1/f:

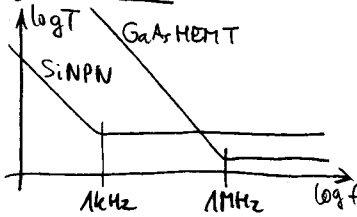

## MMIC:

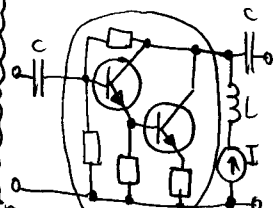


## Šumni izvori:

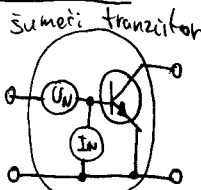


$$F = F_{min} + 4 \frac{R_N}{Z_{in}} \frac{|T_g - T_0|^2}{(1 - |T_g|^2) |1 + T_0|^2}$$

$F_{min}$  = min. šumna števila @  $T_0$   
 $T_0$  = optimalna odbojnost izvora  
 $R_N$  = šumna upornost → vrmirane  $r_n$   
 $F = F_{min} + 4 r_n \frac{|T_g - T_0|^2}{(1 - |T_g|^2) |1 + T_0|^2}$


## Prilagoditev Z

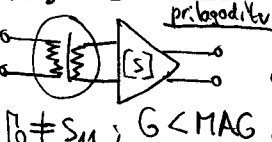


## Merilni izvor:

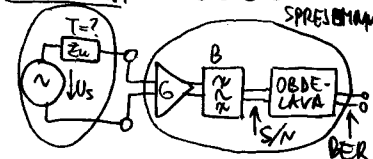


## Zahteve izvora:

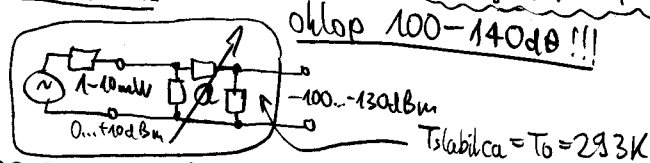


## Meritev $T_S$ :

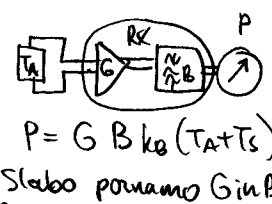


## Vročje/hladno:

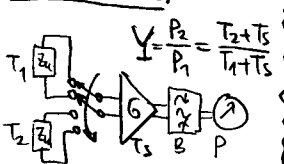



## Nebo/zemlja:

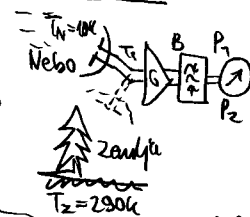

## Mikro/gret upor:

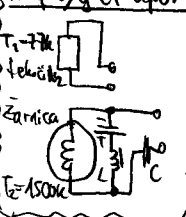

## Plazovna dioda:

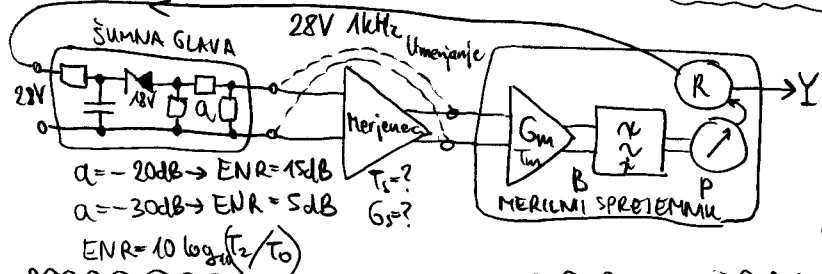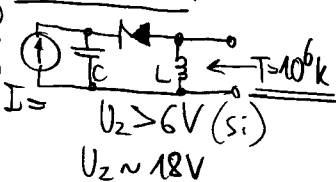

## Brez umejanja:

$$T = \frac{T_2 - Y T_1}{Y - 1}$$

$$T = T_S + \frac{T_m}{G_S}$$

## Z umerjanjem:

4 neznanke:  
 $\rightarrow T_S$   
 $\rightarrow G_S$   
 $\rightarrow T_m$   
 $\rightarrow G_m k_B$


$$P_1 = G_m B k_B (T_1 + T_m)$$

$$P_2 = G_m B k_B (T_2 + T_m)$$

$$P_3 = G_m G_S k_B (T_1 + T_S + \frac{T_m}{G_S})$$

$$P_4 = G_m G_S k_B (T_2 + T_S + \frac{T_m}{G_S})$$
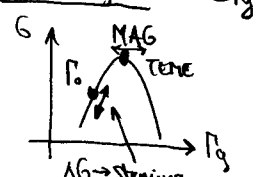
## $\Delta T$ šumne glave: $\rightarrow \Delta T_g = ?$



## Naključni signal

$P_N < P_N(t) >$   
 točnost  $\frac{\Delta P_N}{P_N} = \frac{\pm 1}{\sqrt{B t_m}}$

## Zgled $B = 4 MHz$

$t_m = 400 \mu s$   
 $\frac{\Delta P_N}{P_N} = 2.5\%$   
 $\frac{\Delta Y}{Y} = 3.5\%$

## Povprečje N



$\frac{\Delta P_N}{P_N} = \frac{1}{\sqrt{B t_m N}}$   
 $\frac{\Delta P_N}{P_N} = \frac{1}{\sqrt{N}} \left( \frac{\Delta P_N}{P_N} \right)_{N=1}$

## Zasičenje:


$P_N < \frac{1}{10} P_{dB}$   
 za napako 1%

Zgled  $ENR = 5dB$   
 $F = 15dB$   
 $\frac{\Delta Y}{Y} = 3.5\%$

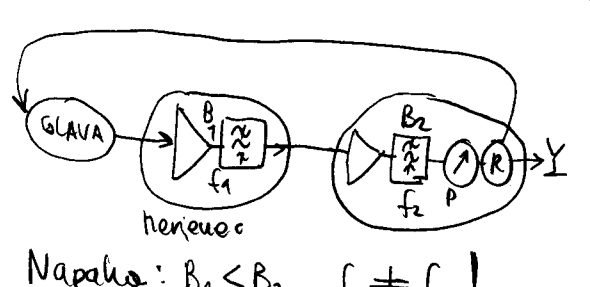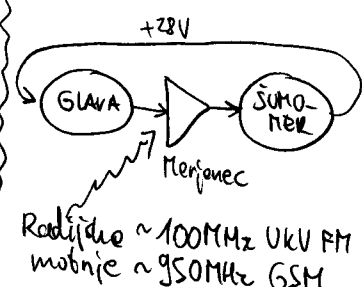
$Y \approx 1.06$   
 $Y = 1.025 \dots 1.095$   
 imeinovalec  $Y - 1 = 0.025 \dots 0.095$   
 $\rightarrow 320\%$  napake!



## Napaka meritve

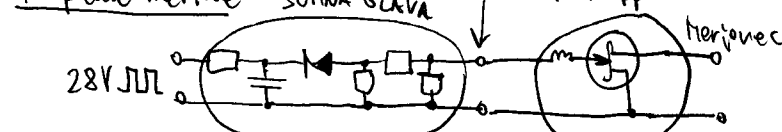

**Nasičenje:**

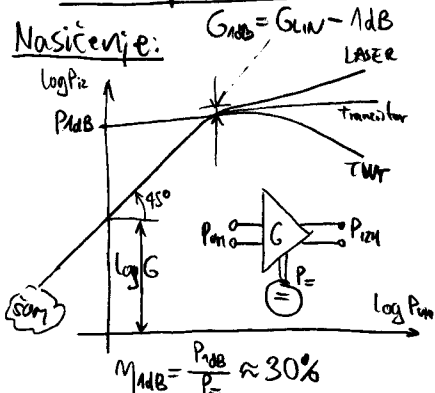

**Zgled: izkoristek OFDM**

$\langle P \rangle = N P_1 \quad N \approx 8192$


$P_{max} = N^2 P_1 \quad \text{TEORUA}$

$M = M_{dB} \frac{\langle P \rangle}{P_{max}} = M_{dB} N \approx 0.004\%$

**PRAKSA**  $EVM \rightarrow \frac{P_{max}}{\langle P \rangle} = 10 \ln 30$




$M = M_{dB} \frac{\langle P \rangle}{P_{max}} = 1\% \dots 3\%$

**Popačenje:**

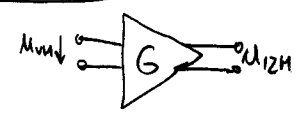

$M_{1zH} = \alpha_0 + \alpha_1 M_{in} + \alpha_2 M_{in}^2 + \alpha_3 M_{in}^3 + \alpha_4 M_{in}^4 + \alpha_5 M_{in}^5 + \dots$

ČLEN	$M_{in}^n$ / $V_{cos \omega t}$	$k_{in} = \frac{U_1}{2} (\cos \omega_1 t + \cos \omega_2 t)$
$\alpha_0$	= (BIAS)	=
$\alpha_1$	$\omega$	$\omega_1, \omega_2$
$\alpha_2$	$2\omega$ (asimetrično)	$= 2\omega_1, 2\omega_2, \omega_2 + \omega_1, \omega_2 - \omega_1$
$\alpha_3$	$3\omega$ (simetrično)	$\omega_1, \omega_2, 3\omega_1, 3\omega_2, \frac{2\omega_1 - \omega_2}{2\omega_2 - \omega_1}, 2\omega_1 + \omega_2, 2\omega_2 + \omega_1$
$\alpha_4$	$= 2\omega, 4\omega$	$= 2\omega_1, 2\omega_2, 4\omega_1, 4\omega_2, \dots$
$\alpha_5$	$\omega, 3\omega, 5\omega$	$\omega_1, \omega_2, \dots, 5\omega_1, 5\omega_2, \dots, \frac{3\omega_1 - 2\omega_2}{2\omega_2 - \omega_1}, 3\omega_1 + 2\omega_2$
$\alpha_6$	$= 2\omega, 4\omega, 6\omega$	$= 2\omega_1, \dots, 6\omega_1, 5\omega_1 + \omega_2, \dots$

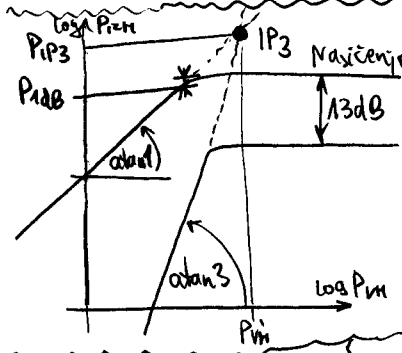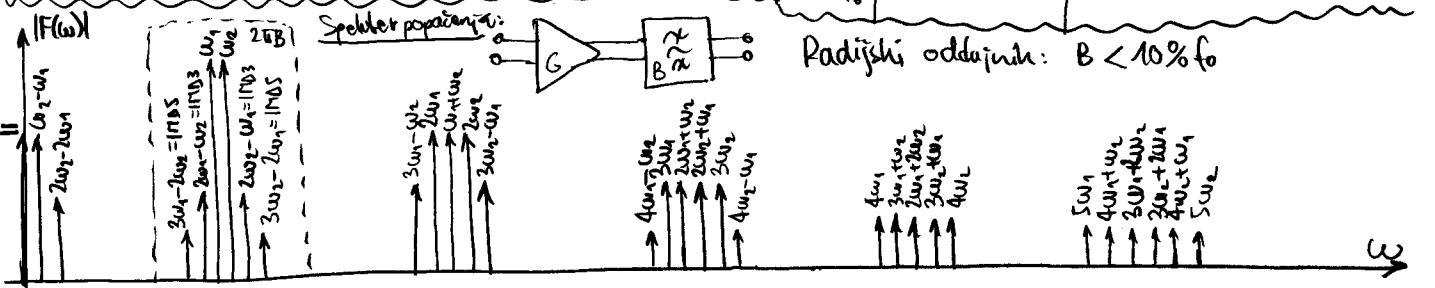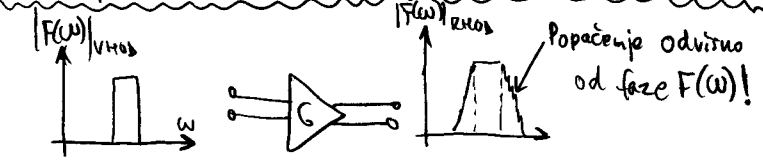

**Moč IMD:**

$P_{LIN} = G P_{in}$

$P_{IMD3} = G_3 P_{in}^3$

$P_{IMD3} = \frac{P_{1dB}^3}{P_{IP3}^2}$

$P_{IMD3} [dBm] = 3 P_{LIN} [dBm] - 2 P_{IP3} [dBm]$


$IMD_5, 7, 9, \dots$

$P_{IMD_N} = \frac{P_{LIN}^N}{P_{IPN}^{N-1}}$


$P_{IMD_N} [dBm] = N P_{LIN} [dBm] - (N-1) P_{IPN} [dBm]$

OBRATNO:  $P_{IMD_N} > P_1$  !


**PIP3 bipolarni T:**

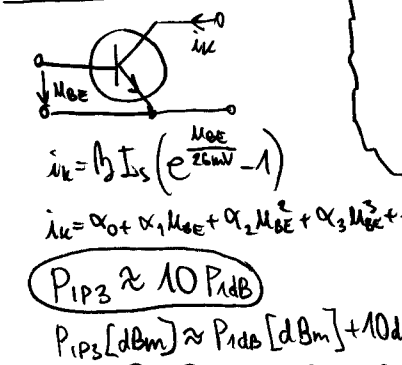

**Bipolarni + RE (MMIC):**

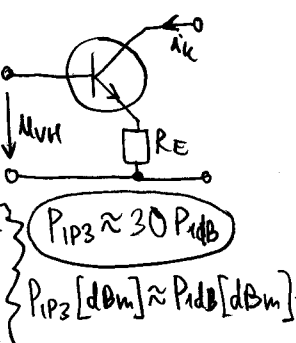

**PIP3 za MOSFET / HEMT:**

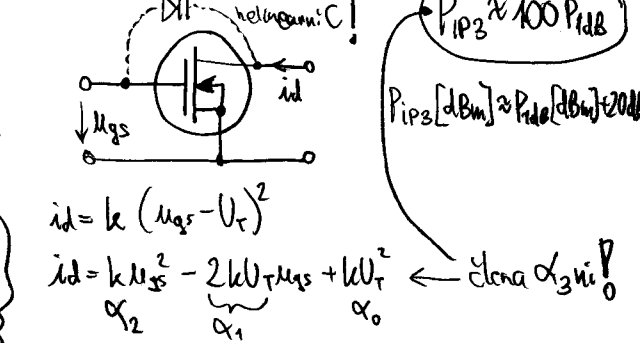

**Zgled:**

$P_{LIN} = 1W = +30dBm$


$P_{IMD3} = 1\mu W = -30dBm$

$P_{IP3} = \sqrt{\frac{P_{LIN}^3}{P_{IMD3}}} = 1kW!$

$P_1$  (bipolarni)  $\approx 333W$

$P_1$  (MOSFET)  $\approx 33W$

**Meritev IMD3:**

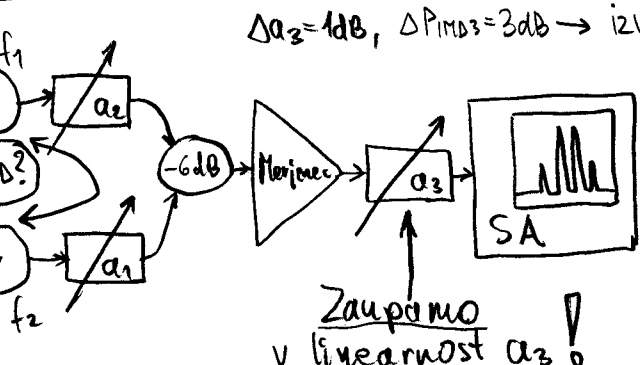


**Zahtevna meritev**

$P_{TX} = +30dBm, P_{RX} = -100dBm$


ANT  $\rightarrow$  SA

Pasovno sito izloči TX

Ponovitev: IMD

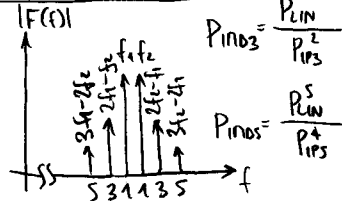


Različni moči:

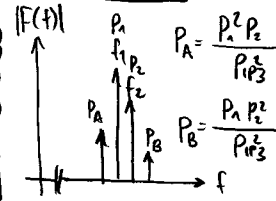


Trije signali:  $f_1, f_2, f_3$   
 9 produktov IMD3:  
 $2f_1 - f_2, 2f_2 - f_1, 2f_1 - f_3,$   
 $2f_2 - f_1, 2f_2 - f_3, 2f_2 - f_2$   
 $f_1 + f_2 - f_3, f_1 + f_3 - f_2$   
 $f_2 + f_2 - f_1 \rightarrow P_{IMD3} = \frac{P_A P_B P_C}{P_{IP3}^2}$


IMD na vnosu:

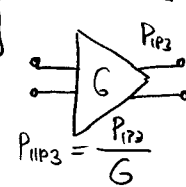


Sprejemnik:

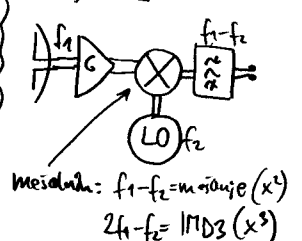

Škodljivost predajačevalnika:

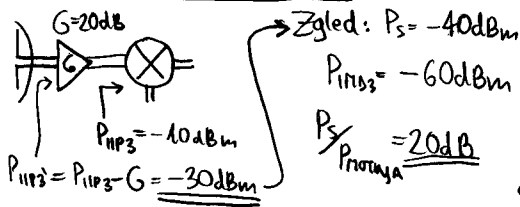


Opazovalna veriga:

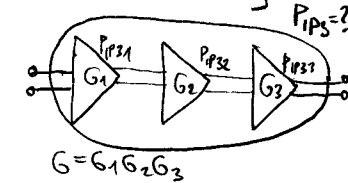


Sestevanje sofaznih kazalcev ( $\alpha_1, \alpha_2 < 0$ )

$$P_{IP3} = \frac{1}{\frac{1}{P_{IP33}} + \frac{1}{P_{IP32} G_3} + \frac{1}{P_{IP31} G_2 G_3}}$$


Sprejemna veriga:

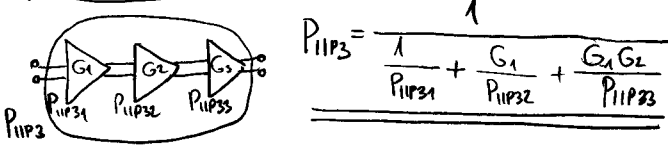

Predpomočje:

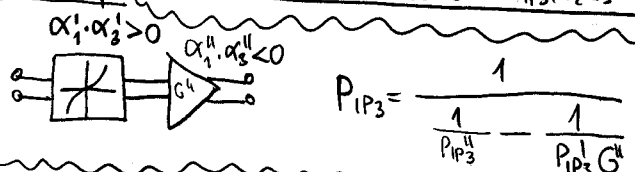



Popačenje popačenja:

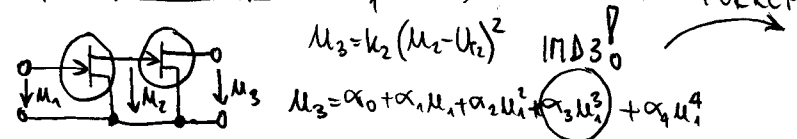


PROTIUKREP




Razred B:

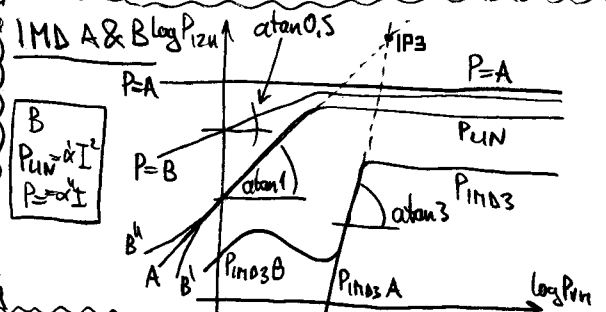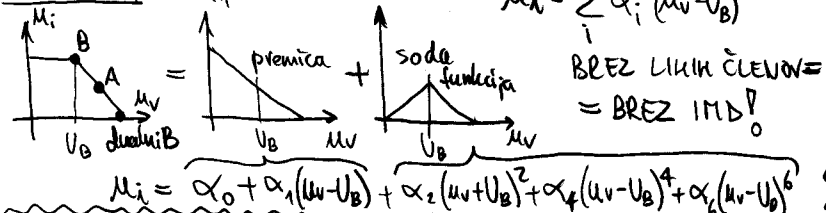




Konstantna ovojnica

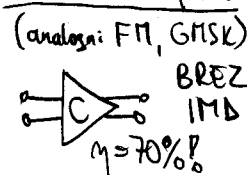


Ločeno faza/ovojnica

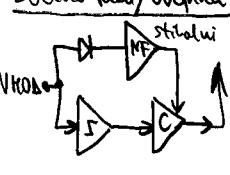


AM oddajnik

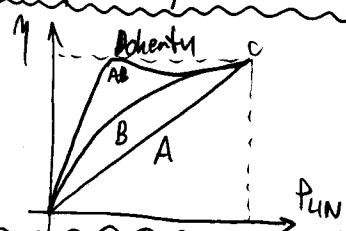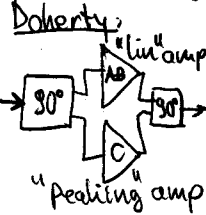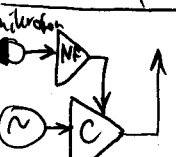


Ena antena RX+TX:

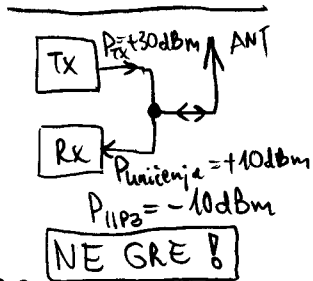

Kretnica RX/TX:

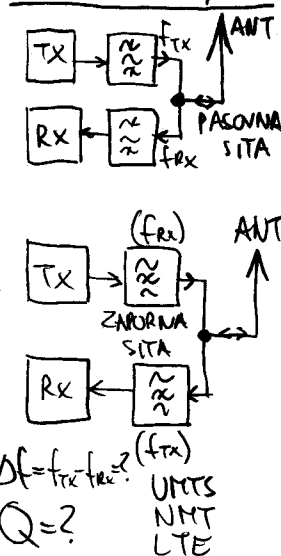

Posivna IMD = PIM:

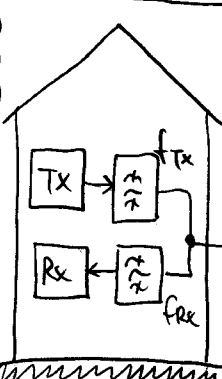

ANTENA na problem  
 $Cu_2O = \text{polprevodnik } \Delta W = 2.1eV$


- Zgled PIM:
- FM TX 1: 95 MHz 1kW
  - FM TX 2: 105 MHz 1kW
  - NMT TX: 425 MHz 10W
  - NMT RX: 415 MHz -120dBm!

$$PIM = f_{NMT RX} - f_2 + f_1 = f_{NMT TX}$$




## Rezonator:


mehanski:

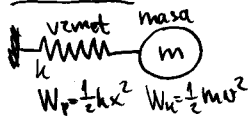

električni:

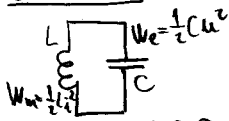

Prevalna funkcija:

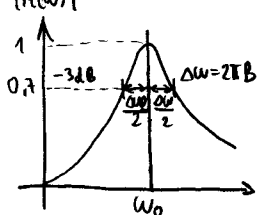

Kvaliteta:

$$Q = \omega \frac{W}{P} \leftarrow \begin{matrix} \text{vshkledjena} \\ \text{izgube} \end{matrix}$$

$$W = \frac{1}{2} L |I|^2$$

$$P = \frac{1}{2} R |I|^2$$


$$Q = \omega \frac{\frac{1}{2} L |I|^2}{\frac{1}{2} R |I|^2} = \frac{\omega L}{R}$$

$$H(\omega) = \frac{\Sigma R}{\Sigma R + (j\omega L + \frac{1}{j\omega C})}$$

$$-3dB \rightarrow \Sigma R = \omega L - \frac{1}{\omega C} = \frac{dX}{d\omega} \cdot \frac{\Delta\omega}{2} \approx 2L \frac{\Delta\omega}{2} = \Delta\omega L = \Delta\omega \frac{Q \Sigma R}{\omega_0} \rightarrow \Delta\omega = \frac{\omega_0}{Q}$$

$$\frac{dX}{d\omega} = L + \frac{1}{\omega^2 C} = L \left( 1 + \frac{\omega_0^2}{\omega^2} \right)$$

Pasovno sito:

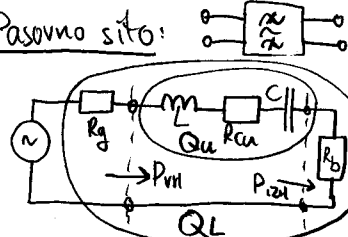

Neobremenjeni  $Q_u = \frac{\omega L}{R_{cu}}$  (UNLOADED)

Obremenjeni  $Q_L = \frac{\omega L}{R_g + R_{cu} + R_b} \leq Q_u$  (LOADED)

Vstavitevno slabljenje

$$a \leq 1$$

$$a = \frac{R_b}{R_{cu} + R_b}$$

Max P  $\rightarrow R_g = R_{cu} + R_b$

$$a = 1 - \frac{2Q_L}{Q_u}$$

Zakasnitev:  $t = \frac{\varphi}{\omega}$


Ozko pasovno vezje

Skupinska zakasnitev  $t_g = \frac{d\varphi}{d\omega} = \frac{1}{1 + \left(\frac{\omega L - \frac{1}{\omega C}}{\Sigma R}\right)^2} \cdot L + \frac{1}{\omega^2 C}$


$$t_{g \max} (\omega = \omega_0) = \frac{L + \frac{1}{\omega_0^2 C}}{\Sigma R} = \frac{2Q}{\omega_0}$$

Nihajni krogi:

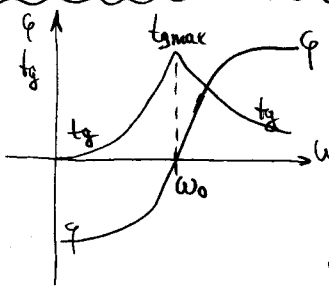
$$\varphi = \arctg \frac{\omega L - \frac{1}{\omega C}}{\Sigma R}$$





Gradnik lestvice:

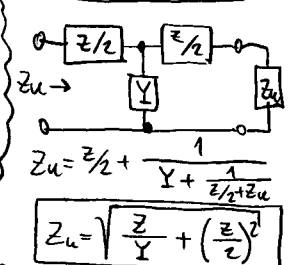



Lestvičasto sito:

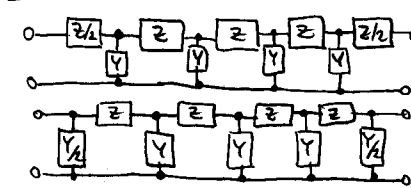


Nizkoprepustno LPF:

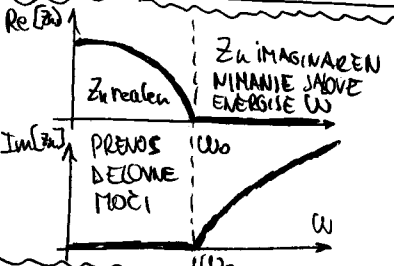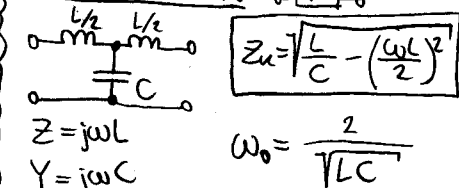

Visokoprepustno HPF:

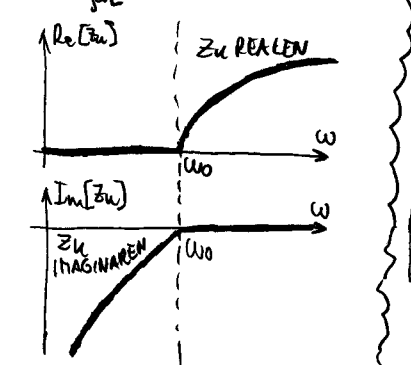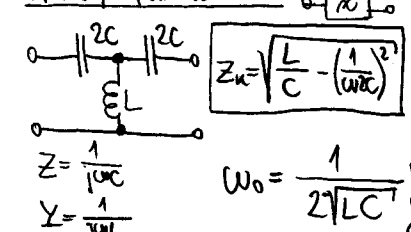


L1L2C2 pasovno BPF:

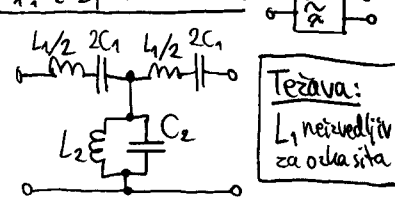


$$Z_u = \sqrt{\frac{j\omega L_1 + \frac{1}{j\omega C_1}}{j\omega C_2 + \frac{1}{j\omega L_2}} + \left(\frac{j\omega L_1 + \frac{1}{j\omega C_1}}{2}\right)^2}$$

$$\omega_{R1} = \frac{1}{\sqrt{L_1 C_1}} = \frac{1}{\sqrt{L_2 C_2}}$$
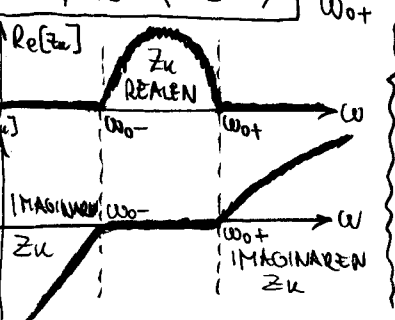
$$Z_u = \sqrt{\frac{L_1}{C_2} - \left(\frac{\omega L_1 - \frac{1}{\omega C_1}}{2}\right)^2}$$




C1L2C2 pasovno BPF:

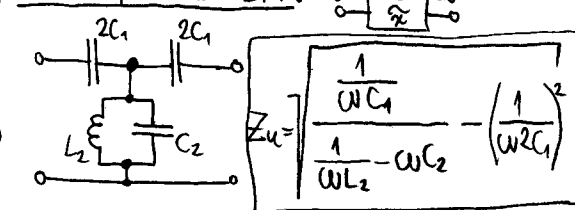


$$Z_u = \sqrt{\frac{\frac{1}{\omega C_1}}{\frac{1}{\omega L_2} - \omega C_2} - \left(\frac{1}{\omega C_1}\right)^2}$$

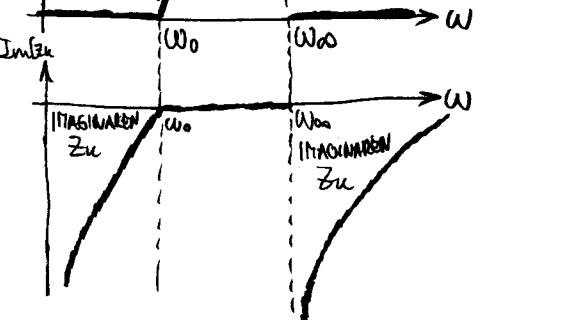
$$\omega_0 = \frac{1}{\sqrt{L_2(4C_1 + C_2)}} \quad \omega_{\infty} = \frac{1}{\sqrt{L_2 C_2}}$$




1/4 REZONATOR:

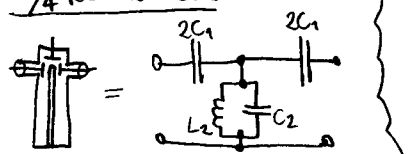


## Zaporedna vezava sit

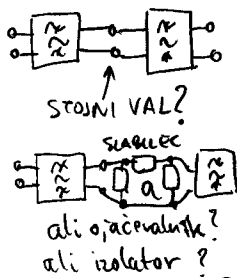


## Antenska kretnica

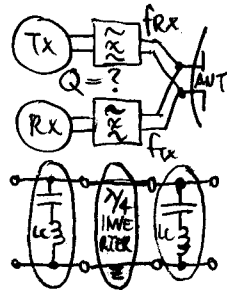


## Mehanska valovanja v trdni snovi:

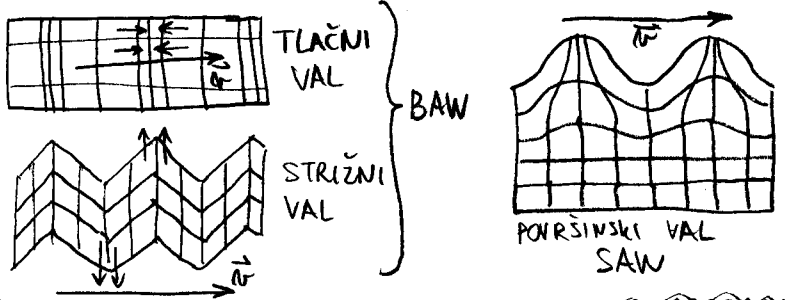

## Mehansko sito:

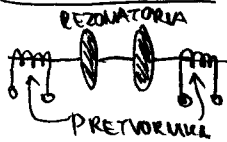

## Piezoelektrik: rezonator + pretvornik

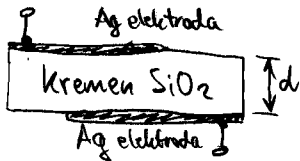

$$d = m \frac{\Lambda}{2}$$



$$\Lambda = \frac{v}{f}$$

$$v = 2 \text{ km/s} - 5 \text{ km/s}$$

kristal SiO<sub>2</sub> AT rez → v = 3.32 km/s

m = 1, 2, 3, 4, 5, 6, ... CELO ŠTEVILCO



## Overtoni:

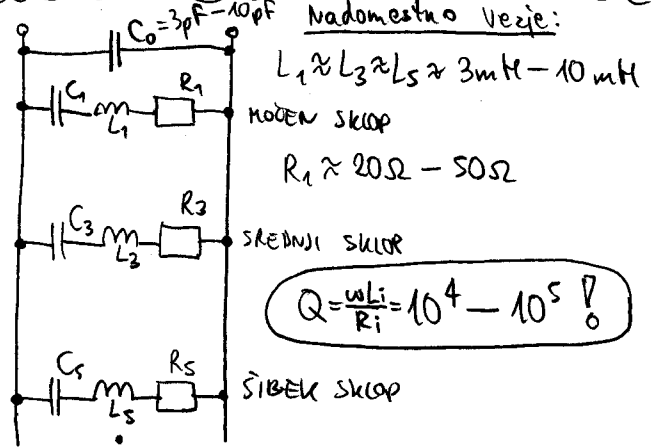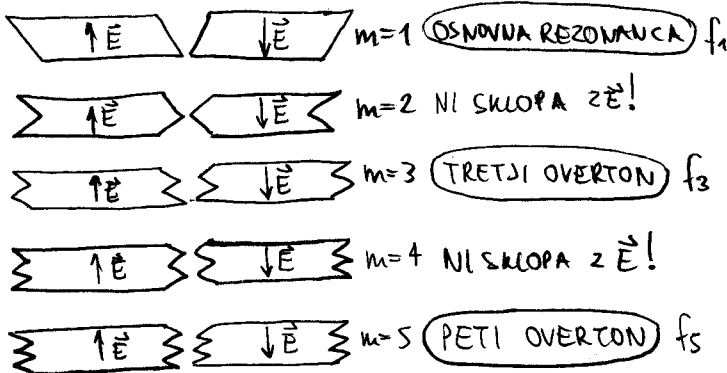



Nadomestna vezje:

L<sub>1</sub> ≈ L<sub>3</sub> ≈ L<sub>5</sub> ≈ 3mH - 10mH  
 R<sub>1</sub> ≈ 20Ω - 50Ω  
 Q = ωLi / Ri = 10<sup>4</sup> - 10<sup>5</sup> !

## Ohisje:

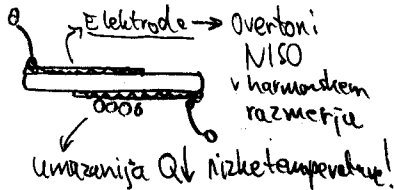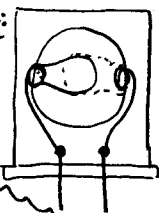


## Kompenzacija Co:

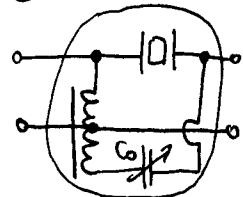
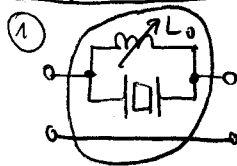


Im(Y)

## Admitanca Y:

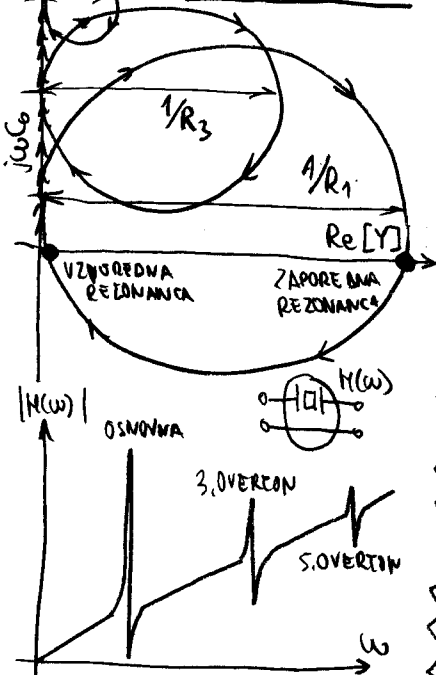

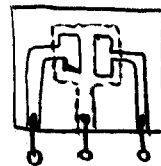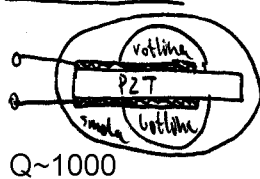
## Piezokeramika: BaTiO<sub>3</sub>, PbZrTi<sub>1-x</sub>O<sub>3</sub> = PZT




## Integracija FBAR: ZnO, AlN

d ≈ 1μm → f ≈ 2GHz

Kristalno sito

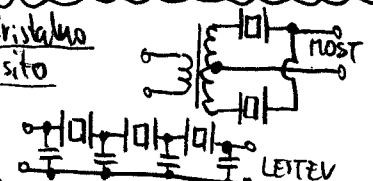


## SAW rezonator:

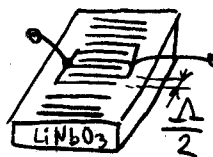

$$300 \text{ MHz} < f < 3 \text{ GHz}$$


## SAW sito:

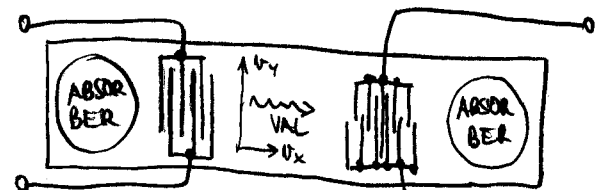


obliskovane elektrode → FIR sito

## Parazitne rezonance:


SiO<sub>2</sub>

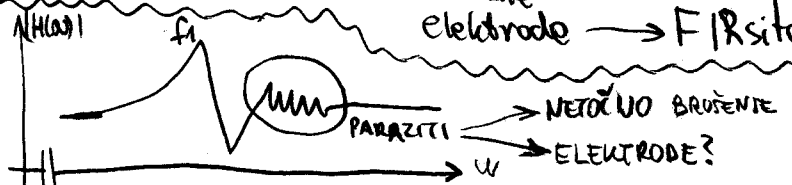



Oscilator:

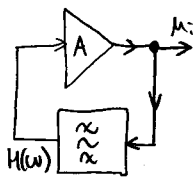


Alexander Meissner 1912:

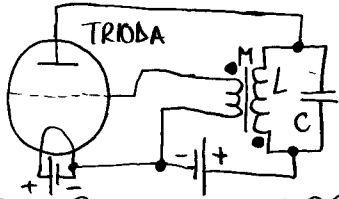


Zagon oscilatorja:

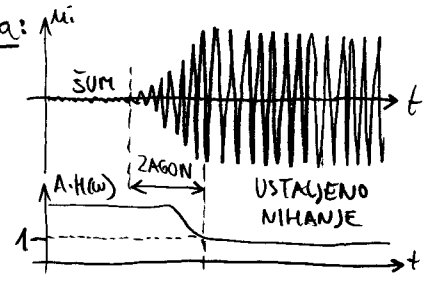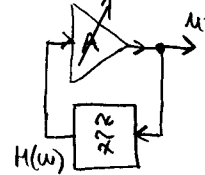

A · H(w):

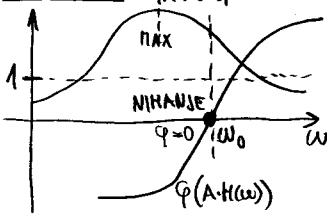

Šum oscilatorja:

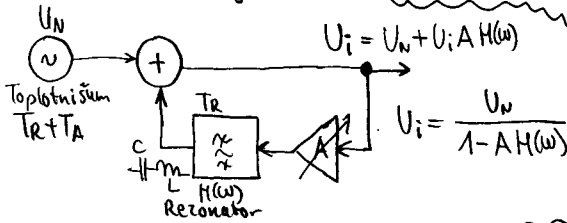

Ustajeno nihanje → A · H(w0) = 1

$$A H(w) = \frac{\Sigma R}{\Sigma R + jwL + \frac{1}{jwC}}$$

$$w = w_0 + \Delta w ; \Delta w \ll w_0$$


$$\frac{jwL + \frac{1}{jwC}}{\Sigma R} \approx 2j \frac{\Delta w L}{\Sigma R} = 2j Q_L \frac{\Delta w}{w_0}$$

$$U_i \approx \frac{U_N}{1 - \frac{1}{1 + 2jQ_L \frac{\Delta w}{w_0}}} = U_N \left( 1 + \frac{1}{2jQ_L} \frac{w_0}{\Delta w} \right) = U_N \left( 1 + \frac{1}{2jQ_L} \frac{f_0}{\Delta f} \right)$$

$$P = \alpha |U|^2$$

$$P_i = P_N \left[ 1 + \left( \frac{f_0}{2Q_L \Delta f} \right)^2 \right]$$
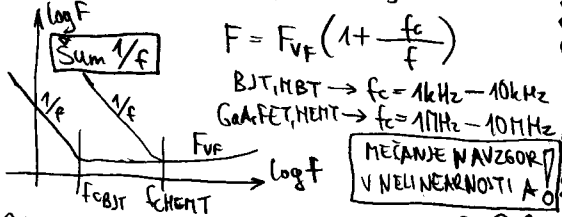
$$P_N = B k_B (T_r + T_A) = B k_B T_0 F$$




Normirani fazni šum L(Δf):

David B. Leeson 1966

$$L(\Delta f) = \frac{P_i/2}{B P_0} = \frac{1}{2} \left[ 1 + \left( \frac{f_0}{2Q_L \Delta f} \right)^2 \right] \cdot \frac{k_B T_0}{P_0} F_{VF} \left( 1 + \frac{f_c}{|\Delta f|} \right) \text{ [rd}^2/\text{Hz]}$$

P0 ≡ izhodna sinusna moč @ w0      P fazni šum = 1/2 P celotni šum!

$$L(\Delta f)_{dB} = 10 \log_{10} \frac{1}{2} \left[ 1 + \left( \frac{f_0}{2Q_L \Delta f} \right)^2 \right] \frac{k_B T_0}{P_0} F_{VF} \left( 1 + \frac{f_c}{|\Delta f|} \right) \text{ [Hz]}$$

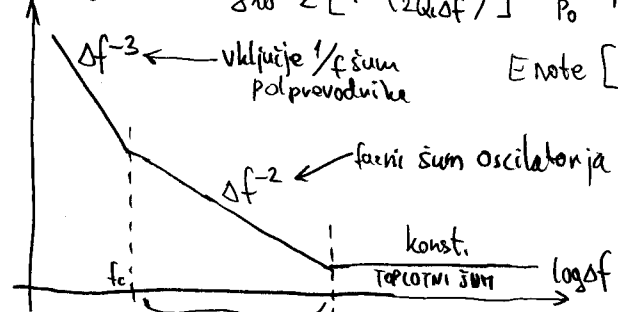


Integrirani šum:

$$\sigma_\phi = \sqrt{2 \int_{f_a}^{f_b} L(\Delta f) df} \text{ RESIDUAL } \phi \text{ M NOISE [rd]}$$


$$\sigma_f = \sqrt{2 \int_{f_a}^{f_b} \Delta f^2 L(\Delta f) df} \text{ RESIDUAL FM NOISE [Hz]}$$

Rieke-jev diagram (Pb):

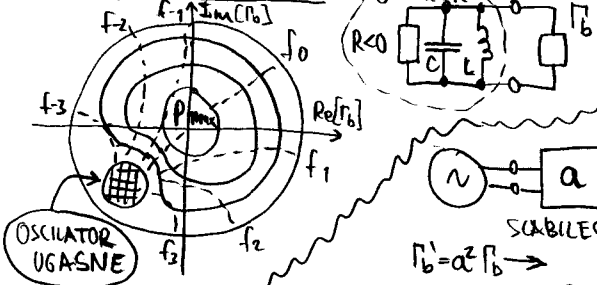


ZANIMIVO OBRNOČE → POENOSTAVLJENI LEESON:  $L(\Delta f) = \frac{f_0^2 k_B T_0 F}{8Q_L^2 \Delta f^2 P_0}$

Protiklop → ločitev bremen:


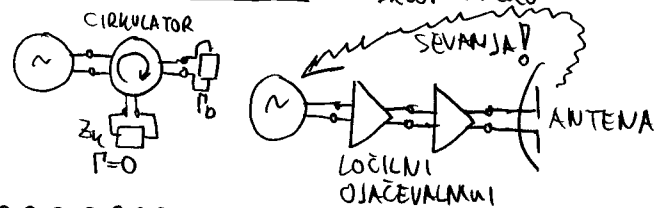


MOTNJE NAPAJANJA?

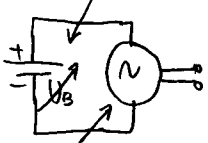


SPREMEMBE TEMPERATURE?

Stabilnost povratne vezave?

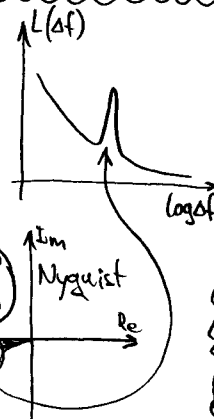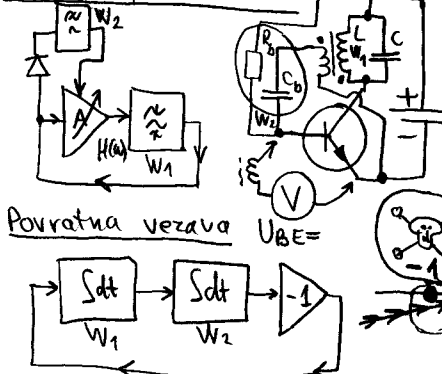



Super-regenerativni RX: Armstrong 1922

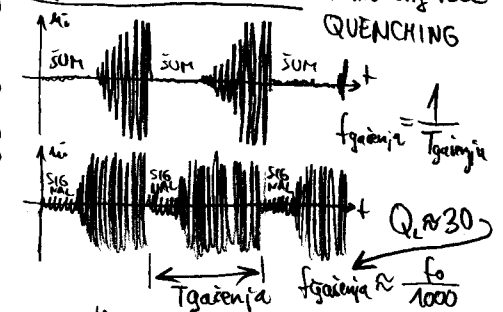


$$G = 20 \log \frac{U_i}{U_{signal}} = 20 \log \frac{10V}{1\mu V} = 140 \text{ dB} + \text{AM down!}$$



**Ponovitev:**

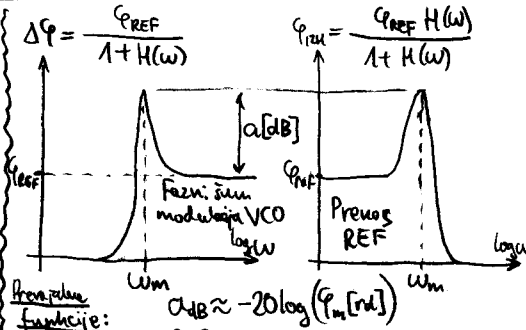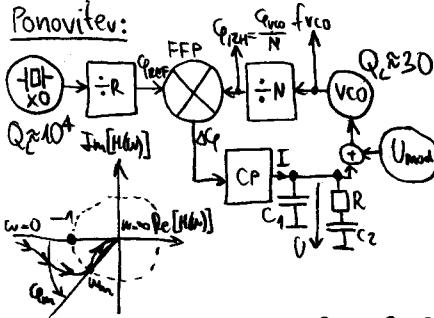

**Fazni šum PLL-a:**

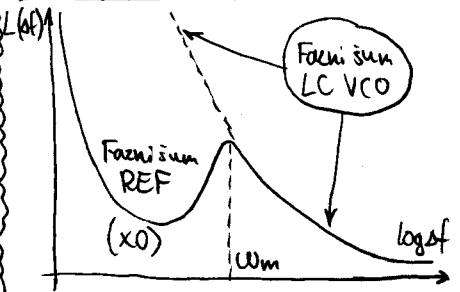

**Območje FFP:**  $|\Delta\phi| < 2\pi$


(mešanik  $|\Delta\phi| < \pi/2$ )  
 Sicer prestop faze!!!

$|\Delta\phi_{VCO}| < 2\pi N$  Zaled  $N=1000, f_{mod}=300\text{kHz}$

$|\Delta f_{VCO}| < 2\pi N f_{mod} \approx 2\text{MHz} \gg 75\text{kHz}$

**UKV FM koleb  $\pm 75\text{kHz}$**

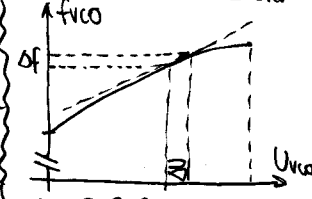**Določanje  $K_{VCO} = \frac{\Delta f_{VCO}}{\Delta U_{VCO}}$**



**Pomembno:  $\frac{K_{VCO}(f)}{N(f)}$**


**PLL z majhnim korakom  $\rightarrow$  počasen!**

Korak =  $f_{REF} = \frac{f_{XO}}{R}$


$\omega_m \approx 2\pi B \ll 2\pi f_{REF}$

Majhen korak  $\rightarrow$  visok  $L(\omega) VCO!$

**Odstajanje dveh PLL:**

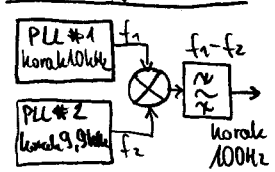


**Veriga PLL:**

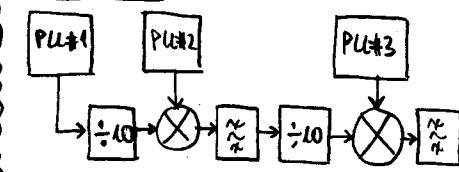


**Ulokovna zanka:**



**(fractional PLL)**

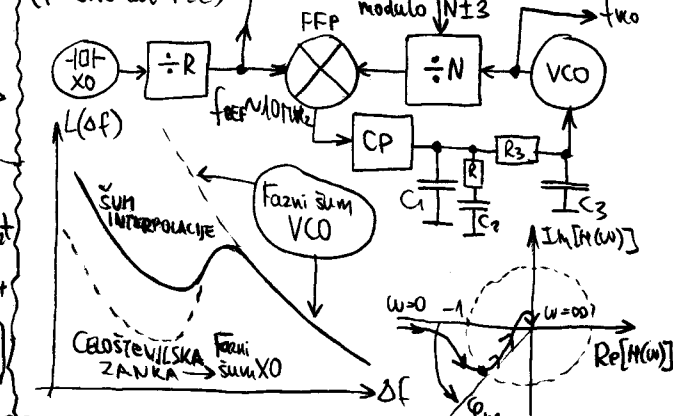


**Neposredni sprejemnik:**

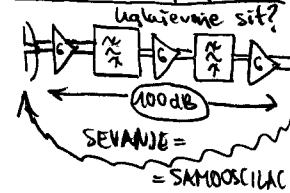



**mešanik (množilnik)**

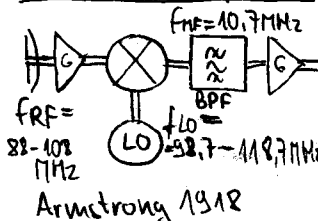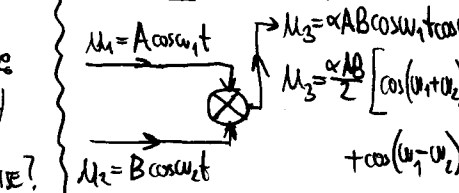

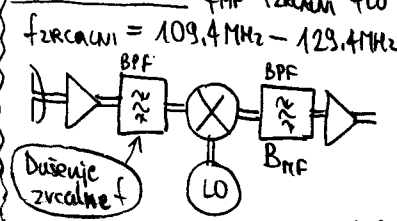
**Zrcalni odziv:  $f_{ZF} = f_{zrcalni} - f_{LO}$**




**Kvadraturni mešanik:**

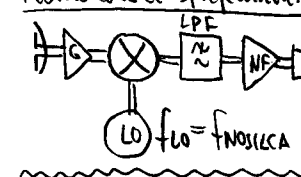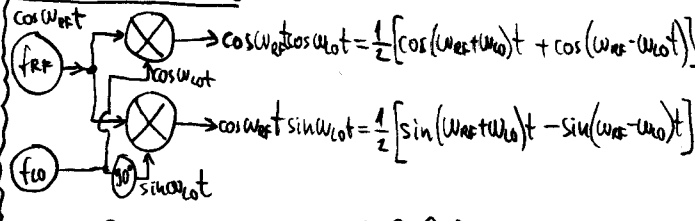

**IMAGE-REJECT MIXER**

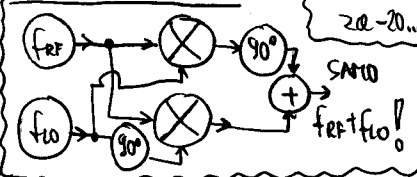

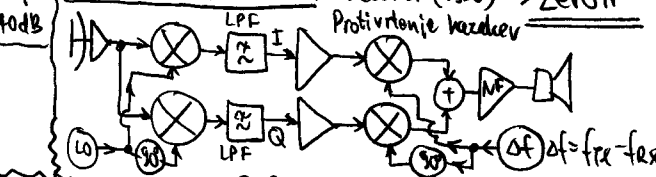**Niščna medfrekvenca: Weaver (1956)  $\rightarrow$  Zero IF**




**Nelinearnost  $\rightarrow$  mešanje:**

$i = I_s (e^{\frac{u}{2kT}} - 1) = \alpha_1 u + \alpha_2 u^2 + \alpha_3 u^3 + \dots$   
 $\alpha_2 u^2 = \alpha_2 (u_{RF}^2 + 2u_{RF}u_{LO} + u_{LO}^2)$


**Fotodioda:  $I_e = \alpha E^2$**

$I_e = \frac{E^2}{P_0} P_0 = \frac{E^2}{2Z_0} \frac{E^2}{2Z_0}$


**Gilbert cell:**

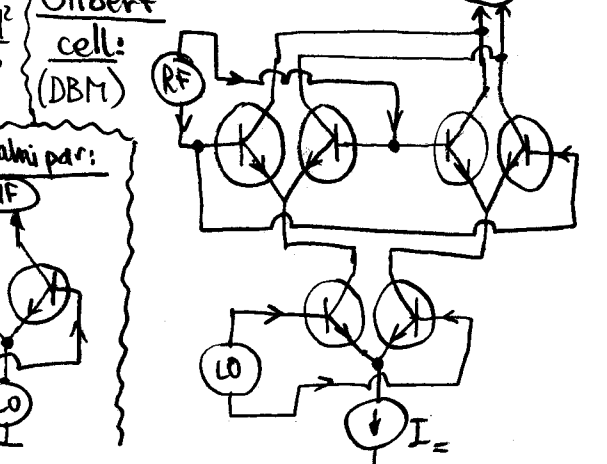


**Balanci mešanik (BM)**

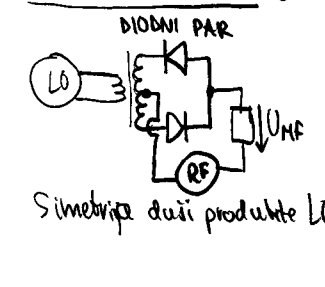

**DBM:**

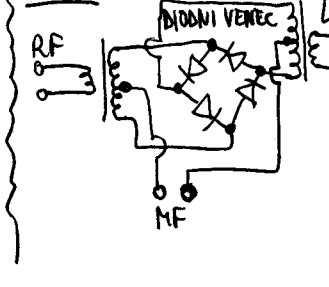

**Diferencialni par:**

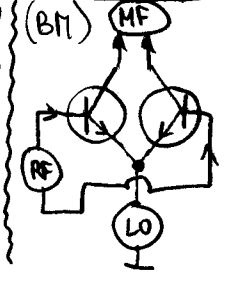

Laminati:

FR-2 papir + fenolna smola (pertinaks)

FR-4 steklena vlakna + epoksi (vitroplast)

$\tan \delta \approx 0.02 \quad Q \approx 50$

$\epsilon_r = 4.3 - 5.3$  (upada 1MHz  $\rightarrow$  10GHz)

PTFE + vlakna  $\tan \delta \approx 0.001$

$\epsilon_r = 2.0 - 2.7$  (vlakna  $\uparrow$ )

PTFE + keramika


$\epsilon_r = 6.0$  ali  $10.0 \quad \tan \delta \approx 0.002$

Ogljikovodiki + keramika (R4000)


$\epsilon_r = 3.0 - 3.5 \quad \tan \delta \approx 0.002$

združljivi s prepregom FR-4



VF vodi:

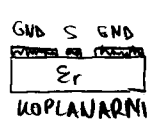

MIKROTRAKASTI (MICROSTRIP)



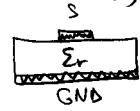


OZEMLJEM KOPLANARNI

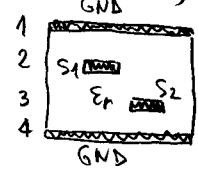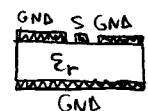

2 - signal vodje

Mikrotrakasti rodovi:

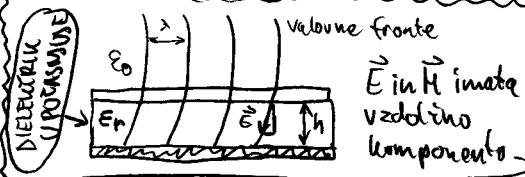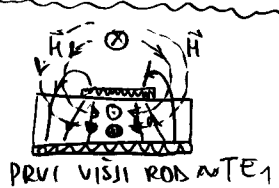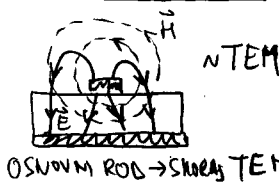

TOČNA OBRAVNAVA:

- 1) HIBRIDNI RODOVI!
- 2) NAPETOST U NE OBSTAJA!
- 3) KARAKTERISTIČNA  $Z_0$  NE OBSTAJA!

NF približek  $k \ll \lambda$ :  $\approx$  TEM,  $E_z \approx 0, H_z \approx 0$   
možna definicija U, I,  $Z_0$

NF približek brez stresanja:




$C \approx \frac{W}{h} \epsilon_0 \epsilon_r$   
 $L \approx \frac{h}{W} \mu_0$   
 $Z_0 \approx \frac{h}{W} \frac{Z_0}{\epsilon_r}$   
NEUPORABNO!  
Zglad  $\epsilon_r = 4.5 \rightarrow \frac{W}{h} = 3.5$   
 $Z_0 = 50 \Omega$


NF približek Wheeler:

enacbe/grafi  
Zglad  $\epsilon_r = 4.5$   
 $Z_0 = 50 \Omega$   
 $\frac{W}{h} = 1.84$

Isiriv toka na rob:

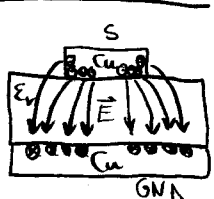


Hrapavost bakra:

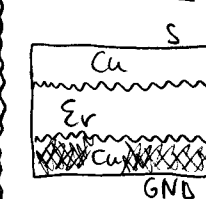


FR-4  $\rightarrow$  navidezni  $\epsilon_{cu} \approx 15.105/\mu m$

- Mikrovalovni laminati
- 1) valjani Cu  $\uparrow$
  - 2) elektrolitski Cu  $\uparrow$


Kapacitivni stroji:

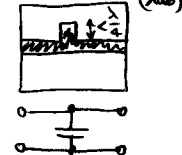


Induktivni stroji:

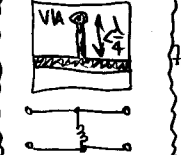


$\lambda/4$  trubi:

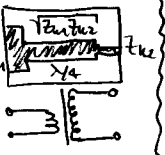



Sklop:

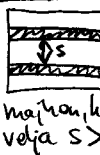


Sodi in lihi rod:

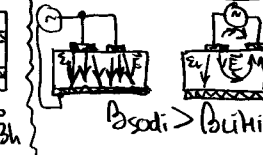


Shlopasti:

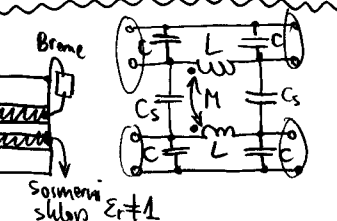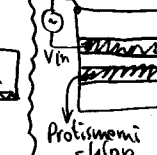


$\lambda/4$  rezonator:

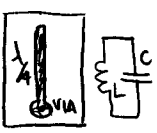


Interdigitalno sito:

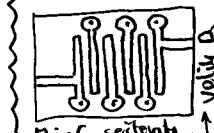



Glavniki:

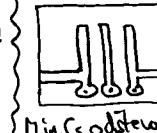


$\lambda/2$  rezonator

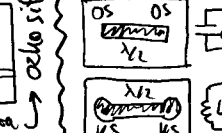


Pasovno sito iz  $\lambda/2$ :

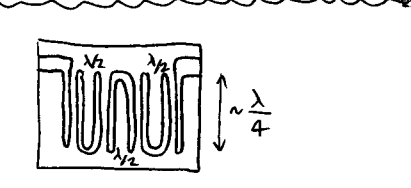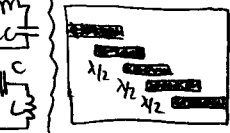


Neenako deljenje?

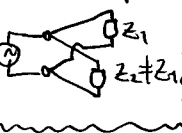



Wilkinsonov hibrid:

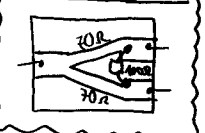


Kvadraturni hibrid:

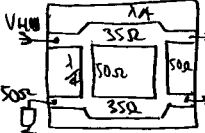


Podgajni hibrid:

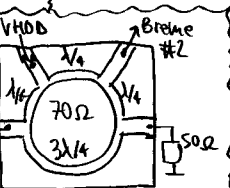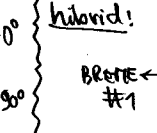


Votlinski rezonator:

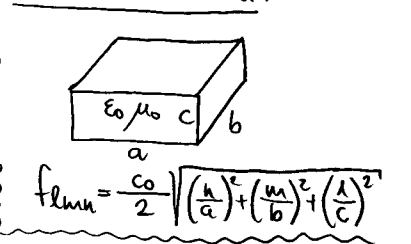


Krpica (Patch) antena:

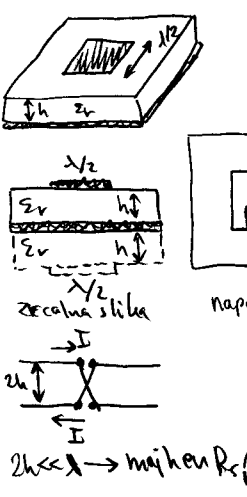

Reza (slot):

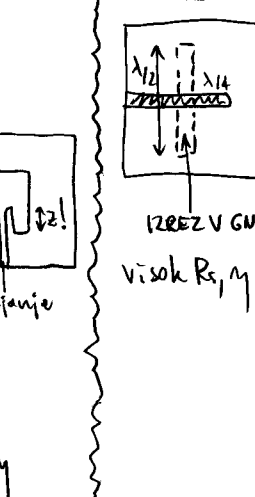

Rezonance olisja:









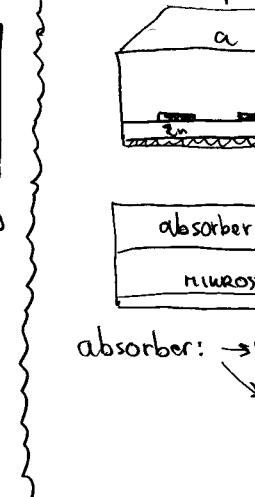


absorber:  $\rightarrow$  prevodna pena  
 $\rightarrow$  gama z deteli Fe





## Osnovne električne lastnosti polprevodnikov

Polprevodnik	Prepovedan energijski pas (bandgap) $\Delta W$ [eV]	Prebojna trdnost $E_{MAX}$ [V/cm]	Mobilnost elektronov $\mu_n$ [cm <sup>2</sup> /Vs]	Mobilnost vrzeli $\mu_p$ [cm <sup>2</sup> /Vs]
PbS	0.37	(preboj<2V)	600	200
Se	1.95	(preboj<25V)	0.005	0.14
PbSe	0.27		900	700
PbTe	0.32		1700	930
Cu <sub>2</sub> O	2.137	(preboj<8V)	0.2	0.1
Si	1.11	$3 \cdot 10^5$	1400	450
Ge	0.67	$10^5$	3900	1900
Si <sub>1-x</sub> Ge <sub>x</sub>	0.67-1.11	$3 \cdot 10^5$		
SiO <sub>2</sub>	9	$10^6$ - $10^7$		
Si <sub>3</sub> N <sub>4</sub>	5.4	$3 \cdot 10^6$		
C (diamant)	5.5	$10^6$ - $10^7$	2200	1800
3C-SiC	2.36	$10^6$	800	320
4H-SiC	3.23	$3 \cdot 10^6$ - $5 \cdot 10^6$	900	120
6H-SiC	3.05	$3 \cdot 10^6$ - $5 \cdot 10^6$	400	90
GaAs	1.43	$4 \cdot 10^5$	5000	400
AlAs	2.16	$6 \cdot 10^5$	1200	420
Ga <sub>1-x</sub> Al <sub>x</sub> As	1.43-2.16	$4 \cdot 10^5$ - $6 \cdot 10^5$		
InP	1.344	$5 \cdot 10^5$	5400	200
GaP	2.26	$10^6$	250	150
GaSb	0.726	50000	3000	1000
InAs	0.354	40000	40000	400
InSb	0.17	1000	77000	850
GaN	3.4	$5 \cdot 10^6$	1800	30
AlN	6.28	$1.2 \cdot 10^6$ - $1.8 \cdot 10^6$	300	14
InN	0.65		3200	
BN	5.4	$3 \cdot 10^6$ - $6 \cdot 10^6$	200	500
CdS	2.42		400	
CdSe	1.74		650	
CdTe	1.44		1100	100
Hg <sub>1-x</sub> Cd <sub>x</sub> Te	0-1.5			






# Diode

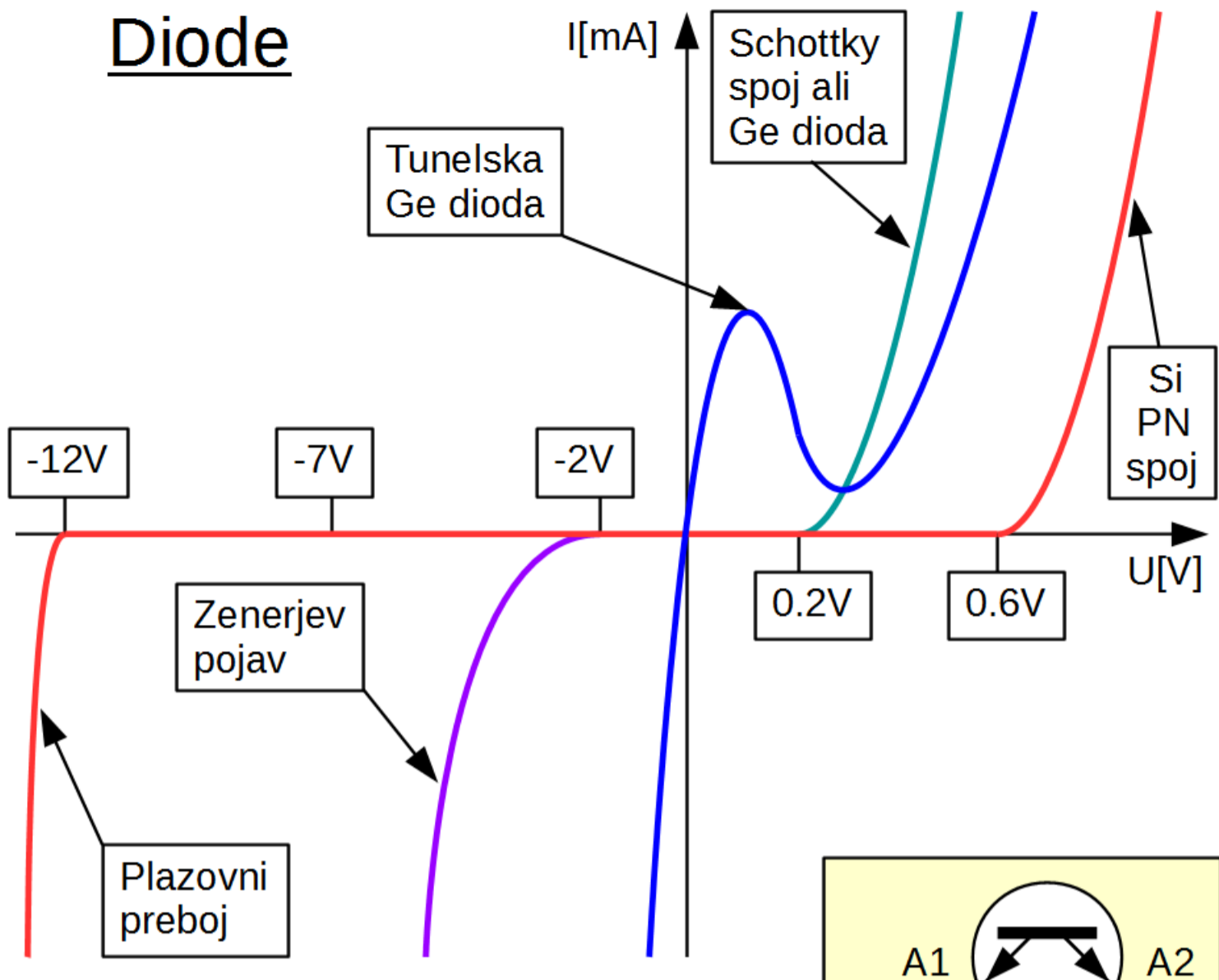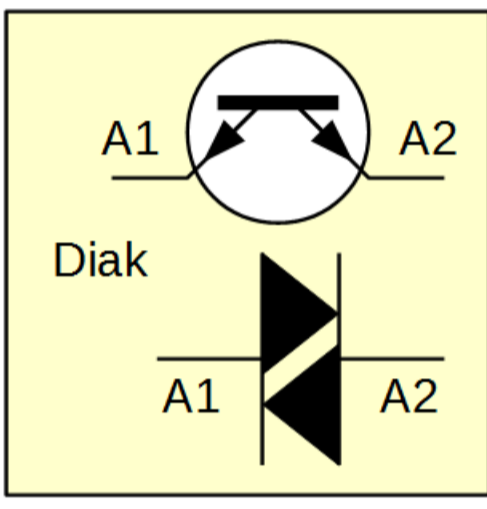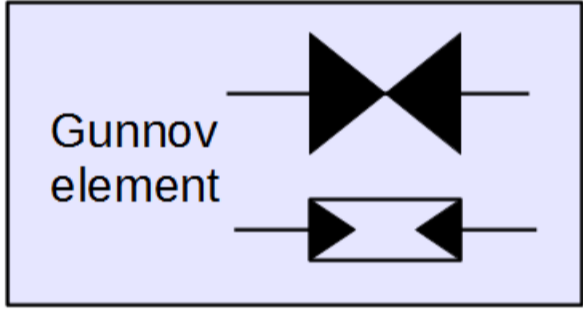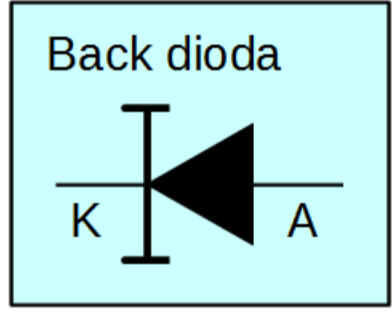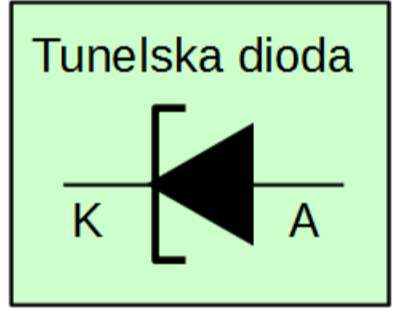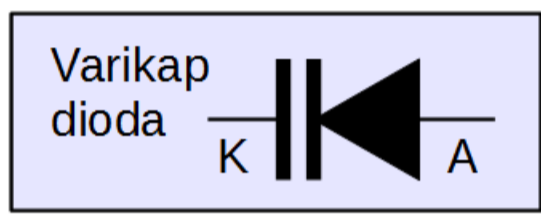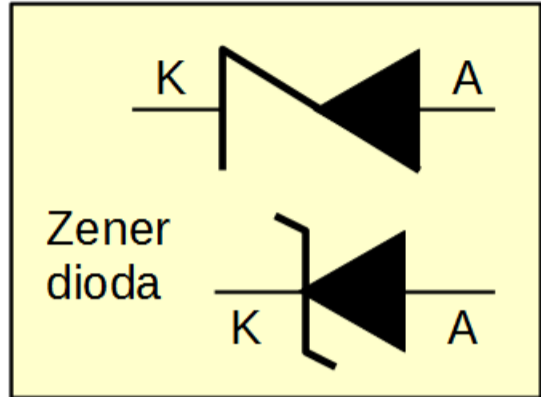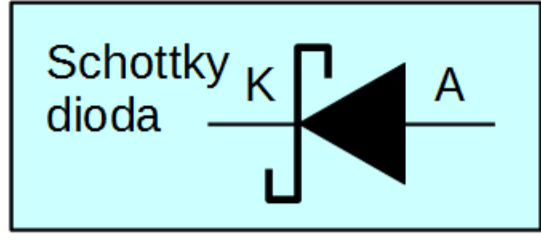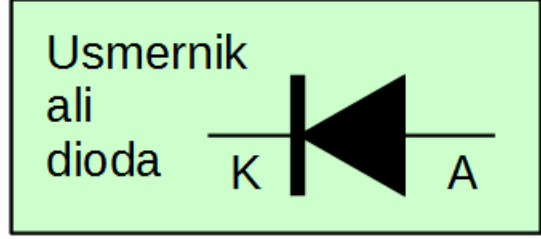

# Spojni tranzistorji

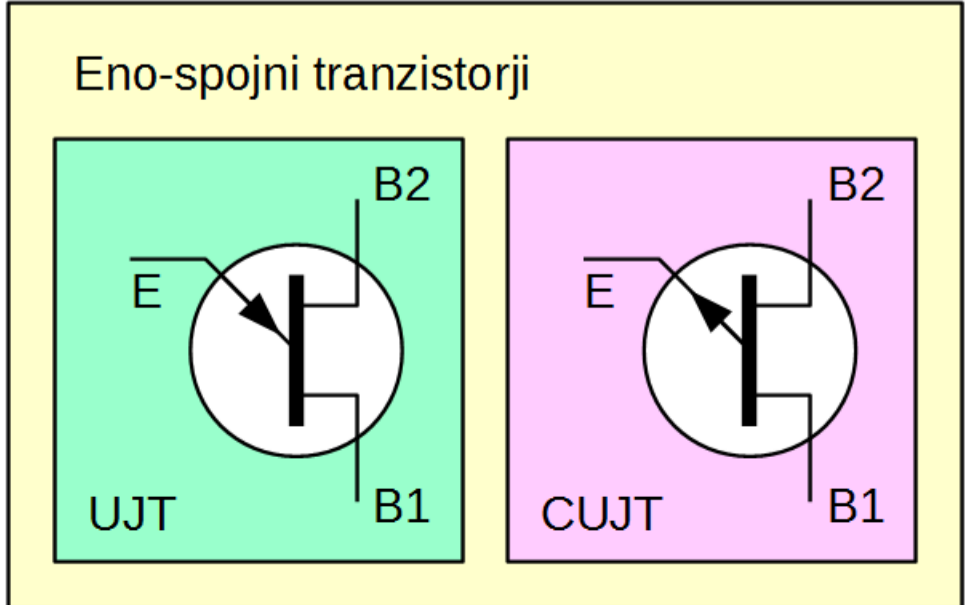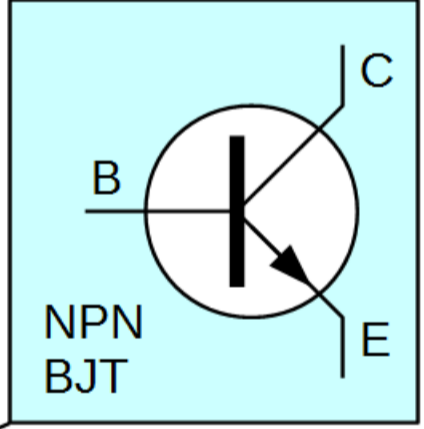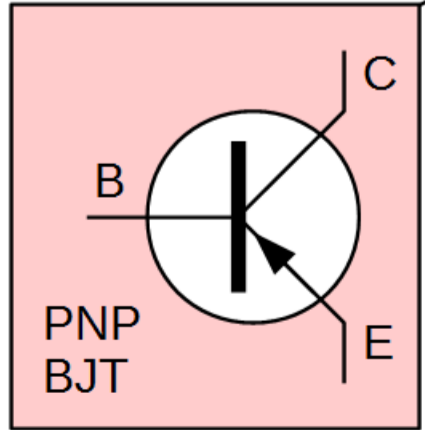
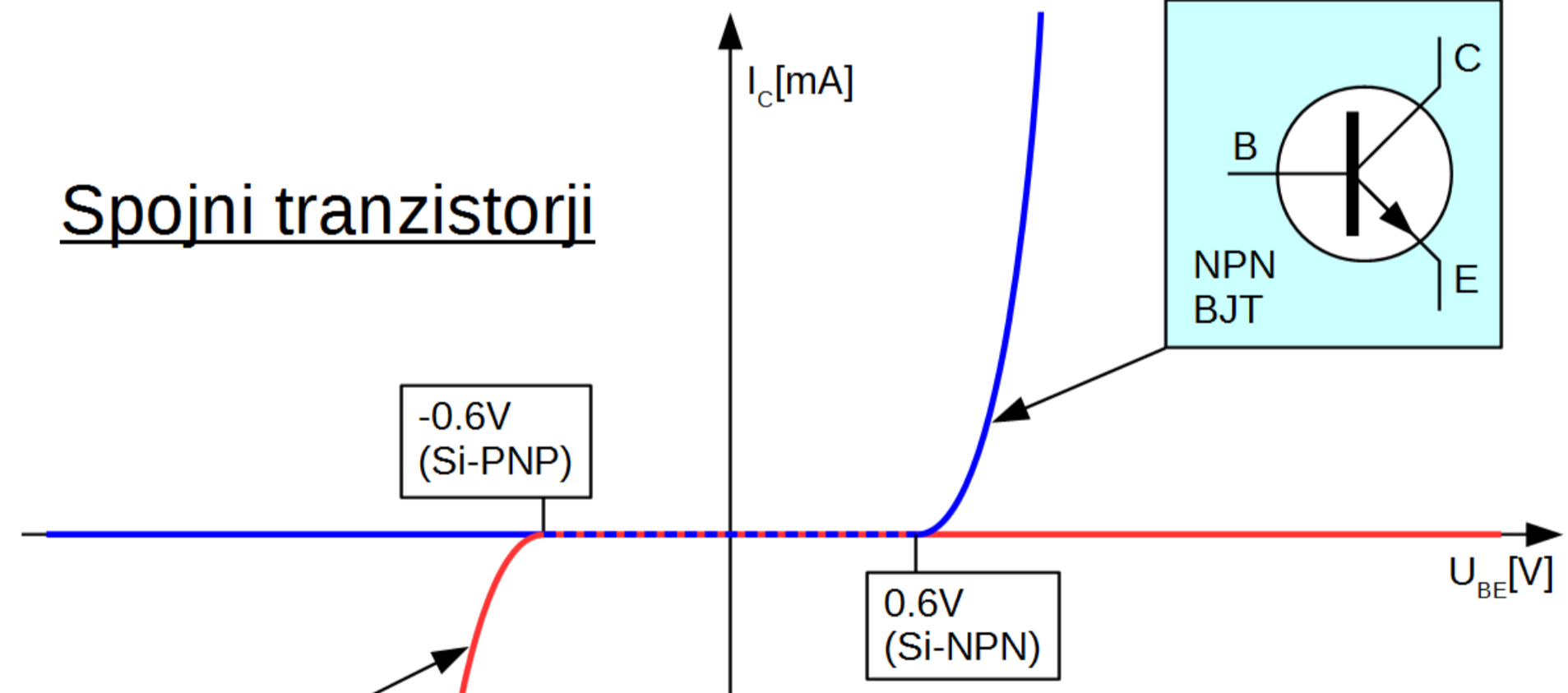




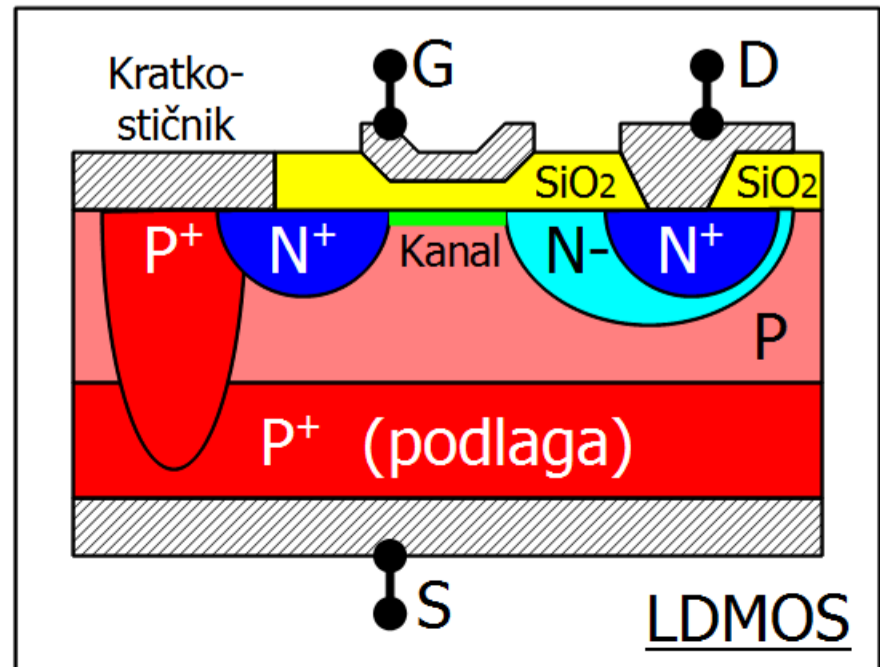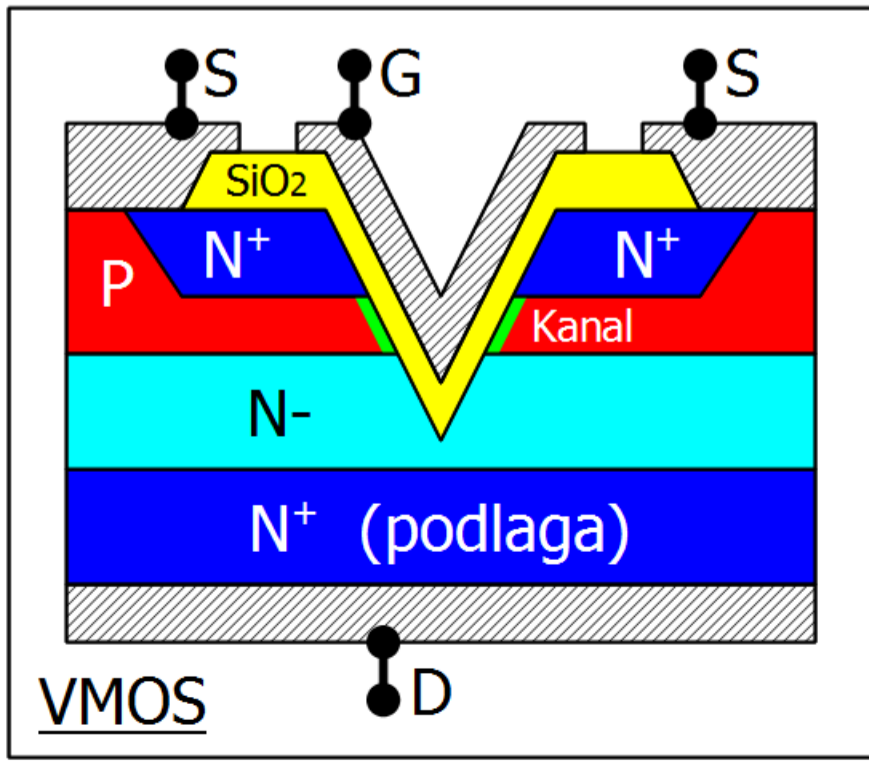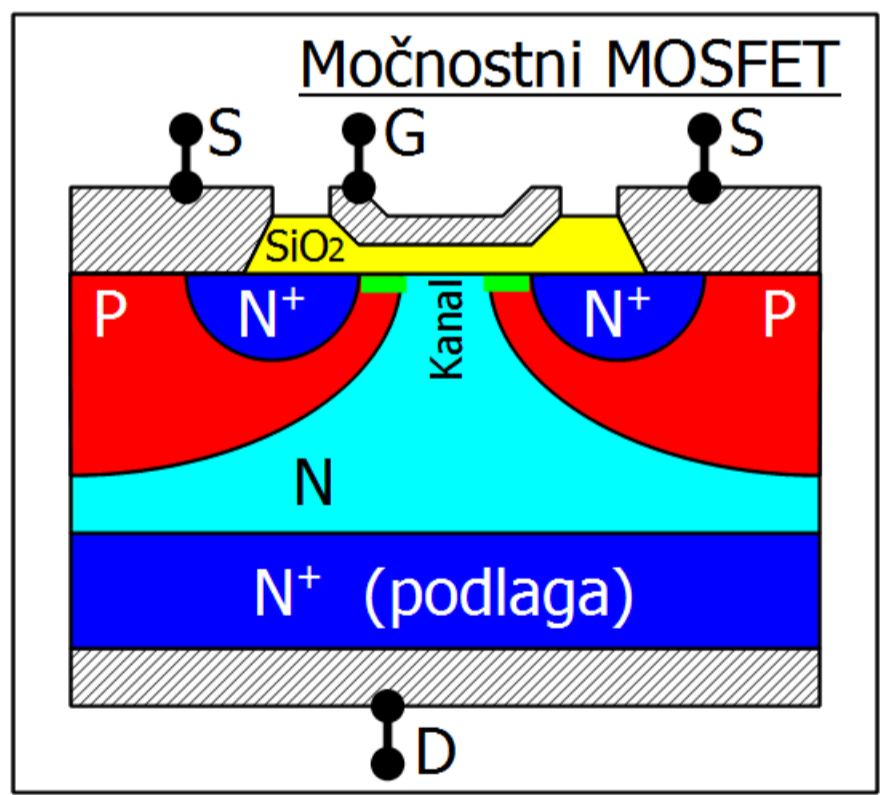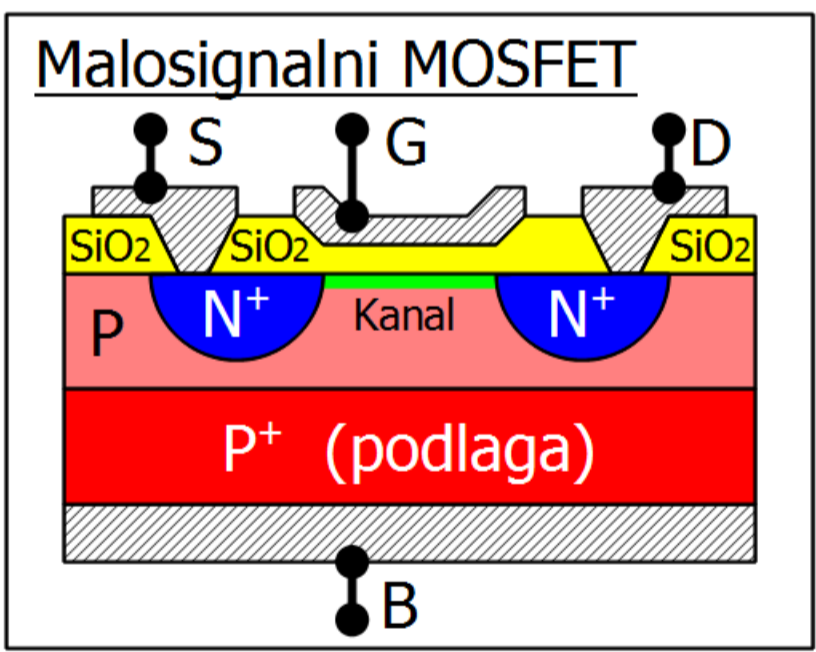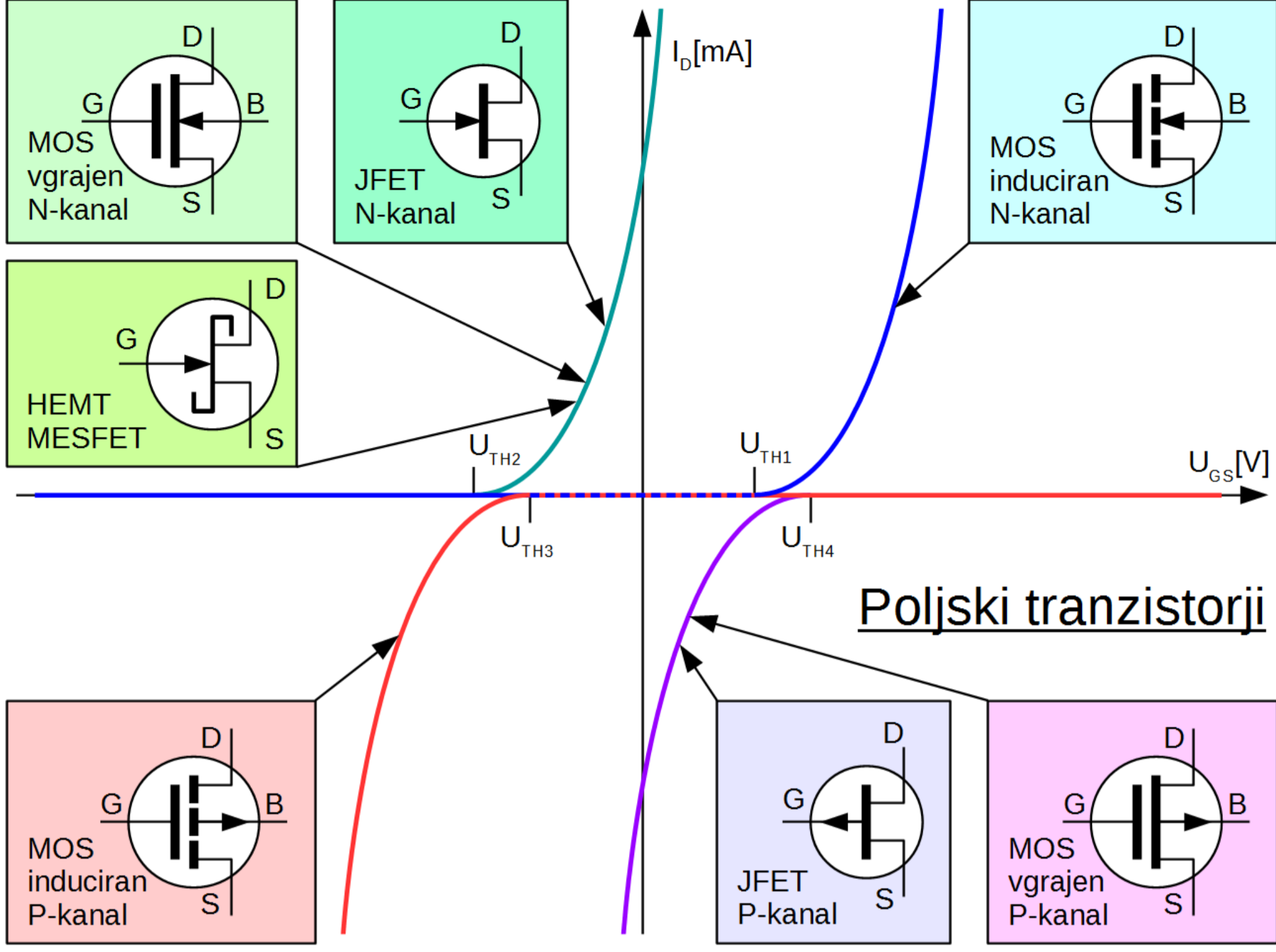


**Izvedbe MOS tranzistorjev**

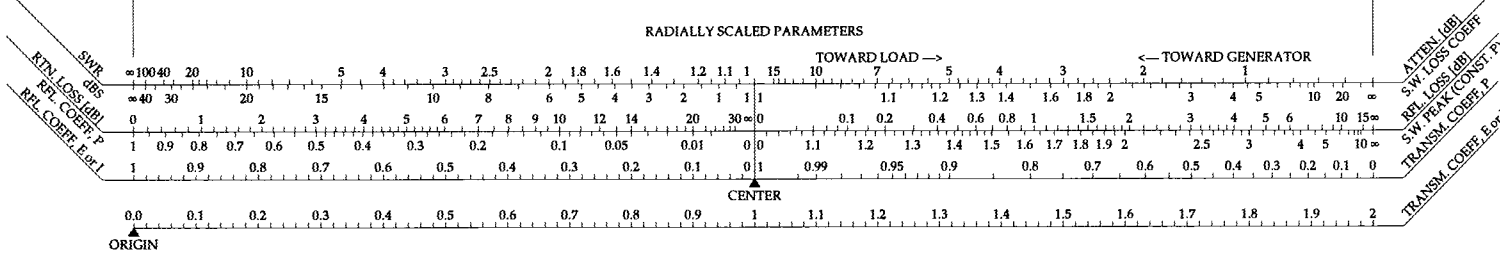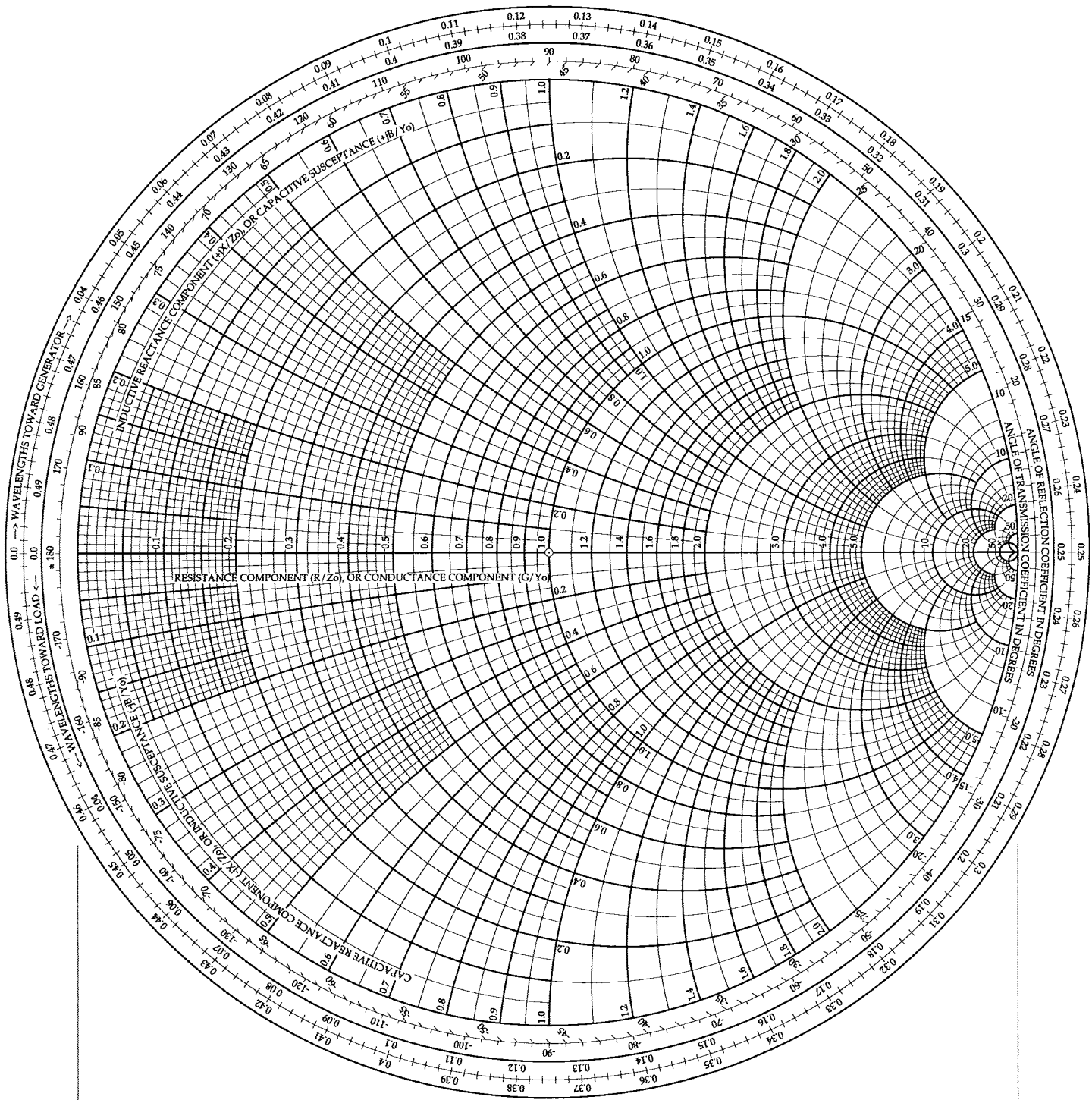
# Smith-ov diagram: impedanca/admitanca v merilu odbojnosti



S-parametri:

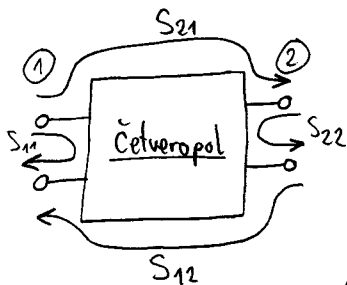


Obremenjen četveropol:

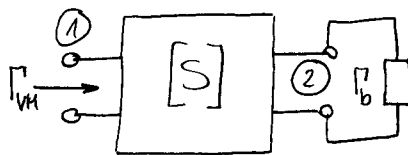

$$\Gamma_{VH} = S_{11} + S_{21} S_{12} (\Gamma_b + S_{22} \Gamma_b^2 + S_{22}^2 \Gamma_b^3 + \dots)$$

$$\Gamma_{VH} = S_{11} + \frac{S_{21} S_{12} \Gamma_b}{1 - S_{22} \Gamma_b}$$


Zaporedni Z:

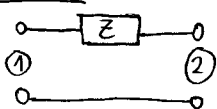

$$S_{11} = S_{22} = \frac{Z}{Z + 2Z_k}$$

$$S_{21} = S_{12} = \frac{2Z_k}{Z + 2Z_k}$$

Vzporedni Z:

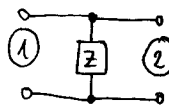


$$S_{11} = S_{22} = \frac{Z || Z_k - Z_k}{Z || Z_k + Z_k} = \frac{-Z_k}{2Z + Z_k}$$

$$S_{21} = S_{12} = \frac{2Z || Z_k}{Z || Z_k + Z_k} = \frac{2Z}{2Z + Z_k}$$

Verižna četveropola:

$$S_{11} = S_{11}' + \frac{S_{21}' S_{12}'' S_{11}''}{1 - S_{22}'' S_{11}'}$$

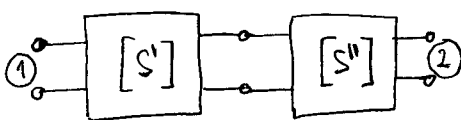
$$S_{12} = \frac{S_{12}'' S_{12}'}{1 - S_{22}'' S_{11}'}$$



$$S_{21} = \frac{S_{21}' S_{21}''}{1 - S_{11}'' S_{22}'}$$

$$S_{22} = S_{22}'' + \frac{S_{12}'' S_{21}' S_{22}'}{1 - S_{22}'' S_{11}'}$$

Rollett-ova stabilnost:

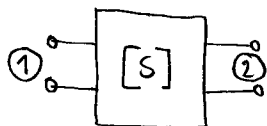

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12} S_{21}|}$$


$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

Brezpogojna stabilnost:

$$K > 1 \text{ in } |\Delta| < 1$$

$$(|S_{11}| < 1 \quad |S_{22}| < 1)$$

Ojačanje:

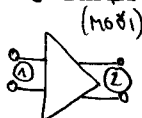

Maximum Available Gain:

(K > 1) RAZPOLOŽLJIVO

$$MAG = (K - \sqrt{K^2 - 1}) \frac{|S_{21}|}{|S_{12}|}$$

Maximum Stable Gain:

(K ≤ 1) STABILNO

$$MSG = \frac{|S_{21}|}{|S_{12}|}$$


Insertion Gain:

VSTAVITVENO

$$G = |S_{21}|^2$$

Brezizgubni vod:

$$S_{11} = S_{22} = 0$$

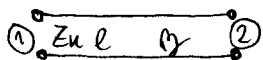

$$S_{21} = S_{12} = e^{-j\beta l}$$

Skok Zk




$$S_{11} = \frac{Z_k - Z_{k1}}{Z_k + Z_{k1}}$$

$$S_{22} = \frac{Z_{k1} - Z_k}{Z_{k1} + Z_k}$$

$$S_{21} = S_{12} = \sqrt{1 - S_{11}^2}$$

Idealni transformator

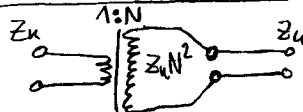

$$S_{11} = \frac{1 - N^2}{1 + N^2}$$

$$S_{22} = \frac{N^2 - 1}{N^2 + 1}$$

$$S_{21} = S_{12} = \frac{2N}{1 + N^2}$$

	S	z	y	h	ABCD
S	$S_{11} \quad S_{12}$ $S_{21} \quad S_{22}$	$S_{11} = \frac{(z'_{11} - 1)(z'_{22} + 1) - z'_{12} z'_{21}}{\Delta_1}$ $S_{12} = \frac{2z'_{12}}{\Delta_1}$ $S_{21} = \frac{2z'_{21}}{\Delta_1}$ $S_{22} = \frac{(z'_{11} + 1)(z'_{22} - 1) - z'_{12} z'_{21}}{\Delta_1}$	$S_{11} = \frac{(1 - y'_{11}x_1 + y'_{22}) + y'_{12}y'_{21}}{\Delta_2}$ $S_{12} = \frac{-2y'_{12}}{\Delta_2}$ $S_{21} = \frac{-2y'_{21}}{\Delta_2}$ $S_{22} = \frac{(1 + y'_{11}x_1 - y'_{22}) + y'_{12}y'_{21}}{\Delta_2}$	$S_{11} = \frac{(h'_{11} - 1)(h'_{22} + 1) - h'_{12}h'_{21}}{\Delta_3}$ $S_{12} = \frac{2h'_{12}}{\Delta_3}$ $S_{21} = \frac{-2h'_{21}}{\Delta_3}$ $S_{22} = \frac{(1 + h'_{11}x_1 - h'_{22}) + h'_{12}h'_{21}}{\Delta_3}$	$A' + B' - C' - D' \quad \frac{2(A'D' - B'C')}{\Delta_4}$ $\frac{2}{\Delta_4} \quad \frac{-A' + B' - C' + D'}{\Delta_4}$
z	$z'_{11} = \frac{(1 + S_{11}x_1 - S_{22}) + S_{12}S_{21}}{\Delta_5}$ $z'_{12} = \frac{2S_{12}}{\Delta_5}$ $z'_{21} = \frac{2S_{21}}{\Delta_5}$ $z'_{22} = \frac{(1 - S_{11}x_1 + S_{22}) + S_{12}S_{21}}{\Delta_5}$	$z_{11} \quad z_{12}$ $z_{21} \quad z_{22}$	$\frac{y_{22}}{ y } \quad \frac{-y_{12}}{ y }$ $\frac{-y_{21}}{ y } \quad \frac{y_{11}}{ y }$	$\frac{ h }{h_{22}} \quad \frac{h_{12}}{h_{22}}$ $\frac{-h_{21}}{h_{22}} \quad \frac{1}{h_{22}}$	$\frac{A}{C} \quad \frac{\Delta_8}{C}$ $\frac{1}{C} \quad \frac{D}{C}$
y	$y'_{11} = \frac{(1 - S_{11}x_1 + S_{22}) + S_{12}S_{21}}{\Delta_6}$ $y'_{12} = \frac{-2S_{12}}{\Delta_6}$ $y'_{21} = \frac{-2S_{21}}{\Delta_6}$ $y'_{22} = \frac{(1 + S_{11}x_1 - S_{22}) + S_{12}S_{21}}{\Delta_6}$	$\frac{z_{22}}{ z } \quad \frac{-z_{12}}{ z }$ $\frac{-z_{21}}{ z } \quad \frac{z_{11}}{ z }$	$y_{11} \quad y_{12}$ $y_{21} \quad y_{22}$	$\frac{1}{h_{11}} \quad \frac{-h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}} \quad \frac{ h }{h_{11}}$	$\frac{D}{B} \quad \frac{-\Delta_9}{B}$ $\frac{-1}{B} \quad \frac{A}{B}$
h	$h'_{11} = \frac{(1 + S_{11}x_1 + S_{22}) - S_{12}S_{21}}{\Delta_7}$ $h'_{12} = \frac{2S_{12}}{\Delta_7}$ $h'_{21} = \frac{-2S_{21}}{\Delta_7}$ $h'_{22} = \frac{(1 - S_{22}x_1 - S_{11}) - S_{12}S_{21}}{\Delta_7}$	$\frac{ z }{z_{22}} \quad \frac{z_{12}}{z_{22}}$ $\frac{-z_{21}}{z_{22}} \quad \frac{1}{z_{22}}$	$\frac{1}{y_{11}} \quad \frac{-y_{12}}{y_{11}}$ $\frac{y_{21}}{y_{11}} \quad \frac{ y }{y_{11}}$	$h_{11} \quad h_{12}$ $h_{21} \quad h_{22}$	$\frac{B}{D} \quad \frac{\Delta_8}{D}$ $\frac{-1}{D} \quad \frac{C}{D}$
ABCD	$A' = \frac{(1 + S_{11}x_1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$ $B' = \frac{(1 + S_{11}x_1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$ $C' = \frac{(1 - S_{11}x_1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$ $D' = \frac{(1 - S_{11}x_1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{z_{11}}{z_{21}} \quad \frac{ z }{z_{21}}$ $\frac{1}{z_{21}} \quad \frac{z_{22}}{z_{21}}$	$\frac{-y_{22}}{y_{21}} \quad \frac{-1}{y_{21}}$ $\frac{- y }{y_{21}} \quad \frac{-y_{11}}{y_{21}}$	$\frac{- h }{h_{21}} \quad \frac{-h_{11}}{h_{21}}$ $\frac{-h_{22}}{h_{21}} \quad \frac{-1}{h_{21}}$	$A \quad B$ $C \quad D$

$$\Delta_1 = (z'_{11} + 1)(z'_{22} + 1) - z'_{12}z'_{21}$$

$$\Delta_2 = (1 + y'_{11}x_1 + y'_{22}) - y'_{12}y'_{21}$$

$$\Delta_3 = (h'_{11} + 1)(h'_{22} + 1) - h'_{12}h'_{21}$$

$$\Delta_4 = A' + B' - C' + D'$$

$$\Delta_5 = (1 - S_{11}x_1 - S_{22}) - S_{12}S_{21}$$

$$\Delta_6 = (1 + S_{11}x_1 + S_{22}) - S_{12}S_{21}$$

$$\Delta_7 = (1 - S_{11}x_1 + S_{22}) + S_{12}S_{21}$$

$$\Delta_8 = AD - BC$$

$$z'_{11} = z_{11}/Z_0, \quad z'_{12} = z_{12}/Z_0, \quad z'_{21} = z_{21}/Z_0, \quad z'_{22} = z_{22}/Z_0$$

$$y'_{11} = y_{11}/Z_0, \quad y'_{12} = y_{12}/Z_0, \quad y'_{21} = y_{21}/Z_0, \quad y'_{22} = y_{22}/Z_0$$

$$h'_{11} = h_{11}/Z_0, \quad h'_{12} = h_{12}, \quad h'_{21} = h_{21}, \quad h'_{22} = h_{22}/Z_0$$

$$A' = A, \quad B' = B/Z_0, \quad C' = CZ_0, \quad D' = D$$


$$|z| = z_{11}z_{22} - z_{12}z_{21}$$

$$|y| = y_{11}y_{22} - y_{12}y_{21}$$

$$|h| = h_{11}h_{22} - h_{12}h_{21}$$

Z = impedančna matrika  
Y = admitančna matrika  
h = hibridna matrika  
ABCD = verižna matrika

# Pretvorbe parametrov četveropola

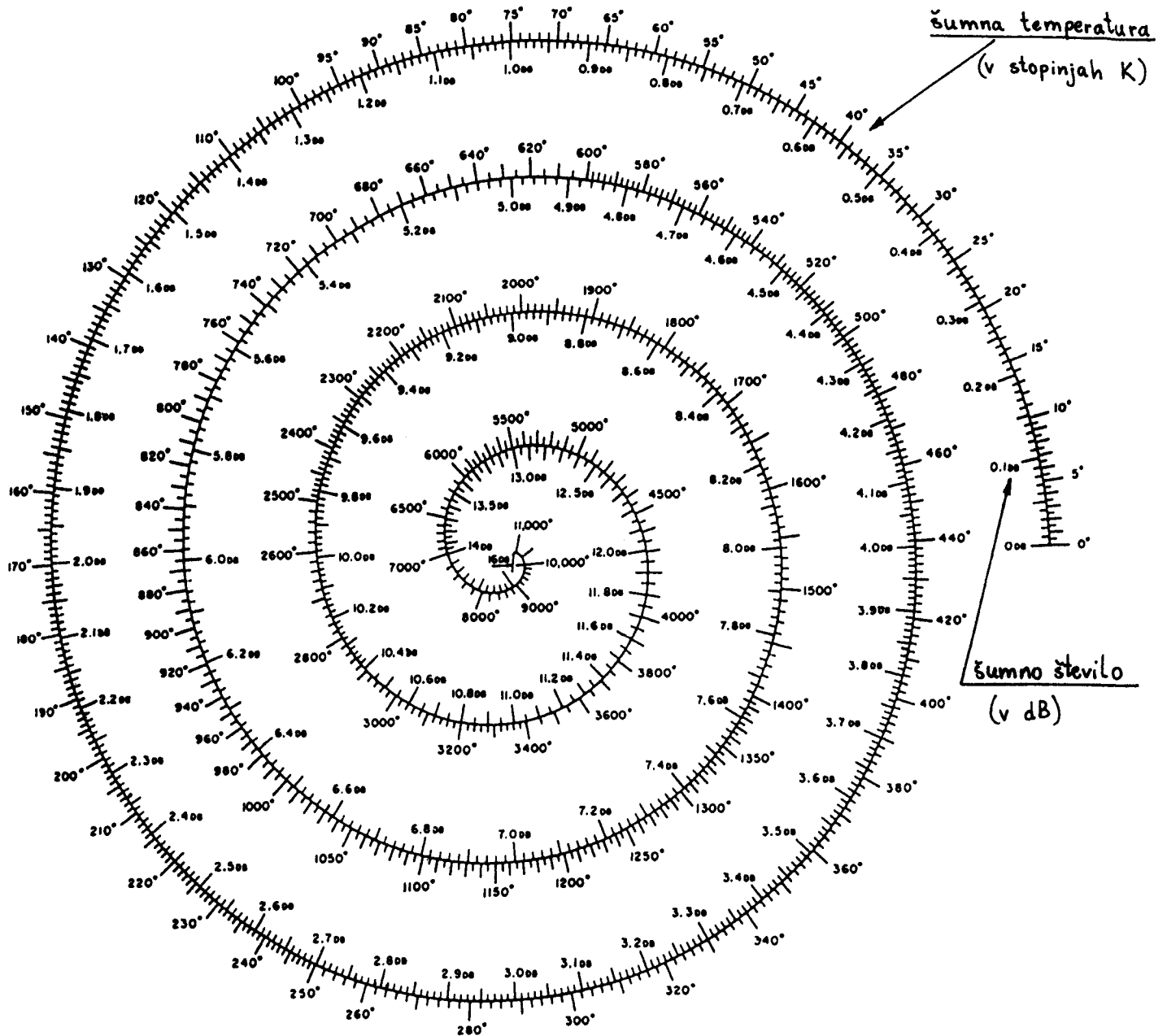


$$F[\text{dB}] = 10 \cdot \log_{10} \left( 1 + \frac{T}{290 \text{ K}} \right)$$

$$T[\text{K}] = 290 \text{ K} \cdot \left( 10^{\frac{F}{10}} - 1 \right)$$

Povezava med šumno temperaturo in šumnim številom
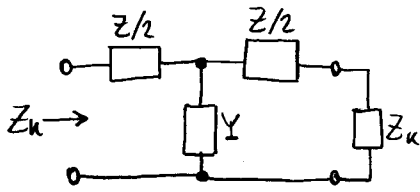
# Frekvenčna sita: izračun $Z_k$ odseka T




$$Z_k = \frac{Z}{2} + \frac{1}{Y + \frac{1}{\frac{Z}{2} + Z_k}}$$

$$\frac{Z}{Z_k^2 - (\frac{Z}{2})^2} = Y$$

$$\frac{1}{Z_k - \frac{Z}{2}} - \frac{1}{Z_k + \frac{Z}{2}} = Y$$

$$Z_k = \sqrt{\frac{Z}{Y} + \left(\frac{Z}{2}\right)^2}$$

## LPF = nizkoprepustno:

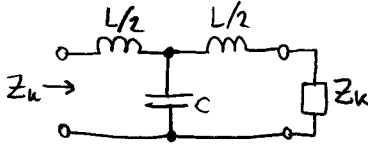

$$Z = j\omega L$$

$$Y = j\omega C$$

$$Z_k = 0$$

$$Z_k = \sqrt{\frac{L}{C} - \left(\frac{\omega L}{2}\right)^2}$$


$$\omega < \omega_0 \rightarrow Z_k = R$$

$$\omega > \omega_0 \rightarrow Z_k = jX$$

$$\frac{L}{C} - \left(\frac{\omega_0 L}{2}\right)^2 = 0$$

$$\omega_0 = \frac{2}{\sqrt{LC}}$$

## HPF = visokoprepustno:

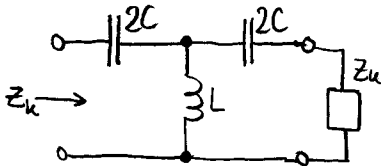

$$Z = \frac{1}{j\omega C}$$

$$Y = \frac{1}{j\omega L}$$

$$Z_k = 0$$

$$Z_k = \sqrt{\frac{L}{C} - \left(\frac{1}{2\omega C}\right)^2}$$


$$\omega < \omega_0 \rightarrow Z_k = -jX$$

$$\omega > \omega_0 \rightarrow Z_k = R$$

$$\frac{L}{C} - \left(\frac{1}{2\omega_0 C}\right)^2 = 0$$

$$\omega_0 = \frac{1}{2\sqrt{LC}}$$

## BPF = pasovno prepustno:

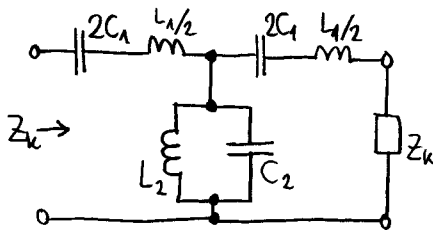

$$Z = \frac{1}{j\omega C_1} + j\omega L_1 = j\left(\omega L_1 - \frac{1}{\omega C_1}\right)$$

$$Y = \frac{1}{j\omega L_2} + j\omega C_2 = j\left(\omega C_2 - \frac{1}{\omega L_2}\right)$$

$$Z_k = 0$$

$$Z_k = \sqrt{\frac{\omega L_1 - \frac{1}{\omega C_1}}{\omega C_2 - \frac{1}{\omega L_2}} - \left(\frac{\omega L_1 - \frac{1}{\omega C_1}}{2}\right)^2}$$

$$\omega < \omega_0 \rightarrow Z_k = -jX$$

$$\omega_0 < \omega < \omega_{ot} \rightarrow Z_k = R$$

$$\omega > \omega_{ot} \rightarrow Z_k = jX$$


$$4 = \left(\omega_0 L_1 - \frac{1}{\omega_0 C_1}\right) \left(\omega_0 C_2 - \frac{1}{\omega_0 L_2}\right)$$

$$\omega_0^4 L_1 C_2 - \omega_0^2 \left(\frac{L_1}{L_2} + \frac{C_2}{C_1} + 4\right) + \frac{1}{L_2 C_1} = 0$$

$$\omega_0 = \sqrt{\frac{\left(\frac{L_1}{L_2} + \frac{C_2}{C_1} + 4\right) \pm \sqrt{\left(\frac{L_1}{L_2} + \frac{C_2}{C_1} + 4\right)^2 - 4 \frac{L_1 C_2}{L_2 C_1}}}{2 L_1 C_2}}$$

### BPF ( $C_1, C_2, L_2$ )

$$L_1 = 0$$

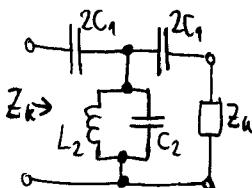

$$Z_k = 0$$


$$\omega_0 = \frac{1}{\sqrt{L_2(4C_1 + C_2)}}$$

$$Z_k = \infty$$

$$\omega_{\infty} = \frac{1}{\sqrt{L_2 C_2}}$$


### BPF ( $C_2, L_1, L_2$ )

$$C_1 \rightarrow \infty$$

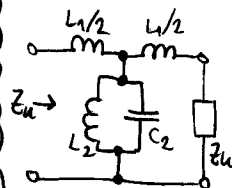

### BPF ( $C_1, C_2, L_1$ )

$$L_2 \rightarrow \infty$$

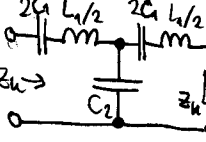


$$\omega < \omega_0 \rightarrow Z_k = -jX$$

$$\omega_0 < \omega < \omega_{\infty} \rightarrow Z_k = R$$

$$\omega > \omega_{\infty} \rightarrow Z_k = -jX$$

### BPF ( $C_1, L_1, L_2$ )

$$C_2 = 0$$

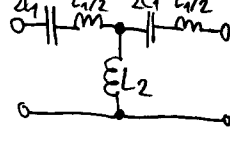






$$\omega_0 = \omega_r \sqrt{\frac{m+2 \pm 2\sqrt{m+1}}{m}}$$

$$Z_k = \sqrt{\frac{1}{m} \left(\frac{L_1}{C_1}\right) - \left(\frac{\omega L_1 - \frac{1}{\omega C_1}}{2}\right)^2}$$
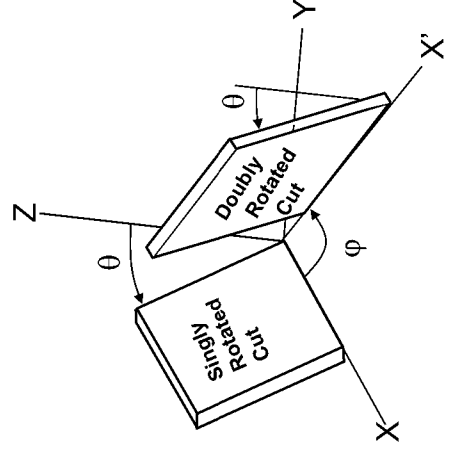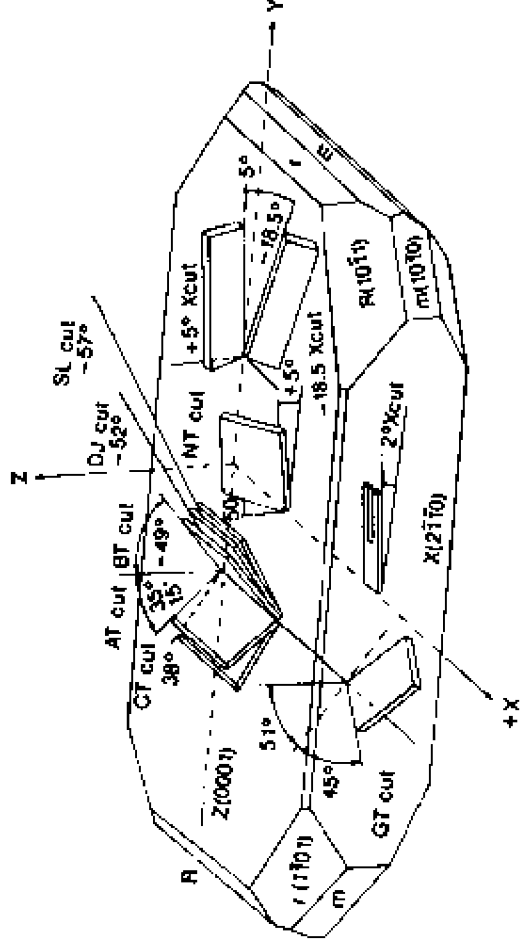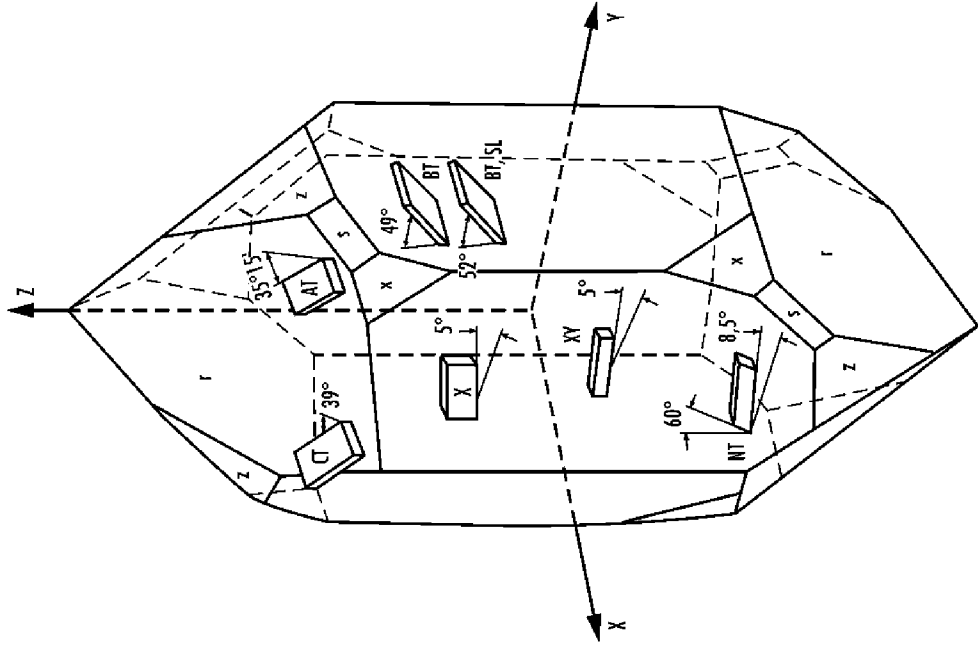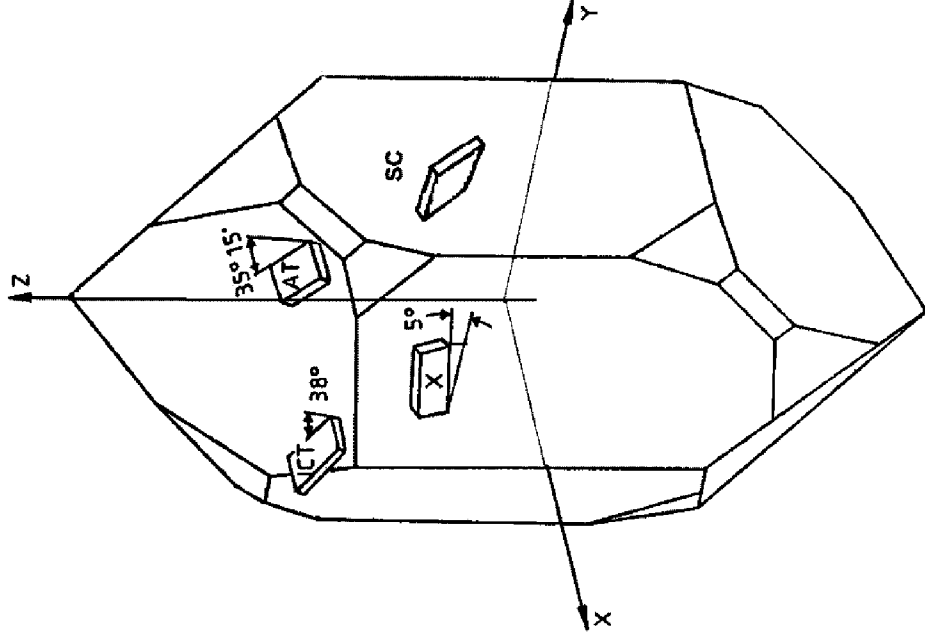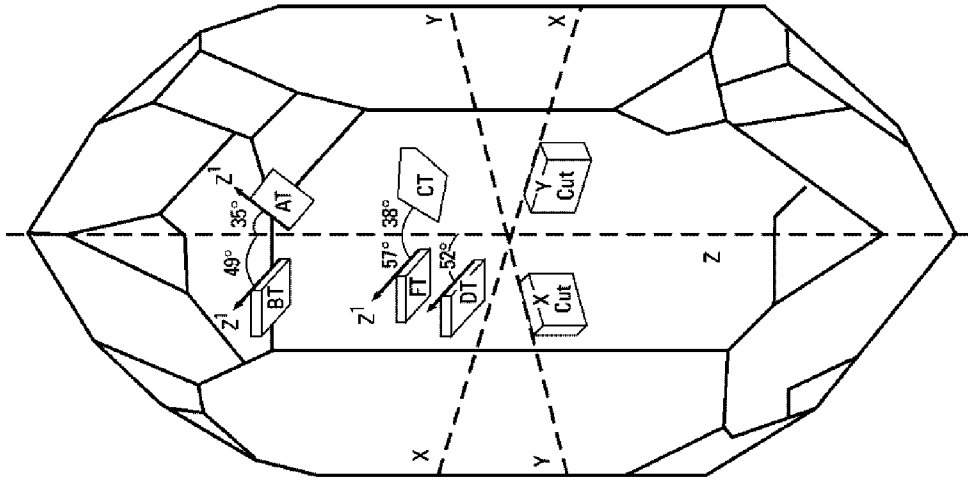
### BPF $L_1 C_1 = L_2 C_2$


$$\frac{L_1}{L_2} = \frac{C_2}{C_1} = m$$

$$\frac{1}{\sqrt{L_1 C_1}} = \frac{1}{\sqrt{L_2 C_2}} = \omega_r$$



Rezine kristala kremena


# Resonant Vibrations of a Quartz Plate

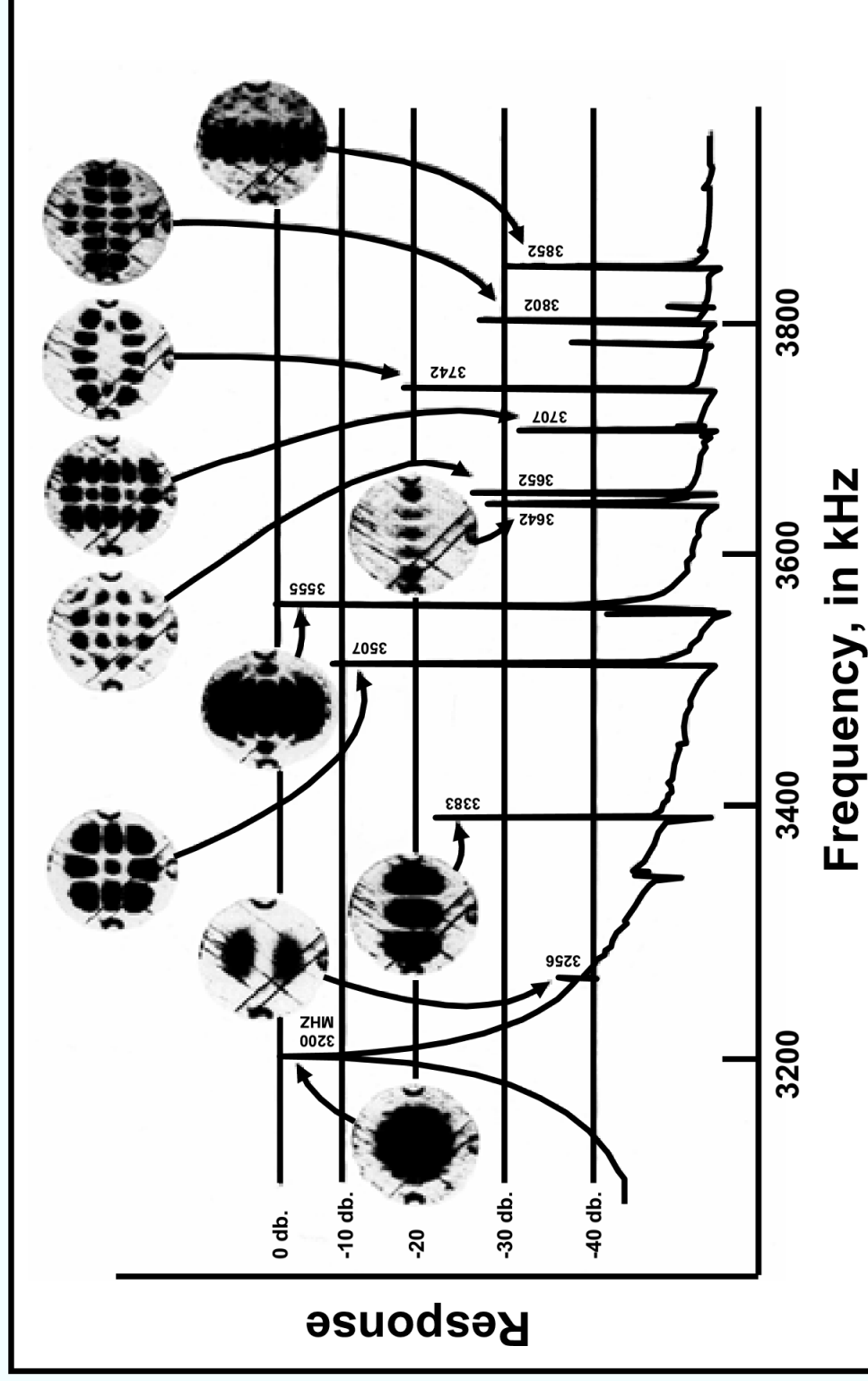

X-ray topographs ( $21\cdot\bar{0}$  plane) of various modes excited during a frequency scan of a fundamental mode, circular, AT-cut resonator. The first peak, at 3.2 MHz, is the main mode; all others are unwanted modes. Dark areas correspond to high amplitudes of displacement.




Refleksni  
klistron  
2K25

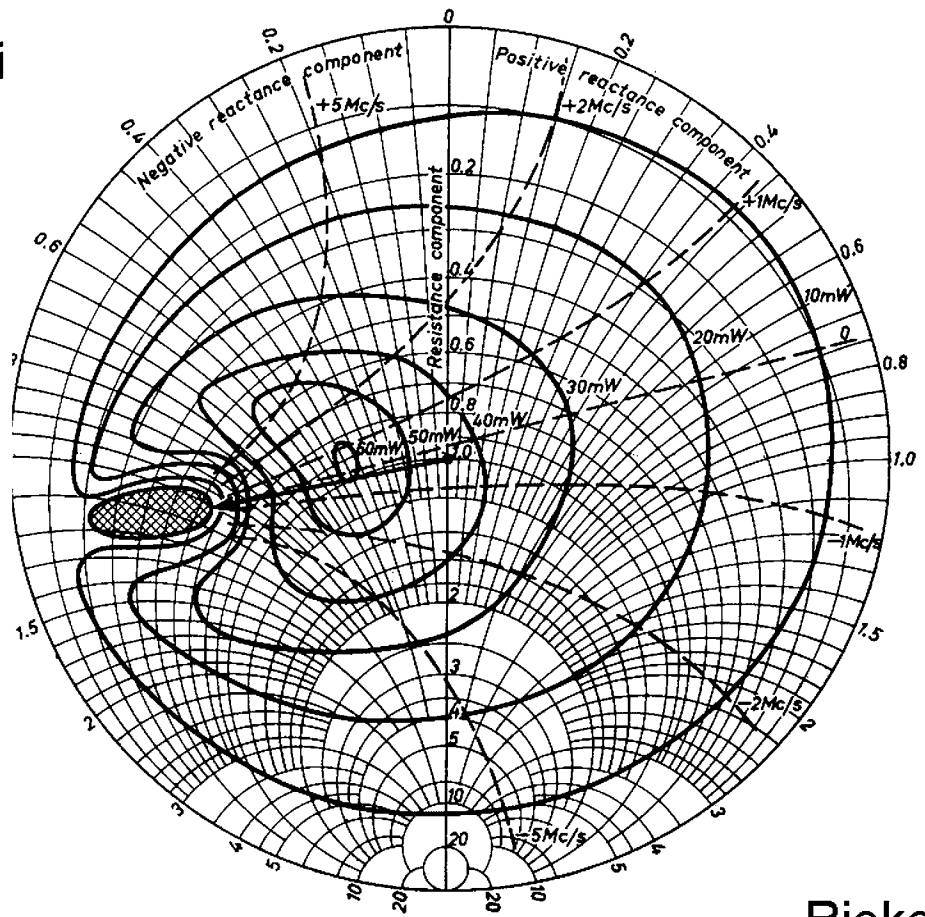


Rieke-jev  
diagram

Magnetron  
2M214

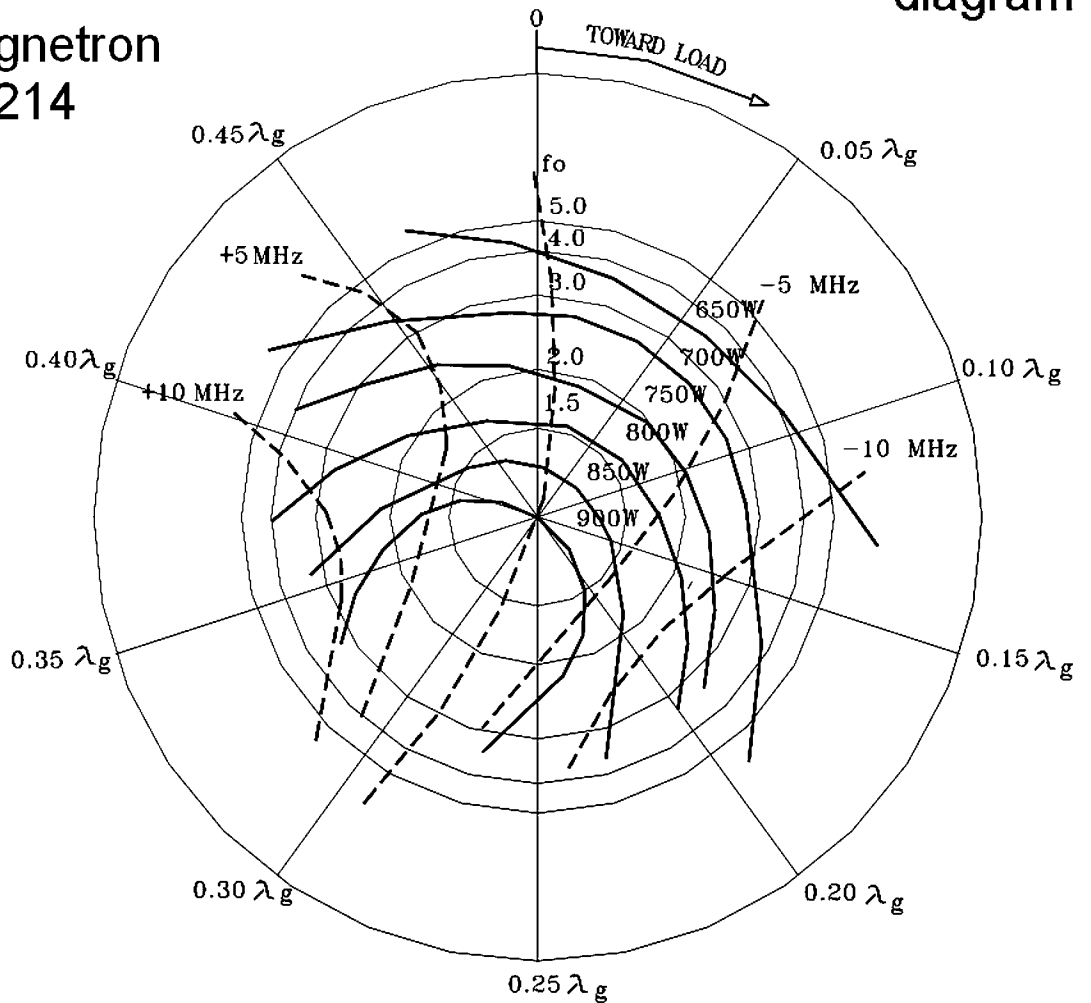
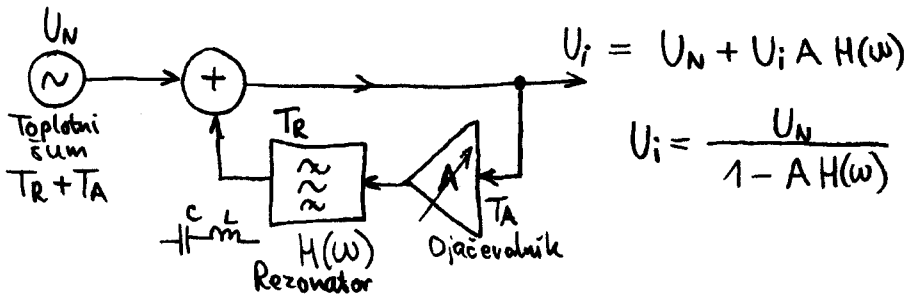
# Fazni šum visokofrekvenčnega oscilatorja



Ustajeno nihanje oscilatorja @  $\omega_0 \rightarrow A$  nastavljen za  $A H(\omega_0) = 1$

$$A H(\omega) = \frac{\Sigma R}{\Sigma R + j\omega L + \frac{1}{j\omega C}}$$

$\omega = \omega_0 + \Delta\omega$  (majhen odvik  $\Delta\omega \ll \omega_0$ )

$$j\omega L = j\omega_0 L + j\Delta\omega L$$

$$A H(\omega) \approx \frac{1}{1 + \frac{2j\Delta\omega L}{\Sigma R}}$$

$$\frac{1}{j\omega C} = \frac{1}{j\omega_0(1 + \frac{\Delta\omega}{\omega_0})C} \approx \frac{1}{j\omega_0 C} \left(1 - \frac{\Delta\omega}{\omega_0}\right)$$

$$j\omega L + \frac{1}{j\omega C} \approx j\omega_0 L - \frac{1}{j\omega_0 C} \frac{\Delta\omega}{\omega_0} = 2j\Delta\omega L$$

$$A H(\omega) \approx \frac{1}{1 + 2jQ_L \frac{\Delta\omega}{\omega_0}}$$

$$\frac{2j\Delta\omega L}{\Sigma R} = 2j \frac{\omega_0 L}{\Sigma R} \frac{\Delta\omega}{\omega_0} = 2jQ_L \frac{\Delta\omega}{\omega_0}$$

$$U_i = \frac{U_N}{1 - \frac{1}{1 + 2jQ_L \frac{\Delta\omega}{\omega_0}}} = U_N \left(1 + \frac{1}{2jQ_L} \frac{\omega_0}{\Delta\omega}\right)$$

$$P = \alpha |U|^2$$

obremenjeni Q

$$P_i = P_N \left[1 + \left(\frac{1}{2Q_L} \cdot \frac{\omega_0}{\Delta\omega}\right)^2\right] = P_N \left[1 + \left(\frac{1}{2Q_L} \cdot \frac{f_0}{\Delta f}\right)^2\right]$$

$$P_N = B k_B (T_R + T_A) = B k_B T_0 F \left(1 + \frac{f_c}{|\Delta f|}\right)$$

Šum  $1/f$ :

BJT, JFET  $\rightarrow f_c = 1\text{kHz} - 10\text{kHz}$

MOSFET, GaAs FET, HEMT  $\rightarrow f_c = 1\text{MHz} - 10\text{MHz}$

$$L(\Delta f) = \frac{1}{2} \frac{P_i}{P_0 B} = \frac{1}{2} \left[1 + \left(\frac{f_0}{2Q_L \Delta f}\right)^2\right] \frac{k_B T_0 F}{P_0} \left(1 + \frac{f_c}{|\Delta f|}\right)$$

[1/Hz] SPEKTRALNA GOSTOTA FAZNEGA ŠUMA

brez amplitudnega šuma

Leeson -ova enačba (David B. Leeson 1966)


$$L(\Delta f)_{\text{dBc}} = 10 \log_{10} \frac{1}{2} \left[1 + \left(\frac{f_0}{2Q_L \Delta f}\right)^2\right] \frac{k_B T_0 F}{P_0} \left(1 + \frac{f_c}{|\Delta f|}\right) \cdot 1\text{Hz} \quad [\text{dBc/Hz}]$$

Fazni šum:  $\sigma_\varphi(f_a, f_b) = \sqrt{2 \int_{f_a}^{f_b} L(\Delta f) d\Delta f}$  [rad] Residual PM noise

Frekvenčni šum:  $\sigma_f(f_a, f_b) = \sqrt{2 \int_{f_a}^{f_b} \Delta f^2 L(\Delta f) d\Delta f}$  [Hz] Residual FM noise

Drhtenje (jitter):  $\sigma_t(f_a, f_b) = \frac{\sigma_\varphi(f_a, f_b)}{2\pi f_0} = \frac{1}{2\pi f_0} \sqrt{2 \int_{f_a}^{f_b} L(\Delta f) d\Delta f}$  [s]

# Stabilnost fazno-sklenjene zanke

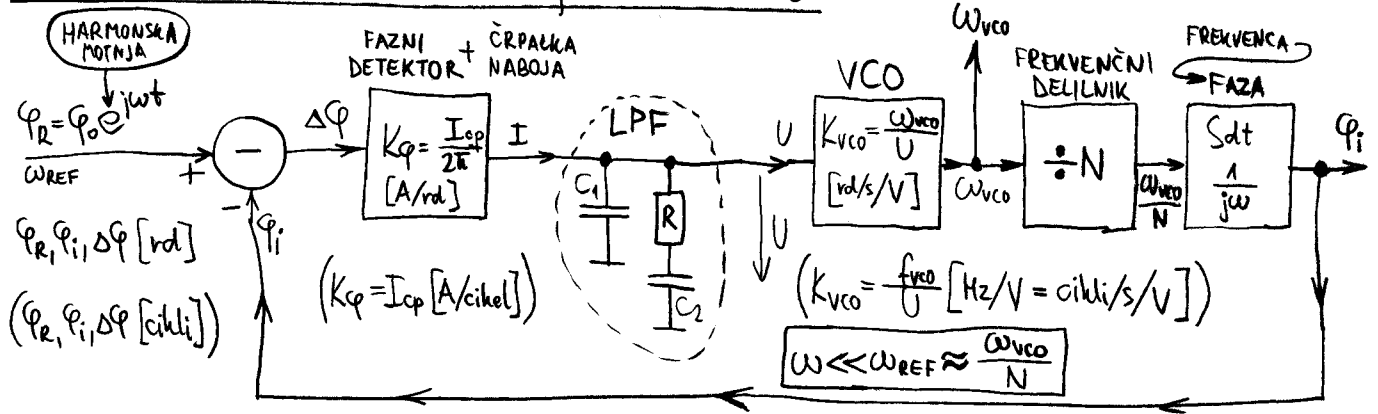

$$\Delta\varphi = \varphi_R - \varphi_i = \varphi_R - \Delta\varphi H(\omega) \rightarrow \Delta\varphi = \frac{\varphi_R}{1+H(\omega)} ; \varphi_i = \varphi_R \frac{H(\omega)}{1+H(\omega)}$$

$$H(\omega) = K_\varphi \cdot \frac{1}{j\omega C_1 + \frac{1}{R + \frac{1}{j\omega C_2}}} \cdot K_{vco} \cdot \frac{1}{N} \cdot \frac{1}{j\omega} = \frac{K_\varphi K_{vco}}{j\omega N} \cdot \frac{j\omega RC_2 + 1}{-\omega^2 RC_1 C_2 + j\omega(C_1 + C_2)}$$


SKLADNE MERSKE ENOTE

$$H(\omega) = \frac{K_\varphi K_{vco}}{\omega^2 (C_1 + C_2) N} \cdot \frac{1 + j\omega RC_2}{1 + j\omega R \frac{C_1 C_2}{C_1 + C_2}} = \frac{K_\varphi K_{vco}}{\omega^2 (C_1 + C_2) N} \cdot \frac{1 + j\omega \tilde{T}_2}{1 + j\omega \tilde{T}_1}$$

$$\tilde{T}_2 = RC_2$$

$$\tilde{T}_1 = R \frac{C_1 C_2}{C_1 + C_2}$$

Nyquist:

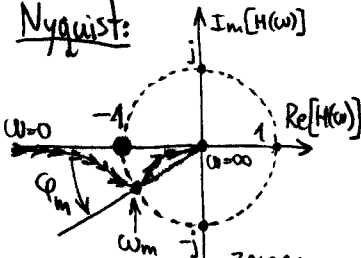

$$\varphi_m = \arctg \frac{\omega_m (\tilde{T}_2 - \tilde{T}_1)}{1 + \omega_m^2 \tilde{T}_1 \tilde{T}_2}$$

$$0 = \frac{d}{d\omega} \left( \frac{\omega (\tilde{T}_2 - \tilde{T}_1)}{1 + \omega^2 \tilde{T}_1 \tilde{T}_2} \right) = \frac{(\tilde{T}_2 - \tilde{T}_1) (1 - \omega_m^2 \tilde{T}_1 \tilde{T}_2)}{(1 + \omega_m^2 \tilde{T}_1 \tilde{T}_2)^2}$$

$$\varphi_m = \arctg \frac{m-1}{2\sqrt{m}}$$

$$\omega_m = \frac{1}{\sqrt{\tilde{T}_2 \tilde{T}_1}} = \frac{1}{\tilde{T}_1 \sqrt{m}}$$

$$\tilde{T}_2 = m \tilde{T}_1$$


$\varphi_m \equiv$  PHASE MARGIN

ZALOGA FAZE

$$1 = |H(\omega_m)| = \frac{K_\varphi K_{vco}}{\omega_m^2 N C_1 m} \cdot \sqrt{\frac{1+m}{1+\frac{1}{m}}} = \frac{K_\varphi K_{vco}}{\omega_m^2 N C_1 \sqrt{m}}$$

$$C_2 = (m-1) C_1$$
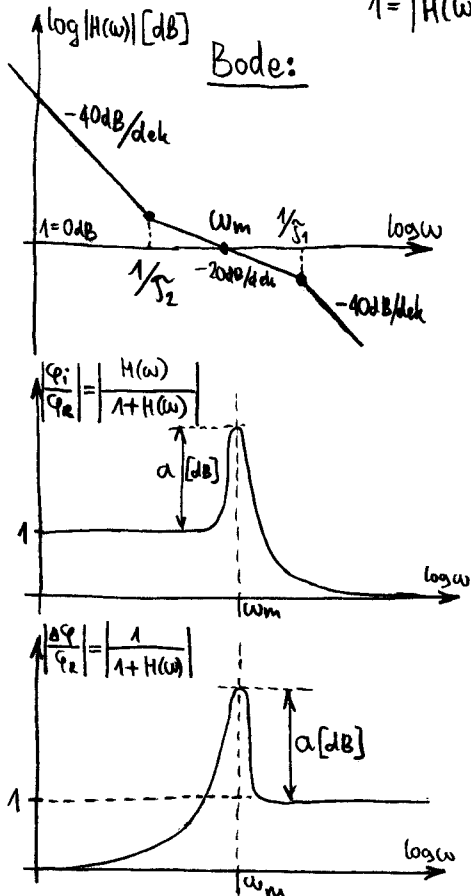
$$C_1 = \frac{K_\varphi K_{vco}}{\omega_m^2 N \sqrt{m}}$$




m	C <sub>2</sub> /C <sub>1</sub>	φ <sub>m</sub> [°]	a [dB] ≈ -20 log φ <sub>m</sub> [rad]
1	0	0°	∞ dB
1.1	0.1	2.7°	26.4 dB
1.2	0.2	5.2°	20.8 dB
1.5	0.5	11.5°	13.9 dB
2	1	19.5°	9.4 dB
3	2	30.0°	5.6 dB
5	4	41.8°	2.7 dB
10	9	54.9°	0.4 dB
20	19	64.8°	—
50	49	73.9°	—
100	99	78.6°	—
200	199	81.9°	—


$$R = \frac{\sqrt{m'}}{\omega_m C_2}$$

$$\omega_m = \sqrt{\frac{K_\varphi K_{vco}}{N C_1 \sqrt{m'}}$$

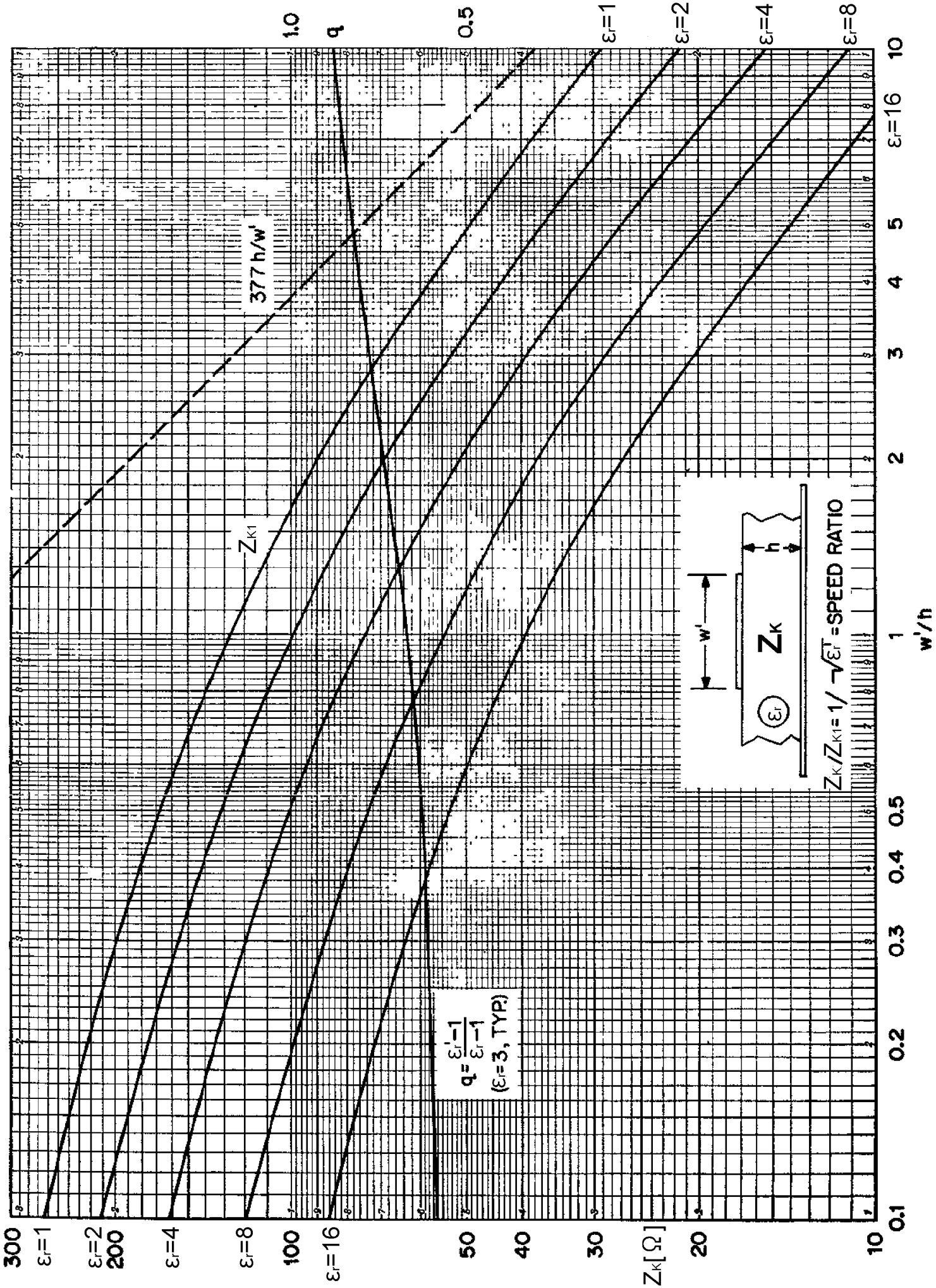
$$B_{ZANKE} \approx \frac{\omega_m}{2\pi}$$



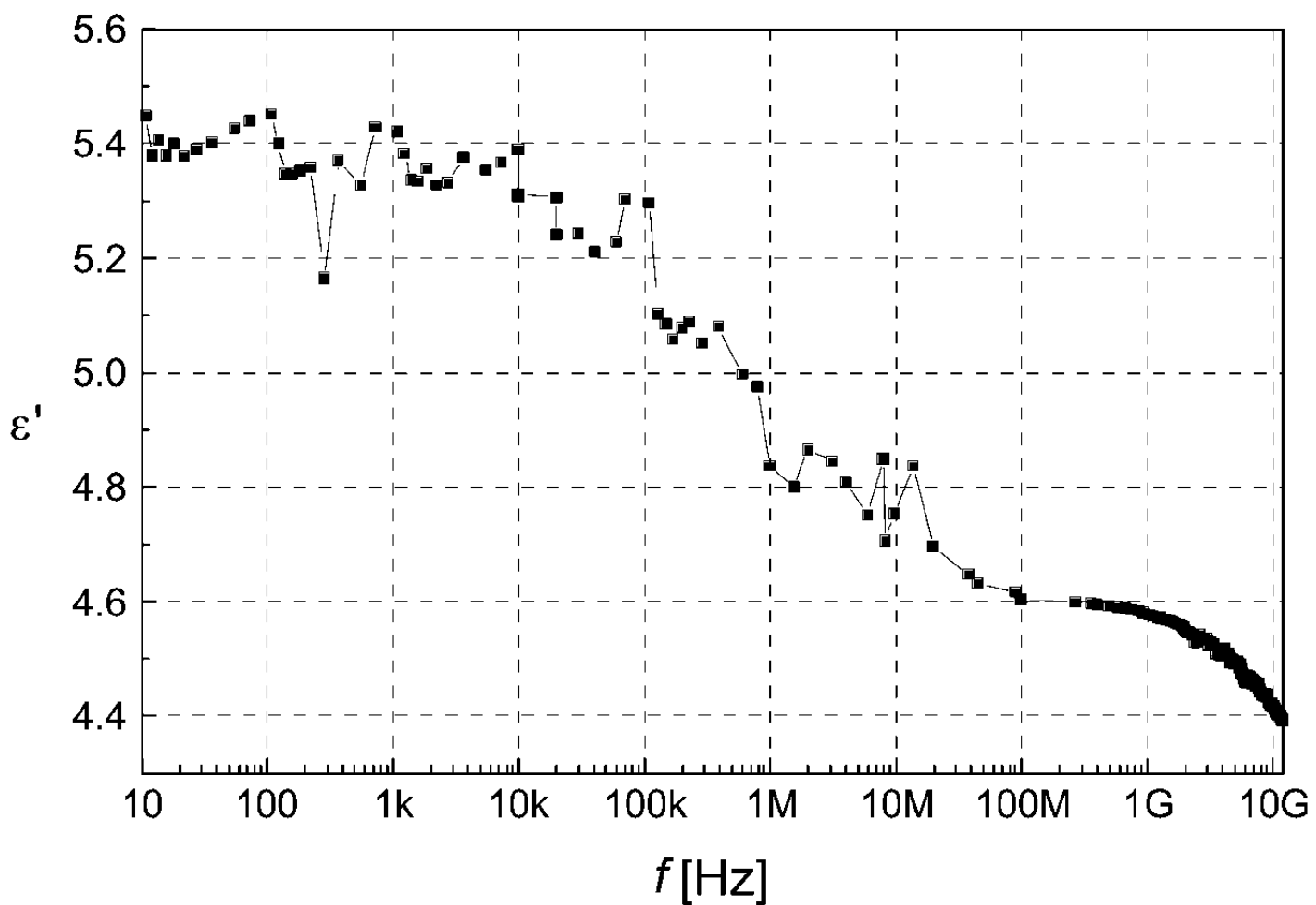Karakteristična impedanca mikrotrakastega voda (TEM približek Wheeler 1977)



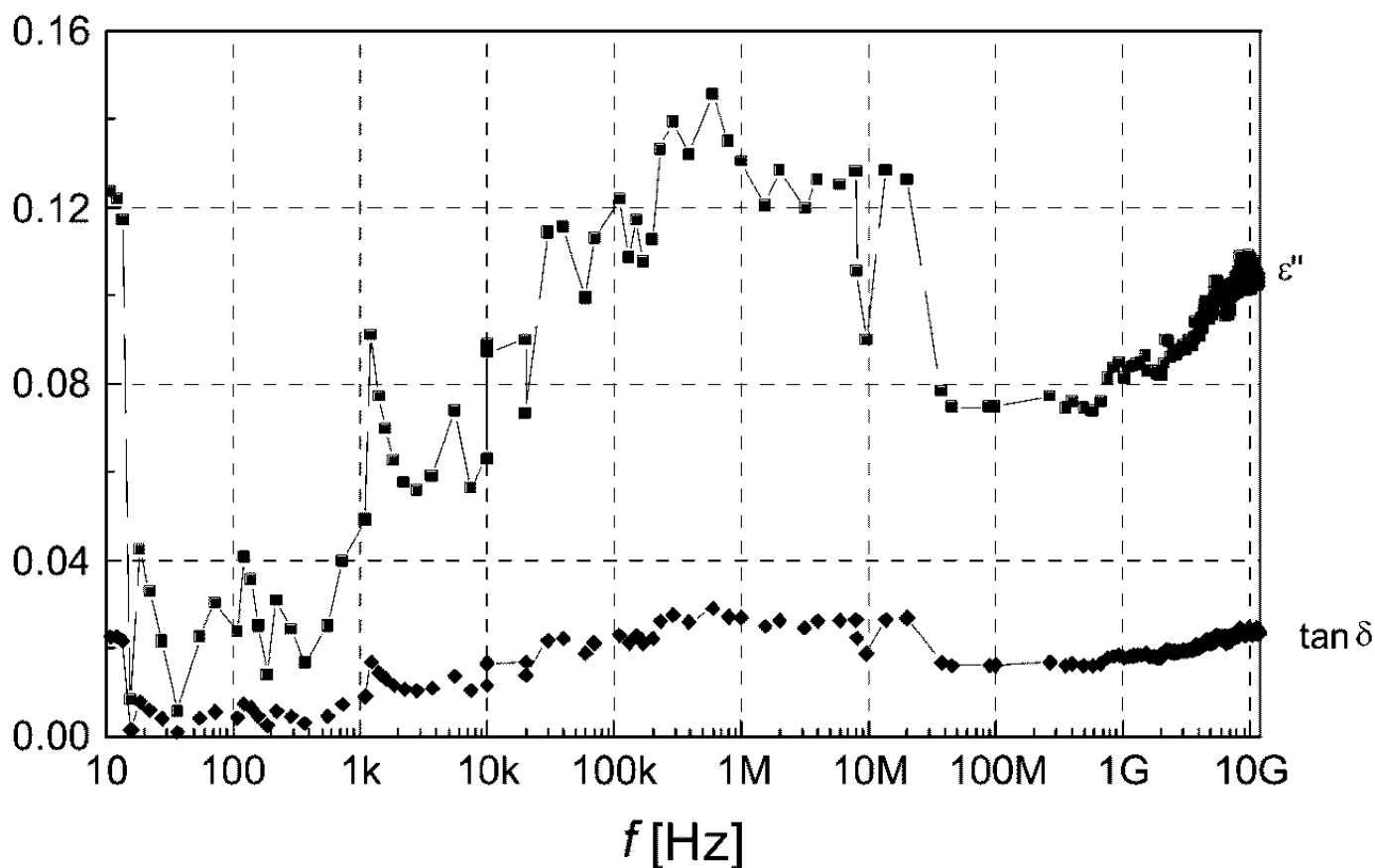Izmerjena relativna dielektričnost vitroplasta



Izmerjene dielektrične izgube vitroplasta